

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

# **EPE** EVERYDAY PRACTICAL ELECTRONICS

www.epemag.com

WIN A  
MICROCHIP  
CAN  
Development  
Kit

## **MULTI-FUNCTION ACTIVE FILTER MODULE**

- Can be configured as a low-pass, high-pass or bandpass filter
- Ideal for use as an active crossover in loudspeaker systems
- Total harmonic distortion typically 0.003%
- Filter attenuation of 80dB per decade

## **LOOP ANTENNA AND AMPLIFIER**

Perfect for long-distance  
AM radio reception

## **BEAM-BREAK FLASH TRIGGER**

Trigger a delay unit/photoflash  
by interrupting an IR light

## **METAL LOCATOR**

Ideal for finding nails, steel  
frames, studs and bracing  
in plaster walls

**PLUS**

## **TEACH-IN 2011 – PART 9**

A not-to-be-missed introduction to analogue-to-digital  
and digital-to-analogue conversion

\$8.99US £4.25UK  
JULY 2011 PRINTED IN THE UK



07

# Low-Power Microcontrollers for Battery-Friendly Design

## Microchip Offers Lowest Currents for Active and Sleep Modes



Extend the battery life in your application using PIC® microcontrollers with nanoWatt XLP Technology and get the industry's lowest currents for Active and Sleep modes.

Microchip's new peripheral-rich PIC12F182X, PIC16F182X and PIC16F19XX families offer active currents of less than 50  $\mu$ A and sleep currents down to 20 nA. These products enable you to create battery-friendly designs that also incorporate capacitive touch sensing, LCD, communications and other functions which help differentiate your products in the marketplace.

Microchip's Enhanced Mid-range 8-bit architecture provides up to 50% increased performance and 14 new instructions that result in up to 40% better code execution over previous-generation 8-bit PIC16 MCUs.

### PIC12F182X and PIC16F182X families include:

- Packages ranging from 8 to 64 pins
- mTouch™ capacitive touch-sensing
- Multiple communications peripherals
- Dual I<sup>2</sup>C™/SPI interfaces
- PWM outputs with independent time bases
- Data signal modulator

### PIC16F19XX family includes:

- mTouch capacitive touch-sensing
- LCD drive
- Multiple communications peripherals
- More PWM channels, with independent timers
- Up to 28 KB of Flash program memory
- Enhanced data EEPROM
- 32-level bandgap reference
- Three rail-to-rail input comparators

### GET STARTED IN 3 EASY STEPS

1. View the Low Power Comparison videos
2. Download the Low Power Tips 'n Tricks
3. Order samples and development tools

[www.microchip.com/XLP](http://www.microchip.com/XLP)



PIC16F193X 'F1' Evaluation Platform - DM164130-1

## Intelligent Electronics start with Microchip

**microchip**  
**DIRECT**  
[www.microchipdirect.com](http://www.microchipdirect.com)

[www.microchip.com/xlp](http://www.microchip.com/xlp)

**MICROCHIP**

ISSN 0262 3617

- **PROJECTS • THEORY •**
- **NEWS • COMMENT •**
- **POPULAR FEATURES •**




**VOL. 40. No 7**

**July 2011**

# **EPE** EVERYDAY PRACTICAL ELECTRONICS

**INCORPORATING ELECTRONICS TODAY INTERNATIONAL**

**www.epemag.com**

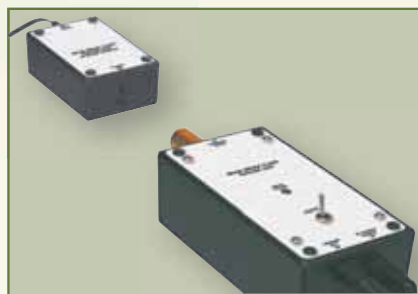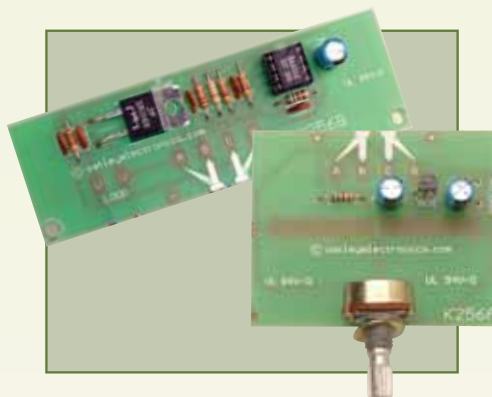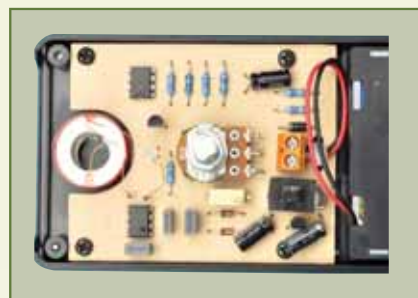

© Wimborne Publishing Ltd 2011. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our August 2011 issue will be published on Thursday 14 July 2011, see page 80 for details.

*Everyday Practical Electronics, July 2011*

## **Projects and Circuits**

- |                                                                                                                                                    |           |
|----------------------------------------------------------------------------------------------------------------------------------------------------|-----------|
| <b>MULTI-FUNCTION ACTIVE FILTER MODULE</b> by John Clarke<br>A versatile design, ideal as an active crossover in loudspeaker systems               | <b>10</b> |
| <b>METAL LOCATOR</b> by John Clarke<br>Perfect for finding steel frames, studs, bracing and nails in plaster walls                                 | <b>22</b> |
| <b>LOOP ANTENNA AND AMPLIFIER</b> by Branko Justic and Ross Tester<br>Listen to faint AM stations, separate close signals – small enough for flats | <b>30</b> |
| <b>A BEAM-BREAK FLASH TRIGGER</b> by Jim Rowe<br>An easy-to-build accessory for the Time Delay Photoflash Trigger                                  | <b>36</b> |
| <b>CONVERTING UNIDEN SCANNERS FOR AIS</b> by Stan Swan<br>How to attach a 'slim Jim' antenna to a popular scanner                                  | <b>42</b> |
| <b>INGENUITY UNLIMITED</b><br>PCB track probing unit                                                                                               | <b>44</b> |

## **Series and Features**

- |                                                                                                                   |           |
|-------------------------------------------------------------------------------------------------------------------|-----------|
| <b>TECHNO TALK</b> by Mark Nelson<br>Blinded by the light                                                         | <b>28</b> |
| <b>TEACH-IN 2011</b> by Mike and Richard Tooley<br>Part 9: Digital-to-analogue and analogue-to-digital conversion | <b>46</b> |
| <b>CIRCUIT SURGERY</b> by Ian Bell<br>LED current drivers                                                         | <b>59</b> |
| <b>PRACTICALLY SPEAKING</b> by Robert Penfold<br>The low down on voltmeters – analogue and digital                | <b>64</b> |
| <b>MAX'S COOL BEANS</b> by Max The Magnificent<br>My Boomerang won't come back... Mega cool iPad oscilloscope     | <b>68</b> |
| <b>NET WORK</b> by Alan Winstanley<br>Radio Ga-Ga... Domotically-enhanced... It's in our DLNA                     | <b>72</b> |

## **Regulars and Services**

- |                                                                                                                  |               |
|------------------------------------------------------------------------------------------------------------------|---------------|
| <b>EDITORIAL</b><br>Computing for the 'common man'                                                               | <b>7</b>      |
| <b>NEWS</b> – Barry Fox highlights technology's leading edge<br>Plus everyday news from the world of electronics | <b>8</b>      |
| <b>MICROCHIP READER OFFER</b><br>EPE Exclusive – Win a Microchip CAN Development Kit                             | <b>21</b>     |
| <b>PIC RESOURCES CD-ROM</b><br>EPE PIC Tutorial V2, plus PIC Toolkit Mk3 and a selection of PIC-related articles | <b>55</b>     |
| <b>EPE BACK ISSUES</b> Did you miss these?                                                                       | <b>56</b>     |
| <b>SUBSCRIBE TO EPE</b> and save money                                                                           | <b>58</b>     |
| <b>EPE PIC PROJECTS CD-ROM VOL.1 AND VOL.2</b><br>A plethora of handPICed projects                               | <b>62, 63</b> |
| <b>CD-ROMS FOR ELECTRONICS</b><br>A wide range of CD-ROMs for hobbyists, students and engineers                  | <b>69</b>     |
| <b>READOUT</b> – Matt Pulzer addresses general points arising                                                    | <b>74</b>     |
| <b>DIRECT BOOK SERVICE</b><br>A wide range of technical books available by mail order, plus more CD-ROMs         | <b>75</b>     |
| <b>EPE PCB SERVICE</b><br>PCBs for EPE projects                                                                  | <b>78</b>     |
| <b>ADVERTISERS INDEX</b>                                                                                         | <b>79</b>     |

**Readers' Services • Editorial and Advertisement Departments**

**7**



**Copyright © 2010, Wimborne Publishing Ltd**  
**(Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU, UK)**  
**and TechBites Interactive Inc.,**  
**(PO Box 857, Madison, Alabama 35758, USA)**  
**All rights reserved.**

## **WARNING!**

The materials and works contained within *EPE Online* — which are made available by Wimborne Publishing Ltd and TechBites Interactive Inc — are copyrighted. You are permitted to make a backup copy of the downloaded file and one (1) hard copy of such materials and works for your personal use.

International copyright laws, however, prohibit any further copying or reproduction of such materials and works, or any republication of any kind. TechBites Interactive Inc and Wimborne Publishing Ltd have used their best efforts in preparing these materials and works. However, TechBites Interactive Inc and Wimborne Publishing Ltd make no warranties of any kind, expressed or implied, with regard to the documentation or data contained herein, and specifically disclaim, without limitation, any implied warranties of merchantability and fitness for a particular purpose. Because of possible variances in the quality and condition of materials and workmanship used by readers, *EPE Online*, its publishers and agents disclaim any responsibility for the safe and proper functioning of reader-constructed projects based on or from information published in these materials and works. In no event shall TechBites Interactive Inc or Wimborne Publishing Ltd be responsible or liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or any other damages in connection with or arising out of furnishing, performance, or use of these materials and works.





**QUASAR**  
electronics  
The Electronic Kit Specialists Since 1993

**Quasar Electronics Limited**  
PO Box 6935, Bishops Cleeve  
CM23 4WP, United Kingdom  
Tel: 01279 467799  
Fax: 01279 267799  
E-mail: sales@quasarelectronics.com  
Web: www.quasarelectronics.com

All prices INCLUDE 20.0% VAT.  
Postage & Packing Options (Up to 0.5Kg gross weight): UK Standard 3-7 Day Delivery - £4.95; UK Mainland Next Day Delivery - £11.95; Europe (EU) - £12.95; Rest of World - £14.95 (up to 0.5Kg).  
Order online for reduced price Postage (from just £1)  
Payment: We accept all major credit/debit cards. Make PO's payable to Quasar Electronics.  
Please visit our online shop now for full details of over 500 electronic kits, projects, modules and publications. Discounts for bulk quantities.



**01279**

**Credit Card  
Sales**

**467799**

## PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

### Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £14.95  
18Vdc Power supply (PSU121) £24.95  
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95

### USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows XP software. See website for PICs supported. ZIF Socket and USB lead extra. 18Vdc.

Kit Order Code: 3149EKT - £49.95

Assembled Order Code: AS3149E - £59.95

Assembled with ZIF socket Order Code: AS3149EZIF - £74.95

### USB Flash/OTP PIC Programmer

USB PIC programmer for a wide range of Flash & OTP devices—see website for details. Free Windows Software. ZIF Socket and USB lead not included. Supply: 16-18Vdc.

Assembled Order Code: AS3150 - £49.95

Assembled with ZIF socket Order Code: AS3150ZIF - £64.95

### ATMEL 89xxxx Programmer

Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16Vdc.

Kit Order Code: 3123KT - £28.95

Assembled Order Code: AS3123 - £39.95

### Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual, Programming Hardware (with LED test section), Win 3.11—XP Programming Software (Program, Read, Verify & Erase), and 1 rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). PC parallel port. Kit Order Code: 3081KT - £16.95  
Assembled Order Code: AS3081 - £24.95

### PIC Programmer Board

Low cost PIC programmer board supporting a wide range of Microchip® PIC™ microcontrollers. Requires PC serial port. Windows interface supplied.

Kit Order Code: K8076KT - £39.95

### PIC Programmer & Experimenter Board

The PIC Programmer & Experimenter Board with test buttons and LED indicators to carry out educational experiments, such as the supplied programming examples. Includes a 16F627 Flash Microcontroller that can be reprogrammed up to 1000 times for experimenting at will. Software to compile and program your source code is included. Kit Order Code: K8048KT - £39.95

Assembled Order Code: VM111 - £59.95



### Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code PSU303 £9.95

### USB Experiment Interface Board

5 digital input channels and 8 digital output channels plus two analogue inputs and two analogue outputs with 8 bit resolution.

Kit Order Code: K8055KT - £39.95

Assembled Order Code: VM110 - £64.95



### Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two & Ten Channel versions also available. Kit Order Code: 3180KT - £54.95

Assembled Order Code: AS3180 - £64.95



### Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of tree software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor. Kit Order Code: 3145KT - £24.95

Assembled Order Code: AS3145 - £31.95

Additional DS1820 Sensors - £4.95 each



### Remote Control Via GSM Mobile Phone

Place next to a mobile phone (not included). Allows toggle or auto-timer control of 3A mains rated output relay from any location with GSM coverage.

Kit Order Code: MK160KT - £14.95



### 4-Ch DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc.

Kit Order Code: 3140KT - £79.95

Assembled Order Code: AS3140 - £94.95



### 8-Ch Serial Port Isolated I/O Relay Module

Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA.

Kit Order Code: 3108KT - £74.95

Assembled Order Code: AS3108 - £89.95



### Infrared RC 12-Channel Relay Board

Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm.

Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - £64.95

Assembled Order Code: AS3142 - £74.95



### Audio DTMF Decoder and Display

Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a

16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU303). Main PCB: 55x95mm.

Kit Order Code: 3153KT - £37.95

Assembled Order Code: AS3153 - £49.95



### 3x5Amp RGB LED Controller with RS232

3 independent high power channels. Preprogrammed or user-editable light sequences. Standalone option and 2-wire serial interface for microcontroller or PC communication with simple command set. Suitable for common anode RGB LED strips, LEDs and incandescent bulbs. 56 x 39 x 20mm. 12A total max. Supply: 12Vdc.

Kit Order Code: 3191KT - £27.95

Assembled Order Code: AS3191 - £37.95



Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

## Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

### 4-Channel Serial Port Temperature Monitor & Controller Relay Board

4 channel computer serial port temperature monitor and relay controller with four inputs for Dallas DS18S20 or DS18B20 digital thermometer sensors (£3.95 each). Four 5A rated relay channels provide output control. Relays are independent of sensor channels, allowing flexibility to setup the linkage in any way you choose. Commands for reading temperature and relay control sent via the RS232 interface using simple text strings. Control using a simple terminal / comms program (Windows HyperTerminal) or our free Windows application software. Kit Order Code: 3190KT - **£84.95**  
Assembled Order Code: AS3190 - **£99.95**



### 40 Second Message Recorder

Feature packed non-volatile 40 second multi-message sound recorder module using a high quality Winbond sound recorder IC. Stand-alone operation using just six onboard buttons or use onboard SPI interface. Record using built-in microphone or external line in. 8-24 Vdc operation. Just change one resistor for different recording duration/sound quality. sampling frequency 4-12 kHz. Kit Order Code: 3188KT - **£29.95**  
Assembled Order Code: AS3188 - **£37.95**  
120 second version also available



### Bipolar Stepper Motor Chopper Driver

Get better performance from your stepper motors with this dual full bridge motor driver based on SGS Thompson chips L297 & L298. Motor current for each phase set using on-board potentiometer. Rated to handle motor winding currents up to 2 Amps per phase. Operates on 9-36Vdc supply voltage. Provides all basic motor controls including full or half stepping of bipolar steppers and direction control. Allows multiple driver synchronisation. Perfect for desktop CNC applications. Kit Order Code: 3187KT - **£39.95**  
Assembled Order Code: AS3187 - **£49.95**



### Video Signal Cleaner

Digitally cleans the video signal and removes unwanted distortion in video signal. In addition it stabilises picture quality and luminance fluctuations. You will also benefit from improved picture quality on LCD monitors or projectors. Kit Order Code: K8036KT - **£32.95**  
Assembled Order Code: VM106 - **£49.95**



## Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

### DC Motor Speed Controller (100V/7.5A)



Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£19.95**  
Assembled Order Code: AS3067 - **£27.95**

### Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - **£16.95**  
Assembled Order Code: AS3179 - **£23.95**



### Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - **£24.95**  
Assembled Order Code: AS3158 - **£34.95**



### Bidirectional DC Motor Speed Controller

Control the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166v2KT - **£23.95**  
Assembled Order Code: AS3166v2 - **£33.95**



### AC Motor Speed Controller (600W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or 230V AC single phase induction motor rated up to 600 Watts. Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors. Kit Order Code: 1074KT - **£15.95**  
Assembled Order Code: AS1074 - **£23.95**



See [www.quasarelectronics.com](http://www.quasarelectronics.com) for lots more motor controllers



**Credit Card Sales**  
**01279 467 799**

## Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

### 500-in-1 Electronic Project Lab

Top of the range. Complete self-contained electronics course. Takes you from beginner to 'A' Level standard and beyond! Contains all the hardware and manuals to assemble 500 projects. You get 3 comprehensive course books (total 368 pages) - *Hardware Entry Course*, *Hardware Advanced Course* and a microprocessor based *Software Programming Course*. Each book has individual circuit explanations, schematic and connection diagrams. Suitable for age 12+. Order Code EPL500 - **£199.95**  
**Also available: 30-in-1 £19.95, 50-in-1 £29.95, 75-in-1 £39.95 £130-in-1 £49.95 & 300-in-1 £89.95 (see website for details)**



## Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

### Advanced Personal Scope 2 x 240MS/s

Features 2 input channels - high contrast LCD with white backlight - full auto set-up for volt/div and time/div - recorder roll mode, up to 170h per screen - trigger mode: run - normal - once - roll ... - adjustable trigger level and slope and much more. Order Code: APS230 - ~~£499.95~~ **£399.95**



### Personal Scope 10MS/s

The Personal Scope is not a graphical multimeter but a complete portable oscilloscope at the size and the cost of a good multimeter. Its high sensitivity - down to 0.1mV/div - and extended scope functions make this unit ideal for hobby, service, automotive and development purposes. Because of its exceptional value for money, the Personal Scope is well suited for educational use. Order Code: HPS10 - ~~£189.95~~ **£159.95**  
**See website for more super deals!**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).



[www.quasarelectronics.com](http://www.quasarelectronics.com)

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads



CELEBRATING  
**30**  
YEARS  
OF SERVICE

# Everyday Practical Electronics FEATURED KITS

JULY 2011

Everyday Practical Electronics Magazine has been publishing a series of popular kits by the acclaimed Silicon Chip Magazine Australia. These projects are 'bullet proof' and already tested Down Under. All Jaycar kits are supplied with specified board components, quality fibreglass tinned PCBs and have clear English instructions. Watch this space for future featured kits.

## Automotive Kits

### Courtesy Interior Light Delay Kit

**KC-5392 £7.50 plus postage & packing**

Many modern cars feature a time delay on the interior light. It still allows you time to buckle up and get organised before the light dims and finally goes out. This kit provides that feature for cars which don't already provide it. It has a soft fade out after a set time has elapsed, and features a much simpler universal wiring than our previous models.

- Kit supplied with PCB with overlay, and all electronic components.
- Suitable for circuits switching ground or +12V or 24VDC
- PCB Dimensions: 78 x 46mm

Featured in EPE February 2007




### Programmable Ignition System

**KC-5442 £34.50 plus postage & packing**

This advanced and versatile ignition system is suited for both two and four stroke engines. Used to modify the factory ignition timing or as the basis for a stand-alone ignition system with variable ignition timing, electronic coil control and anti-knock sensing (available separately).

- Timing retard & advance over a wide range
- Suitable for single coil systems
- Dwell adjustment
- Single or dual mapping ranges
- Max & min RPM adjustment
- Kit includes PCB with overlay, programmed micro, all electronic components and die cast box

Featured in EPE November 2009

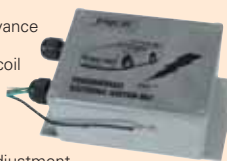

## Capacitor Discharge Ignition Kit for Motor Bikes

**KC-5466 £8.00 plus postage & packing**

Many modern motor bikes use a Capacitor Discharge Ignition (CDI) to improve performance and enhance reliability. However, if the CDI ignition module fails, a replacement can be very expensive. This kit will replace many failed factory units and is suitable for engines that provide a positive capacitor voltage and have a separate trigger coil. This CDI module uses cheap and readily available parts and is worth a try before shelling out lots of hard-earned cash for a genuine replacement module. Supplied with solder masked PCB and overlay, case and components. Some mounting hardware required.

- PCB: 45 x 64mm
- Featured in EPE June/July 2010



## Delta Throttle Timer Kit

**KC-5373 £9.25 plus postage & packing**

This brilliant design will trigger a relay when the accelerator is pressed or lifted quickly. Used for automatic transmission switching of economy to power modes or trigger electronic blow-off valves on quick throttle lifts etc. It is completely adjustable, and uses the output of a standard throttle position sensor.

- Kit supplied with PCB, and all electronic components
- Featured in EPE November 2006



## Tempmaster Fridge Controller Mk II

**KC-5476 £12.00 plus postage & packing**

Turn an old chest freezer into an energy-efficient fridge or beer keg fridge. Or convert a standard fridge into a wine cooler. These are just two of the jobs this low-cost and easy-to-build electronic thermostat kit can do without the need to modify internal wiring! Used also to control 12V fridges or freezers, as well as heaters in hatcheries and fish tanks. Short-form kit contains PCB, sensor and all specified components. You'll need to add your own 240V GPO, switched IEC socket and case.

- PCB Dimensions: 68 x 67mm
- Featured in EPE February 2011



## Water Tanks Kits

### PIC Based Water Tank Level Meter Kit

**KC-5460 £39.50 plus postage & packing**

This PIC-based unit uses a pressure sensor to monitor water level and will display tank level via an RGB LED at the press of a button. The kit can be expanded to include and optional wireless remote display panel that can monitor up to ten separate tanks (KC-5461) or you can add a wireless remote controlled mains power switch (KC-5462) to control remote water pumps. Kit includes electronic components, case, screen printed PCB and pressure sensor.

Featured in EPE May 2010

Also available: KC-5461 Remote display kit £31.00



### Remote Control Mains Switch

**KC-5462 £36.25 plus postage & packing**

Commercial remote control mains switches are available but these are generally limited to a range of less than 20m. This UHF system will operate up to 200m and is perfect for remote power control systems etc. The switch can be activated using the included hand held controller. Kit supplied with case, screen printed PCB, RF modules and all electronic components. Note: Requires UK mains socket or adaptor.

Featured in EPE May 2010



## Improved Low Voltage Adaptor

**KC-5463 £6.75 plus postage & packing**

This versatile regulator will let you run a variety of devices such as CD, DVD or MP3 players, digital cameras or even powered speakers in your car or from the power supply inside your PC. This unit can supply either 3V, 5V, 6V, 9V, 12V or 15V from a higher input voltage at up to four amps (with a suitable heatsink). Kit includes screen printed PCB and all specified components.

Note: To ensure trouble free 4 amp output, a heatsink with a thermal resistance of 1.4 degrees C per watt, and an input voltage 3VDC above the output voltage is required.

- PCB Dimensions: 108 x 37mm
- Featured in EPE November 2007



## 3V to 9V DC to DC Converter Kit

**KC-5391 £6.00 plus postage & packing**

This great little converter allows you to use regular Ni-Cd or Ni-MH 1.2V cells, or Alkaline 1.5V cells for 9V applications. Using low cost, high capacity rechargeable cells, the kit will pay for itself in no-time! You can use any 1.2-1.5V cells you desire. Imagine the extra capacity you would have using two 9000mAh D cells in replacement of a low capacity 9V cell.

- PCB Dimensions: 59 x 29mm
- Featured in EPE June 2007



## Low Cost Programmable Interval Timer

**KC-5464 £12.75 plus postage & packing**

Here's a new and completely updated version of the very popular low cost 12VDC electronic timer. It is link programmed for either a single ON, or continuous ON/OFF cycling for up to 48 on/off time periods. Selectable periods are from 1 to 80 seconds, minutes, or hours and it can be restarted at any time. Kit includes PCB and all specified electronic components.

- 12VDC required
  - PCB Dimensions: 102 x 42mm
- Featured in EPE August 2010



## 433MHz Remote Switch Kit

**KC-5473 £16.50 plus postage & packing**

Suitable for remote control of practically anything up to a range of 200m. The receiver has momentary or toggle output and the momentary period can be adjusted. Up to five receivers can be used in the same vicinity. Short-form kit contains two PCBs and all specified components.

- Extra transmitter kit: KC-5474 £8.50
  - PCB Dimensions: Tx: 85 x 63mm Rx: 79 x 48mm
- Featured in EPE August/September 2008



**Jaycar**  
Electronics

Freecall order: 0800 032 7241



# Sight & Sound Kits for Electronic Enthusiasts

## KIT OF THE MONTH

### Hearing Loop Receiver Kit KC-5497 £12.75 plus postage & packing

A hearing loop is an inductive assisted listening system for the hearing impaired. They're typically installed in venues such as churches and conference rooms to enable listeners to receive in-ear communication via a wireless induction loop. You can now install this technology on your own TV, home theatre or hi-fi system. This will enable someone who's hard of hearing to hear at their own volume level without having to turn the volume up to a level too high for everyone else. The receiver will drive a pair of headphones or earbuds from the signal picked up from the hearing loop. The whole unit is completely self-contained and can be carried around in a pocket or you can add your own belt clip, so the user isn't constrained by a set of headphone leads. The kit is complete with case, label, PCB and components.



- Current consumption: 10mA
  - Frequency response: 100Hz - 5kHz
  - S/N ratio: 67dB
  - Battery voltage indication: Down to 7V
  - PCB: 65 x 86mm
- Note: Transmitter not included


**Improve Your Hearing Without The EXPENSE!**

## 45 Second Voice Recorder Module

### KC-5454 £16.00 plus postage & packing

Will record two, four or eight different messages for random-access playback or a single message for "tape mode" playback. It also provides cleaner and glitch-free line-level audio output suitable for feeding an amplifier or PA system. It can be powered from any source of 9 - 12VDC. Supplied with silk screened and solder masked PCB and all electronic components.

- PCB: 58 x 120mm

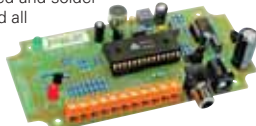

## Audio Kits

### Studio 350 - High Power Amplifier KC-5372 £63.50 plus postage & packing

The studio 350 power amplifier will deliver a whopping 350WRMS into 4 ohms or 200WRMS into 8 ohms. It offers real grunt using a high power MJ21193/4 transistor and is super quiet with a very low signal to noise ratio and harmonic distortion. This kit is supplied in short form with PCB and electronic components. Kit requires heatsink and (+/-) 70V power supply as described in instructions. See website for more specifications.

- PCB: 136 x 241mm




## Clifford The Cricket
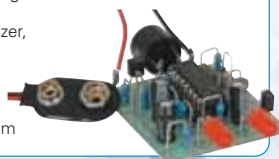
### KC-5178 £6.25 plus postage & packing

Clifford hides in the dark and chirps annoyingly until a light is turned on - just like a real cricket. Clifford is created on a small PCB, measuring just 40 x 35mm and has cute little LED insect eyes that flash as it sings. Just like a real cricket, it waits a few seconds after darkness until it begins chirping, and stops instantly when a light comes back on.

- PCB, piezo buzzer, LDR plus all electronic components supplied
- PCB: 41 x 36mm



## SCI-FI Kits

### Jacob's Ladder High Voltage Display Kit MK2

#### KC-5445 £15.75 plus postage & packing

With this kit and the purchase of a 12V ignition coil (available from auto stores and parts recyclers), create an awesome rising ladder of noisy sparks that emits the distinct smell of ozone. This improved circuit is suited to modern high power ignition coils and will deliver a spectacular visual display.

Kit includes PCB, pre-cut wire/ladder and all electronic components.

- 12V automotive ignition coil and case not included
- 12V car battery, 7Ah SLA or >5Amp DC power supply required and not included
- PCB: 170 x 76mm

**Warning:** The Jacobs Ladder Kit uses potentially dangerous voltage.



## Bridge Mode Adaptor

### KC-5469 £10.25 plus postage & packing

Enables you to run a stereo amplifier in 'Bridged Mode' to effectively double the power available to drive a single speaker. There are no modifications required on the amplifier and the signal processing is done by this clever kit. Supplied with silk screened PCB and components. Requires balanced (+/-) 15-60V power supply.

- PCB: 103 x 85mm



### Balanced to Unbalanced Audio Converter KC-5468 £12.00 plus postage & packing

This kit will adapt an unbalanced input to balanced output and vice versa and allows domestic equipment to be integrated into a professional installation while maintaining the inherent high immunity to noise pick-up on long cable runs provided by balanced lines. Kit supplied with solder masked PCB and all specified components.

- PCB: 85 x 103mm



## "Minivox" Voice Operated Relay

### KC-5172 £6.00 plus postage & packing

Voice operated relays are used for 'hands free' radio communications and some PA applications etc. Instead of pushing a button, this device is activated by the sound of a voice. This tiny kit fits in the tightest spaces and has almost no turn-on delay. 12VDC @ 35mA required. Kit is supplied with PCB electret mic, and all specified components.

- PCB: 47 x 44mm



**Communicate Hands Free!**

## Theremin Synthesiser Kit MkII

### KC-5475 £27.25 plus postage & packing

The ever-popular Theremin is better than ever! From piercing shrieks to menacing growls, create your own eerie science fiction sound effects by simply moving your hand near the antenna. It's now easier to build with PCB-mounted switches and pots to reduce wiring to just the hand plate, speaker and antenna and has the addition of a skew control to vary the audio tone from distorted to clean.

- Complete kit contains PCB with overlay, pre-machined case and all specified components
- PCB: 85 x 145mm




**Don't just sit there BUILD SOMETHING!**

## Starship Enterprise Door Sound Emulator
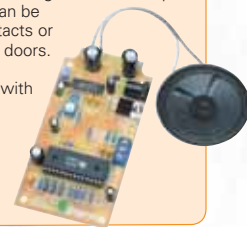
### KC-5423 £14.50 plus postage & packing

This easy to build kit emulates the unique sound of a cabin door opening or closing on the Starship Enterprise. The sound can be triggered by switch contacts or even fitted to automatic doors.

- Kit supplied with PCB with overlay, speaker, case and all specified components
- 9-12VDC regulated
- PCB: 84 x 148mm



## Flickering Flame Lighting

### KC-5234 £6.25 plus postage & packing

This lighting effect uses a single 20 watt halogen lamp (the same as those used for domestic down lights) to mimic its namesake. Mounted on a compact PCB, it operates from 12VDC and uses just a handful of readily available components. Use it for stage performances or for unique lighting effects at home.

- Kit includes 20W halogen lamp
- PCB plus electronic components
- Includes ceramic base for halogen lamp
- PCB: 38 x 58mm



## Post & Packing Charges

Order Value	Cost	Note: Products are despatched from Australia, so local customs duty & taxes may apply.
£10 - £49.99	£5	
£50 - £99.99	£10	
£100 - £199.99	£20	
£200 - £499.99	£30	
£500+	£40	
Max weight 12lb (5kg)		
Heavier parcels POA		
Minimum order £10		

**All pricing in Pounds Sterling**  
**Minimum order £10**  
**Prices valid until 31/7/2011**

## HOW TO ORDER

**WEB:** [www.jaycarelectronics.co.uk](http://www.jaycarelectronics.co.uk)  
**PHONE:** 0800 032 7241\*  
**FAX:** +61 2 8832 3118\*  
**EMAIL:** [techstore@jaycarelectronics.co.uk](mailto:techstore@jaycarelectronics.co.uk)  
**POST:** P.O. Box 107, Rydalmere NSW 2116 Australia  
 \*Australian Eastern Standard Time  
 (Monday - Friday 09.00 to 17.30 GMT + 10 hours)  
 Expect 10-14 days for air parcel delivery

Order online: [www.jaycarelectronics.co.uk](http://www.jaycarelectronics.co.uk)

**Jaycar**  
Electronics

**velleman®****0845 251 4363****Kit Catalogue Available****cebek®****UK's No 1 source for VELLEMAN® Kits**

**Self Assembly Kits & Ready made Modules - See our web site for details on the whole range, Data sheets, Software and more.**

**www.esr.co.uk**

**Now Available - Cebek Modules**  
All modules assembled & tested.

**Digital Echo Chamber Kit**

A compact sound effects kit, with built-in mic or line in, line out or speaker (500mW). 4 Adjustment controls  
Power: 9Vdc 150mA

**MK182 Velleman kit £11.43****3rd Brake Light Flasher Kit**

Works with any incandescent or LED rear centre brake light. Flashes at 7Hz for 5 or 10 times, adjustable re-triggering.  
Power: 12Vdc max load 4A

**MK178 Velleman kit £6.30****Digital Clock Mini Kit**

Red 7 Segment display in attractive enclosure, automatic time base selection, battery back-up, 12 or 24Hr modes.  
Power: 9Vac or dc

**MK151 Velleman kit £15.09****Proximity Card Reader Kit**

A simple security kit with many applications. RFID technology activates a relay, either on/off or timed. Supplied with 2 cards, can be used with up to 25 cards.  
Power: 9Vac or dc

**MK179 Velleman kit £14.25****Running Microbug Kit**

Powered by two subminiature motors, this robot will run towards any light source. Novel shape PCB with LED eyes.  
Power: 2 x AAA Batteries

**MK127 Velleman kit £9.02****200W Power Amplifier**

A high quality audio power amp, 200w music power @ 4Ω 3-200kHz Available as a kit without heatsink or module including heatsink.  
**K8060 Velleman kit £12.85**  
**Heatsink for kit VM100 Module £9.95**  
**VM100 Module £38.54**

**MP3 Player Kit**

Plays MP3 files from an SD card, supports ID3 tag which can be displayed on optional LCD. Line & headphone output. Remote control add-on. Power: 12Vdc 100mA

**K8095 Velleman kit £39.99****DC to Pulse width Modulator**

A handy kit to accurately control DC motors etc. Overload & short circuit protection. Input voltage 2.5-35Vdc, Max output 6.5A.  
Power: 8-35Vdc

**K8004 Velleman kit £9.95****Audio Analyser Kit**

A small spectrum analyser with LCD. Suitable for use on 2, 4 or 8Ω systems. 300mW to 1200W(20) 20-20kHz Panel mounting, back-lit display. Power: 12Vdc 75mA

**K8098 Velleman kit £31.65****USB DMX Interface**

512 DMX Channels controlled by PC via USB. Software & case included. Available as a kit or ready assembled module.

**K8062 Velleman kit £47.90**  
**VM116 Module £67.15****USB Interface Board**

Featuring 5 in, 8 digital outputs, 2 in & 2 analogue outputs. Supplied with software. Available as a kit or ready assembled module.

**K8055 Velleman kit £24.80**  
**VM110 Module £34.90****8 Channel USB Relay Board**

PC Controlled 16A relays with toggle, momentary or timed action. Test buttons included, available in a kit or assembled.

**K8090 Velleman kit £39.95**  
**VM8090 Module £58.40****Multifunction Up/Down Counter**

An up or down counter via on-board button or ext input. Time display feature. Alarm count output. 0-9999 display.  
Power: 9-12Vdc 150mA

**K8035 Velleman kit £17.85****Nixie Clock Kit**

Gas filled nixie tubes with their distinctive orange glow. HH:MM display, automatic power sync 50/60Hz  
Power: 9-12Vdc 300mA

**K8099 Velleman kit £64.96****Mini USB Interface Board**

New from Velleman this little interface module with 15 inputs/outputs inc digital & analogue in, PWM outputs. USB Powered 50mA. Software supplied

**VM167 Module £26.80****Thermostat Mini Kit**

General purpose low cost thermostat kit. +5 to +30°C Easily modified temperature range/min/max/hysteresis 3A Relay.  
Power: 12Vdc 100mA

**MK138 Velleman Kit £4.55****Velleman Function Generator**

PC Based USB controlled function generator. 0.01Hz to 2Mhz Pre-defined & waveform editor. Software supplied. See web site for full feature list.

**PCGU1000 Velleman £118.38****Velleman PC Scope**

PC Based USB controlled 2 channel 60MHz oscilloscope with spectrum analyser & transient recorder. 2 Scope probes & software included. See web site for full feature list.

**PCSU1000 Velleman £249.00****Velleman PC Scope/Generator**

PC Based USB controlled 2 channel oscilloscope AND Function generator. Software included. See web site for full feature list.

**PCSGU250 Velleman £113.67****RF Remote Control Transmitter**

Single channel RF keyfob transmitter with over 13,122 combinations. Certified radio frequency 433.92MHz. Power: 12Vdc 2mA (inc) For use with TL-1,2,3,4 receivers.

**TL-5 Cebek Module £14.64****RF Remote Control Receiver**

Single channel RF receiver with relay output. Auto or manual code setup. Momentary output, 3A relay  
Power: 12Vdc 60mA For use with TL-5 or TL-6 transmitters.

**TL-1 Cebek Module £28.25****Keypad Access Control**

An electronic lock with up to ten 4 digit codes. Momentary or timed (1-60sec/1-60min) output. Relay 5A  
Power: 12Vdc 100mA Keypad included.

**DA-03 Cebek Module £54.26****AC Motor Controller**

A 230Vac 375W motor speed control unit giving 33 to 98% of max power.  
Power: 230Vac

**R-8 Cebek Module £12.14****Digital Record/Player**

Non volatile flash memory. Single 20 sec recording via integral mic, 2W output to 8Ω speaker.  
Power: 5Vdc 100mA

**C-9701 Cebek Module £7.89****2 Digital Counter**

Standard counter, 0 to 99 from input pulses or external signal. With reset input, 13.5mm Displays.  
Power: 12Vdc 90mA.

**CD-9 Cebek Module £12.99****1.8W Mono Amplifier**

Compact mono 1.8W RMS 4Ω power stage, short circuit & reverse polarity protection. 30-18kHz, Power: 4-14Vdc 150mA

**E-1 Cebek Module £5.87****20W 2 Channel Amplifier**

Mono amplifier with 2 channels (Low & High frequency), 20W RMS 4Ω per channel, adjustable high level. 22-22kHz, short circuit & reverse polarity protection. Power: 8-18Vdc 2A

**E-14 Cebek Module £22.11****5W Stereo Amplifier**

Stereo power stage with 5W RMS 4Ω. 30-18kHz, short circuit & reverse polarity protection.  
Power: 6-15Vdc 500mA

**ES-2 Cebek Module £21.54****12Vdc Power Supply**

Single rail regulated power supply complete with transformer. 130mA max, low ripple, 12Vdc with adjustment.

**FE-103 Cebek Module £13.16****1-180 Second Timer**

Universal timer with relay output. Time start upon power up or push button. LED indication. 5A Relay  
Power: 12Vdc 60mA

**I-1 Cebek Module £12.92****Cyclic Timer**


Universal timer with relay output. Time start upon power up or push button. On & Off times 0.3-60 Seconds, LED indication. 5A Relay  
Power: 12Vdc 80mA

**I-10 Cebek Module £14.12****Light Detector**

Adjustable light sensor operating a relay. Remote sensor & terminals for remote adjustment pot. 5A Relay  
Power: 12Vdc 60mA

**I-4 Cebek Module £13.98****Liquid Level Detector**

A liquid level operated relay. Remote sensor operates relay when in contact with a liquid. 5A Relay  
Power: 12Vdc 60mA

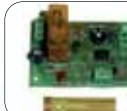**I-6 Cebek Module £13.08****Thermostat**

A temperature controlled relay. Adjustable between -10 to 60°C Sensor on remote PCB. Connector for external adjustment pot. 5A Relay  
Power: 12Vdc 60mA

**I-8 Cebek Module £12.80****Start / Stop Relay**

Simple push button control of a relay. Either 1 or 2 button operation 5A Relay  
Power: 12Vdc 60mA

**I-9 Cebek Module £12.83****Components****Hardware****Soldering****Switches****Test Equipment****Transformers****Motors****PCB Equipment****Connectors****Power Supplies****Enclosures****Relays**

**Tel: 0191 2514363**  
**Fax: 0191 2522296**  
**sales@esr.co.uk**

**Station Road**  
**Cullercoats**  
**Tyne & Wear**  
**NE30 4PQ**



Prices Exclude Vat @20%.  
UK Carriage £2.50 (less than 1kg)  
£6.50 greater than 1kg or >£30  
Cheques / Postal orders payable to  
ESR Electronic Components Ltd.  
PLEASE ADD CARRIAGE & VAT TO ALL ORDERS



**Editorial Offices:**

EVERYDAY PRACTICAL ELECTRONICS  
 EDITORIAL Wimborne Publishing Ltd., 113 Lynwood  
 Drive, Merley, Wimborne, Dorset, BH21 1UU  
**Phone:** (01202) 880299. **Fax:** (01202) 843233.  
**Email:** enquiries@wimborne.co.uk  
**Website:** www.epemag.com

See notes on **Readers' Technical Enquiries** below  
 – we regret technical enquiries cannot be answered  
 over the telephone.

**Advertisement Offices:**

Everyday Practical Electronics Advertisements  
 113 Lynwood Drive, Merley, Wimborne, Dorset,  
 BH21 1UU  
**Phone:** 01202 880299 **Fax:** 01202 843233  
**Email:** stewart.kearn@wimborne.co.uk

**Editor:**

MATT PULZER

**Consulting Editor:**

DAVID BARRINGTON

**Subscriptions:**

MARILYN GOLDBERG

**General Manager:**

FAY KEARN

**Graphic Design:**

RYAN HAWKINS

**Editorial/Admin:**

(01202) 880299

**Advertising and****Business Manager:**

STEWART KEARN

(01202) 880299

**On-line Editor:**

ALAN WINSTANLEY

**EPE Online**(Internet version) **Editors:**

CLIVE (Max) MAXFIELD

and ALVIN BROWN

**Publisher:**

MIKE KENWARD

**READERS' TECHNICAL ENQUIRIES****Email:** techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years' old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. We are not able to answer technical queries on the phone.

**PROJECTS AND CIRCUITS**

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in EPE employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains-powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

**COMPONENT SUPPLIES**

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

**ADVERTISEMENTS**

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

**TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT**

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment, as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.

# EPE EVERYDAY PRACTICAL ELECTRONICS

**Computing for the 'common man'**


An electronics celebrity came to town last month (town being Brighton for me) – a certain Steve from Apple attended a conference by the seaside. There was a time when the name 'Steve', in relation to Apple, meant two people. Of course one of them was (and still is) Steve Jobs, who has become one of the most famous people in the world of electronics and information technology. Apple, the company he co-founded, is the richest technology corporation in the world; the Apple brand is the world's most valuable; and Jobs was voted CEO of the decade by Fortune magazine in 2009. One of the ironies of this achievement is that Steve Jobs is not an engineer. He would be the first to admit that he hasn't 'engineered' any of their products, but what he does have is a crystal clear vision of what he wants to produce and how to achieve it.

The very first Apple product Jobs launched was the 'Apple 1' computer in 1976. However, it was designed and built by the other Steve, Steve Wozniak. Between them, the two Steves went on to lay the foundations of the modern Apple company. Although Wozniak left Apple in 1987, without his input and foresight about what a PC should be, it is doubtful that Apple could have got off the ground and computers would look very different today. I doubt if we'd still be stuck in the 'command line prompt' world of MS-DOS, but a big part of Microsoft's initial impetus for moving to Windows came from the success of Apple's early graphical user interface.

Although never one for the limelight, engineer Steve is still an important figure in the history of PCs, so it is worth following his views on what the future holds for computing. One thing he has always been passionate about is spreading the use of computers for everyone. The earliest PCs were little more than kits of parts and a PCB. If you were lucky you got an assembled motherboard, but no case, no monitor and certainly no hard drive (programs were stored and loaded using compact cassette tapes). Things changed quickly and complete systems – at a price – were soon available, but you needed a fair amount of knowledge and perseverance to become PC literate.

Contrast that with today, where modern systems easily play music and films, search the Internet, and a whole host of other activities. What is surprising though, is how similar many modern computers look to models 25 or more years old – a box, attached to a display, keyboard and mouse. Now, however, there is a completely new format in the shape of tablet computers, the most famous being the iPad from Apple. And what does pioneer Wozniak think of them? A quote from him caught my eye recently; speaking to engineers at a conference in California, he said: 'The tablet is not necessarily for the people in this room. It's for the normal people in the world.' Which is exactly the product both Steves set out to make 35 years ago.

*Mail*

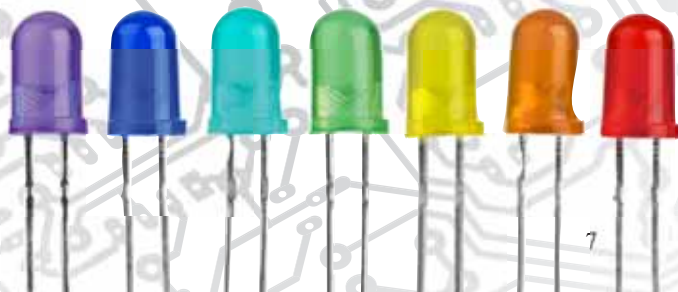



# NEWS

**A roundup of the latest Everyday News from the world of electronics**



## 3D video on demand by Barry Fox

The annual European press conference held to promote the *IFA Electronics Show* was again enlivened by the now traditional slanging match between the organisers of the September IFA show in Berlin and the January *CES* event in Las Vegas. But, also by tradition, the two shows never refer to each other by name.

'If there is one single piece of information I want you to take away from this event, it is that IFA is the number one show for the trade and media,' Dr Christian Göke, CEO Messe Berlin told 300 journalists flown in from around the world to sunny Alicante, Spain.

'Anyone who has already got that message is free to leave the room and go to the pool. But if you would like to stay, I will give good reasons why IFA is global number one, and the *only* place in the world for so many international retailers and media.'

'We are number one in the world with stable and positive growth. This sets us apart from all other shows in the world.'

Several manufacturers were given 20-minute slots to promote their electronic wares. Michael Zoller, Samsung's European marketing director was clearly under orders from his Korean bosses to try and cool the bitter dispute over active-shutter versus passive-polarising 3DTV – while promoting Samsung's continuing commitment to active shutter in the face of rival LG's high profile criticism of active shuttering.

This came as Toshiba followed Philips and quietly slid passive TV sets into its new TV range, to sell alongside the company's existing active shutter sets.

This summer, Samsung will launch a free 3D video on demand service, delivered direct by broadband to Samsung active shutter Internet TV sets. 3D clips, trailers and ten Imax Theatre 3D movies – each of 45 minutes length and as currently available on Blu-ray discs – will stream for free.

To boost 3D sales, Samsung will start selling packs of two pairs of active

shutter glasses, for 79 euros (approx £67). These glasses will use an RF connection, working on the 2.4GHz Bluetooth frequency and using pairing technology similar to, but not to quite the same standard, as Bluetooth. The glasses need only be push-button paired once with the TV, and then remain paired.

Using RF avoids the problem of interference, which has plagued infrared active shutter connection, particularly in stores where retailers want to demonstrate several 3DTV sets and different brands in close proximity. The IR signals for one set can stop other sets' glasses working.

Zoller confirmed that all 2011 Samsung 3DTVs will use RF Bluetooth-style connection, and there is no compatibility between 2011 glasses and 2010 infrared sets.

'We are now 100% Bluetooth. Infrared is finished', he said.

However, Samsung pledges to keep selling IR glasses for owners of existing 3D sets.

## Arduino-compatible 32-bit microcontroller development platform

Microchip has launched the first 32-bit-microcontroller-based, open-source development platform that is compatible with Arduino hardware and software. Designed and manufactured by Digilent, a Microchip authorised design partner, the chipKIT platform is a 32-bit Arduino solution to enable hobbyists and academics to easily, and inexpensively, integrate electronics into their projects, even if they do not have an electronic-engineering background.

The boards' starting price is \$26.95 each. The platform consists of two PIC32-based development boards and open-source software that is fully compatible with the Arduino

programming language and development environment. The chipKIT hardware is compatible with existing Arduino shields and applications, and can be developed using the Arduino IDE and existing resources, such as code examples, libraries, references and tutorials. The easy-to-use kit supports project development in many disciplines, such as mechanical engineering, computer science and even art.

The PIC32-based chipKIT boards enable 80MHz performance, and provide up to 512KB Flash, with up to 128KB RAM. They feature connectivity peripherals, including Ethernet, CAN, and USB (Full-Speed Host, Device and OTG), plus peripherals such as



multiple timers, a 16-channel 1 MSPS Analogue-to-Digital Converter (ADC), two comparators, and multiple I2C, SPI, and UART interfaces. The chipKIT integrates Microchip's PIC32 microcontroller which is the highest performance 32-bit microcontroller in its class.

A ChipKIT video demo is available at: [www.microchip.com/get/D268](http://www.microchip.com/get/D268)

## WORLD RECORD

Researchers at the Karlsruhe Institute of Technology (KIT) have succeeded in encoding data at a rate of 26 terabits per second (26,000 billion bits per second) on a single laser beam, transmitting them over a distance of 50km, and decoding them successfully. This is the largest data volume ever transported on a laser beam. The process developed by KIT allows the contents of 700 DVDs to be transmitted in just one second.

With this experiment, the KIT scientists in the team of Professor Jürg Leuthold beat their own record in high-speed data transmission of 2010, when they exceeded the 10 TB/s barrier. 'Our result shows that physical limits have not yet been exceeded, even at

very high data rates', Leuthold says.

'A few years ago, data rates of 26 terabits per second were deemed Utopian, even for systems with many lasers... and there would not have been many applications. With 26 terabits per second, it would have been possible to transmit up to 400 million telephone calls at the same time. Nobody needed this at that time. Today, the situation is different. Video transmissions predominate on the Internet and require extremely high bit rates.


Companies and scientists from all over Europe were involved in the experimental implementation of ultrarapid data transmission at KIT. Among them were members of the University of Southampton.

## Revolutionary 3D Transistor

Intel has announced a significant breakthrough in the evolution of the transistor, the building block of modern electronics. For the first time since the invention of silicon transistors over 50 years ago, transistors using a three-dimensional structure will be put into high-volume manufacturing. Intel will introduce a revolutionary 3D transistor design called 'Tri-Gate', first disclosed by Intel in 2002, into high-volume manufacturing at the 22nm level.

The three-dimensional Tri-Gate transistors represent a fundamental departure from the two-dimensional planar transistor structure that has powered not only all computers, mobile phones and consumer electronics to date, but also the electronic controls within cars, spacecraft, household appliances, medical devices and thousands of other everyday devices for decades.

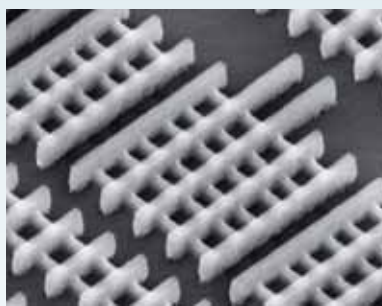Tri-Gate transistors enable chips to operate at lower voltage with lower leakage, providing an unprecedented combination of improved performance and energy efficiency compared to



Intel's 22nm 3D Tri-Gate Transistor

previous state-of-the-art transistors. The capabilities give chip designers the flexibility to choose transistors targeted for low power or high performance, depending on the application.

These new transistors provide up to 37% performance increase at low voltage versus Intel's 32nm planar transistors. This gain means that they are ideal for use in small handheld devices, which operate using less energy to 'switch' – less than half the power when at the same performance level as 2D planar transistors on 32nm chips.

## New evaluation kit for Sensirion's differential pressure sensors



EK-P3 is an evaluation kit from Swiss CMOS-based sensor manufacturer Sensirion. It is a straightforward and cost-effective option for testing their digital differential pressure sensors.

The set consists of a USB stick that is connected to the SDP610 sensor by an adapter cable. Software available online enables a PC to display the data or save it to a spreadsheet. The sensors have a digital (I2C) output signal and provide excellent accuracy and sensitivity. For more information, see: [www.sensirion.com/ekp3](http://www.sensirion.com/ekp3)

## Competition time!

A couple of competitions that will be of interest to EPE readers who have a creative streak...

### Picture Bletchley Park

Bletchley Park, Milton Keynes, once a top-secret institution where all photography was banned, is now welcoming photographers with open arms to take part in its inaugural 'Picture Bletchley Park' photographic competition.

The prestigious board of judges includes Kate Day, communities editor for [telegraph.co.uk](http://telegraph.co.uk), who is also well known for her blogs about photography and Damien Demolder, editor of the magazine, *Amateur Photographer*.

The competition is open to everyone, regardless of experience. Participants may submit photographs of any aspect of Bletchley Park, from the buildings and the army of staff and volunteers who work there, to its priceless historic collections and lovely gardens.

The winners will feature in Bletchley Park's official 2012 calendar, with the photograph by the overall winner featuring on the front cover. The 13 winning entries, along with 25 runners up, will also be displayed at Bletchley Park during the 'Picture This' event on 2 October, where the winners will each be presented with a framed copy of their entry.

To enter, or for more information and rules, go to: [www.bparkcomp.org.uk](http://www.bparkcomp.org.uk).

### Pylon design competition

Love them or hate them, the great British pylon is an unmistakable part of the landscape. The current 'iconic' design is essentially 80 years old and has been a constant since the birth of the national grid.




Make your mark by redesigning the pylon!

If you fancy a change from designing amplifiers or PIC projects then why not enter the 'Pylon design competition' run by RIBA? ([www.ribapylondesign.com](http://www.ribapylondesign.com)) It's an opportunity to get involved with enormous currents and voltages by designing a new generation of pylons. Potential pylon aficionados can gain inspiration from Flash Bristow's pylon-themed website at: [www.gorge.org/pylons](http://www.gorge.org/pylons), and if you are really keen then why not join the Pylon Appreciation Society at: [www.pylons.org](http://www.pylons.org).
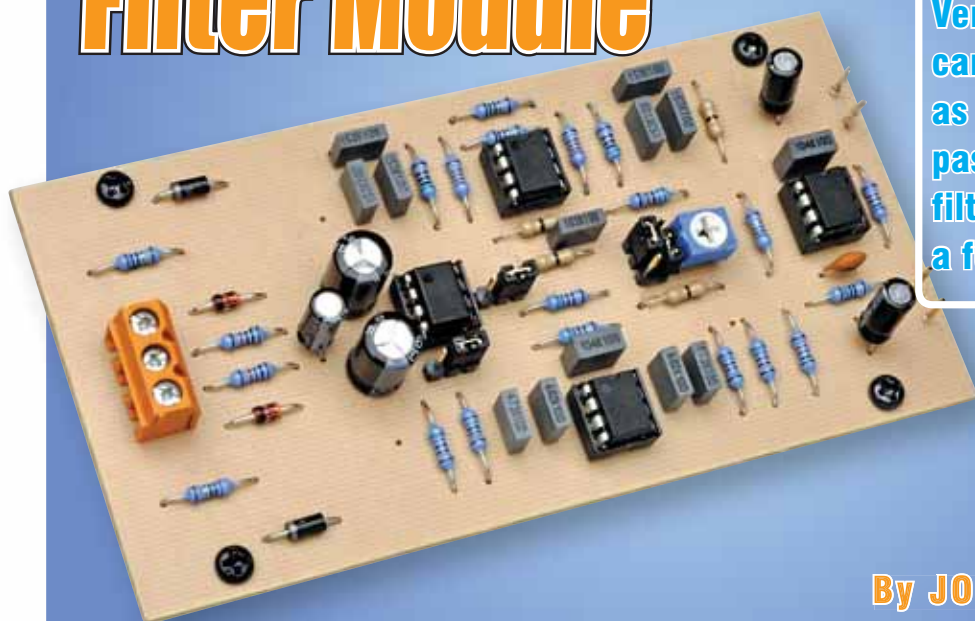
# Multi-Function Active Filter Module

Versatile design – can be configured as a low-pass, high-pass or bandpass filter just by moving a few jumper links



By JOHN CLARKE

This versatile Active Filter is ideal for use as an active crossover in loudspeaker systems, but has lots of other uses as well. It can be configured as a low-pass filter (for driving sub-woofer amplifiers), as a high-pass filter or as a bandpass filter, simply by moving a few on-board jumper links.

**A**CTIVE filters are used in many analogue circuits to tailor the frequency response. For example, an active filter could be used to prevent signals below 20Hz from passing through to the next stage (eg, to an amplifier). In this case, the filter allows the higher audio frequencies to pass through, but blocks the sub-audio signals (including DC).

This type of filter is called a 'high-pass' (HP) filter. If an HP filter is incorporated into an audio amplifier, it will prevent the woofer in a loudspeaker system from being driven at very low frequencies. In fact, it could be used as a turntable rumble filter to follow a magnetic cartridge preamplifier.

Preventing a loudspeaker from being driven at very low frequencies is important because such frequencies would cause audible distortion in the sound due to excessive cone movement. In addition, excessive cone movement at or below the loudspeaker's resonance frequency could damage the loudspeaker.

Similarly, an active filter could also be used to limit signals above 20kHz. This will prevent supersonic signals from driving the loudspeaker and protect the tweeter(s) from damage. This type of filter is called a low-pass (LP) filter; it allows frequencies below a certain frequency to pass through, but blocks higher frequencies.

## Bandpass filter

Cascading a high-pass filter and a low-pass filter produces a bandpass filter. So, if a 20Hz high-pass filter and a 20kHz low-pass filter are cascaded, we end up with a bandpass ranging from 20Hz to 20kHz. This means that the signal is attenuated both below 20Hz and above 20kHz, while those frequencies between 20Hz and 20kHz are basically left unattenuated.

However, some attenuation (or reduction in level) does occur as the signal frequency approaches 20Hz and 20kHz, ie, near the so-called corner or 'roll-off' frequencies.

Additional filters can also be used to split the 20Hz to 20kHz audio



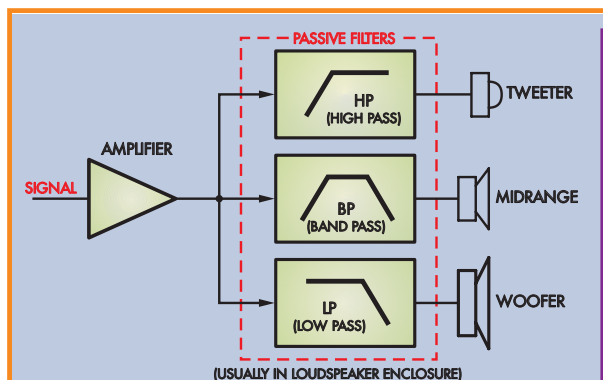


Fig.1: a single power amplifier is usually used to drive a passive crossover network in a loudspeaker box.

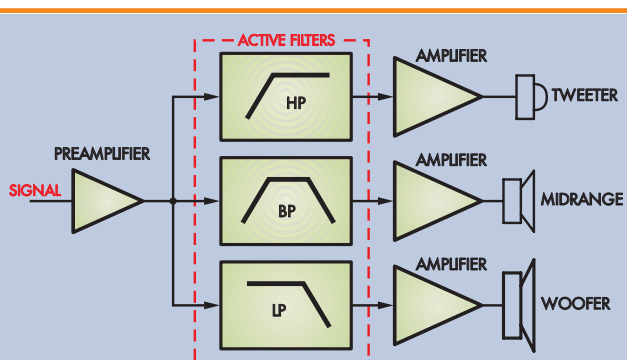


Fig.2: the arrangement for an active crossover filter system. The filters go before the power amplifiers and a separate amplifier is required for each loudspeaker driver.

frequency range into separate frequency ranges or bands. This might be done to produce a 2-way or 3-way active crossover for two or three drivers in a loudspeaker system.

In greater detail, many loudspeaker systems include woofer, midrange and tweeter drivers in the same box – see Fig.1. This is called a 3-way system, while a 2-way system includes just a woofer and a tweeter.

The separate drivers are used because no single driver can faithfully reproduce the whole audible range from 20Hz to 20kHz. So the audio band of frequencies is divided up and each driver is fed with its own ‘ideal’ range of frequencies. In a 3-way system, for example, the woofer could be provided with signals ranging from 20Hz to say 150Hz, while the midrange would handle signals ranging from 150Hz to 2kHz. The tweeter would then cover the remainder of the audio range, ie, from 2kHz to 20kHz.

## Passive crossovers

In most loudspeaker systems, the incoming audio signal is divided into separate frequency bands using passive filters. These ‘crossover filters’ are located inside the loudspeaker box itself, and are made up using inductors, capacitors and resistors.

A well-designed crossover network gives outputs to match the particular drivers used. This ensures that each driver (ie, woofer, midrange and tweeter) is fed only with a frequency band it can effectively reproduce. In addition, the design must cater for drivers that have different sensitivities and set the signal levels to achieve an overall flat frequency response.

For example, the woofer is often less sensitive than the midrange driver and tweeter, and so the signals to the latter drivers must be reduced so that the output levels from the three drivers are well matched. This does waste amplifier power, however.

Another problem to contend with is non-linearity in the driver impedances. Extra components are often used in the crossover network to correct this, so that the filter appears to drive a purely resistive load. As a result, the crossover networks in high-performance speaker systems are often complex and can be difficult to design and optimise.

They also interpose a complex *RLC* network between the amplifier and the speakers, which can mean a loss of damping factor. This particularly affects the lower frequencies, where a high damping factor is most needed to achieve tight, clean bass and midrange reproduction.

As shown in Fig.1, a single power amplifier usually drives the passive

crossover network in a loudspeaker system. However, some loudspeaker systems provide additional connections so that each driver can either be driven independently by its own amplifier (via its passive filter) or by a single amplifier, but with separate wiring to each passive filter section.

## Active crossovers

Active crossovers are an alternative to passive filtering. However, for this to work, a separate amplifier is required for each driver – see Fig.2. For a stereo system, that means six (mono) power amplifiers (or three stereo amplifiers) to drive 3-way loudspeakers or four amplifiers for 2-way loudspeakers.

As shown in Fig.2, the crossover filtering is now placed ahead of each amplifier to set the frequency band applied to its driver. There are two advantages to this scheme: (1) better control of the driver and (2) the inductive load presented by the driver does not affect the filter response (as it does in a passive system).

## Specifications

**Voltage gain:** adjustable from 0-2; typically set at 1

**Frequency response:** filter dependent

**Filter attenuation slope:** 24dB/octave or 80dB/decade

**Total harmonic distortion (THD):** typically 0.003% at 1V RMS


**Signal-to-noise ratio (SNR):** >100dB with respect to 1V input and 22Hz to 22kHz unweighted

**Input impedance:** 47k $\Omega$

**Supply Voltage:**  $\pm 15V$  to  $\pm 60V$  DC dual rail supply, or +12V to 30V DC single rail supply, or 11V to 43V AC

**Current Consumption:** 40mA maximum

# Constructional Project

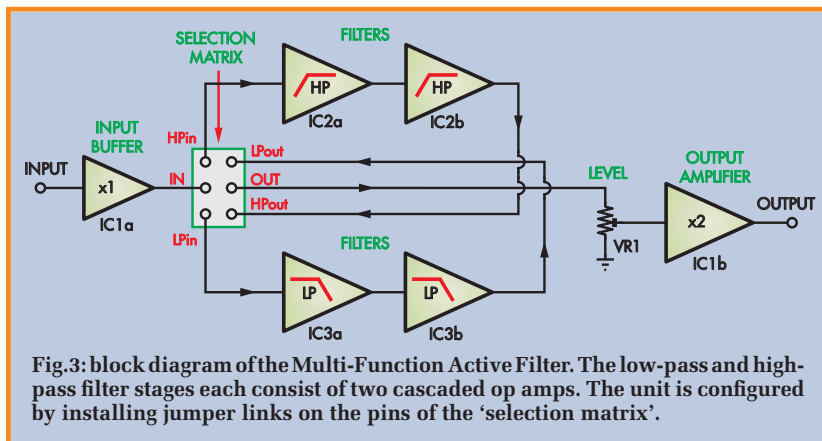

So, our Multi-Function Active Filter module is designed to be used ahead of each amplifier. Basically, you need to build and configure one module for each driver (and amplifier) in the system. For a woofer, the module would be configured as a low-pass (LP) filter, while a bandpass (BP) filter would be used ahead of the midrange amplifier. The tweeter driver amplifier would have a high-pass (HP) filter ahead of it.

## Supply options

In operation, the Multi-Function Active Filter would typically be powered from the supply rails of the amplifier. Options are available to power the module from supply rails ranging from  $\pm 60V$  down to  $\pm 15V$ , or from an 11V to 43V AC source.

The filter can also be powered from a single supply rail, such as +25V, +15V or +12V. The 12V option enables it to be used in cars.

On-board jumper links are used to configure the module for LP, BP or

HP operation. The roll-off frequencies are set by selecting the appropriate resistor and capacitor values in the filter feedback networks. These filter component calculations are made easy by using freely available software from the Internet.

## Block diagram

The block diagram of the Multi-Function Active Filter (minus the power supply) is shown in Fig.3. It uses an input buffer stage (IC1a), four op amps to form the filter stages (IC2a, IC2b and IC3a, IC3b) and an output amplifier stage (IC1b).

IC1a is configured with a gain of one and can be connected to drive either the HP or LP filter stages, depending on the jumper options on the 'Selection Matrix' block. If we want an HP filter, then terminal 'IN' is connected to 'HPin' on the matrix block. Alternatively, for an LP filter, 'IN' is connected to terminal 'LPin'.

As shown, the high-pass filter uses two 2-pole HP filters based on IC2a and

IC2b. These are connected in series (or 'cascaded'). Similarly, the low-pass filter stage consists of 2-pole LP filters, based on IC3a and IC3b.


The response for an HP filter and the way the filter response is described, is shown in Fig.4a. As indicated, the region where frequencies pass through unattenuated is called the passband. Below the cutoff frequency, the response begins to roll off (or is reduced) in level. This roll-off region is called the stopband.

An LP filter is similar, except that it allows low-frequency signals to pass through, and blocks signals above the cutoff point (Fig.4b). Finally, the bandpass filter rolls off both the low and high-frequency signals, and the pass band is between the high-pass and low-pass cutoff frequencies (Fig.4c).

## Roll-off slope

Note that the signal is not fully attenuated at the cutoff points, but instead gradually decreases at a rate determined by the roll-off slope. In this case, each 2-pole filter stage has a roll off of 40dB per decade or 12dB per octave. However, because the filter stages are cascaded, this roll-off increases to 80dB per decade, or 24dB per octave, and the signal level is actually 6dB down at the cutoff (crossover) points.

For a high-pass filter, the output from IC2b is fed through to level control VR1 by connecting point 'HPout' to 'OUT' in the selection matrix. Alternatively, for a low-pass filter, the output of IC3b at 'LPout' is connected to the 'OUT' terminal.

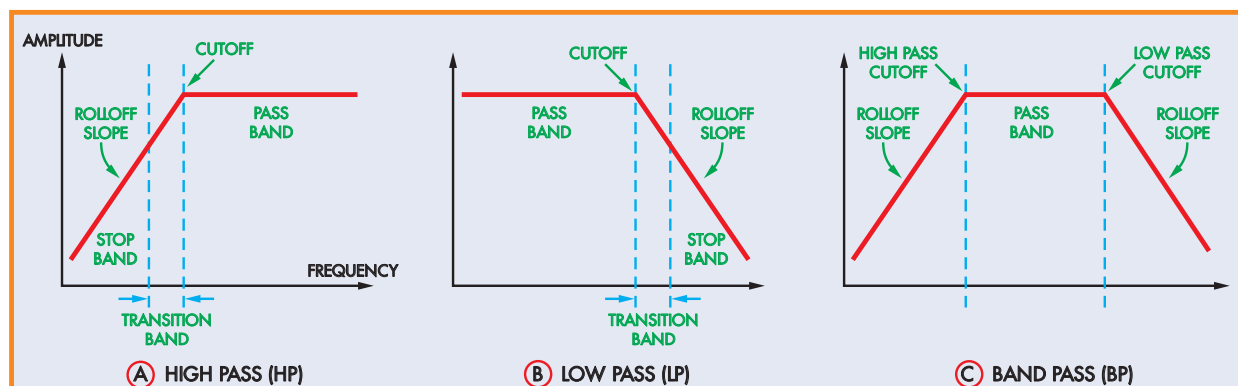

**Fig.4: the high-pass filter (A), low-pass filter (B) and bandpass filter (C) response characteristics. Because the op amp filter stages are cascaded, the rolloff slope in each case is 24dB per octave and the signal is actually 6dB down at the cutoff (crossover) points.**

## Amplifiers For Active Crossover Systems

### THE AUDIO AMPLIFIER

requirements for active crossover loudspeaker systems depend on the power handling rating for each loudspeaker. Typically, a woofer (or sub-woofer) amplifier should have twice the power of the midrange and treble amplifiers. For example, a 100W power amplifier could be used for the woofer, and 50W amplifiers used for the mid-range and treble drivers.

One problem is that the output from a preamplifier will only have a single RCA phono output for each left and right channel. However, you will need to connect the preamp signal to two or three active filters, depending on how many drivers are in the loudspeaker.

This problem is easily overcome by using an RCA phono Plug to 2 × RCA phono Socket, such as the Jaycar Cat. PA-3560. Two such adaptors will be required for each channel if you want to drive three active filter modules (ie, if you have a 3-way loudspeaker system).

Alternatively, you could use RCA phono plug-to-plug leads, with piggyback RCA phono sockets (eg, Jaycar WA-7090/1/2/3) or you could make up your own 2-way or 3-way phono socket panels.

### Bandpass filter connections

Bandpass filtering is achieved by cascading the high-pass and low-pass filter stages; ie, by connecting the output of the high-pass stages to the input of the low-pass stages, or vice versa. However, it is normal to feed the signal to an HP filter first, and then use this to drive the LP filter, rather than placing the LP filter first. This will result in less noise due to the final low-pass filtering.

However, you can connect the LP filters first if that's what you want to do.

Normally, to configure a bandpass filter, the signal is first fed to HP filter stage IC2a by linking 'IN' to 'HPin'. The output from IC2b is then fed to the input of low-pass stage IC3a by connecting 'HPout' to 'LPin' in the Selection Matrix. The resulting bandpass filtered signal at the output of IC3b is then fed to VR1 by connecting 'LPout' to 'OUT'.

### Level control

The signal on VR1's wiper is fed to IC1b. This is configured as a non-inverting

amplifier with a gain of two. As a result, VR1 can be adjusted to vary the signal at its output between zero and x2. This level adjustment allows the sound levels from the woofer, midrange and tweeter drivers to be adjusted when multiple filter modules are used.

By the way, the recommended design for each 2-pole stage is for a Butterworth response. When connected in series, the result of cascading two Butterworth filters is a Linkwitz-Riley (L-R) response.

This is ideal because at the crossover region, where one filter takes over from another, the overall L-R frequency response is flat. Note that the HP and LP filters must be set to the same crossover frequency for this to happen.

As indicated previously, the Multi-Function Active Filter board can only produce a single LP, HP or BP filter output. This means that it can only provide a signal to one loudspeaker driver – it is not designed to provide two (or more) outputs.

## Parts List

- 1 PC board, code 812, available from the *EPE PCB Service*, size 123mm × 63mm
- 1 UB3-size plastic case, 130mm × 68mm × 44mm (optional)
- 1 3-way PC-mount screw terminal block, 5.08mm pin spacing
- 4 8-pin DIP IC sockets
- 1 3-way DIL pin header, with 2.54mm pin spacings
- 2 3-way SIL pin headers, with 2.54mm pin spacings
- 5 jumper plugs, to suit pin headers
- 1 100mm length of 0.8mm tinned copper wire or four 0Ω links
- 4 PC stakes

### Semiconductors

- 3 LM833 dual op amps (IC1 to IC3)
- 1 TL071, LF351 single op amp (IC4)
- 2 1N4744 15V 1W Zener diodes (ZD1, ZD2)
- 2 1N4004 1A 400V diodes (D1, D2)

### Capacitors

- 2 470µF 16V PC electrolytic
- 1 100µF 16V PC electrolytic
- 2 4.7µF non-polarised (NP) electrolytic
- 2 100nF MKT polyester
- 1 10nF MKT polyester
- 1 220pF ceramic
- C1, C2, C3 to suit application (use MKT polyester) (see text and tables)

### Resistors (0.25W, 1%)

- 1 47kΩ      2 150Ω
- 4 10kΩ      3 10Ω
- Ra, Rb, R1, R2 and R3 to suit power supply and filter type (use 1% 0.25W for R1, R2 and R3) (see text / tables)

**This in turn means that if you want to separate LP, BP and HP filter outputs, then three filter modules must be built (or six for a stereo system). Basically, a different filter is required for each amplifier, and each can be installed inside its associated amplifier's case.**

The inputs of the various active filter modules are then all driven in parallel by the preamplifier.

### Circuit details

OK, let's now take a look at the full circuit details – see Fig.7. It comprises





Fig.5: this screen grab shows the frequency response for the low-pass filter configuration with a nominal corner frequency of 1kHz. The attenuation slope is 24dB per octave.



Fig.6: the frequency response for a high-pass filter configuration with a nominal corner frequency of 1kHz. Once again, the attenuation slope is 24dB per octave.

three dual op amps (IC1 to IC3) plus a single op amp (IC4) in the power supply section.

The first thing to note here is that the designations for the op amps used in the input buffer, filter and output stages match those shown on the block diagram of Fig.3. So, if you've followed the description for Fig.3, understanding how the full circuit works should be a snack.

As shown, the incoming audio signal is applied to unity-gain buffer stage IC1a via a 4.7μF non-polarised capacitor and a 10Ω stopper resistor. The capacitor is there to block any DC voltage, while the stopper resistor blocks any stray RF signals that may have been picked up by the leads.

IC1a is biased to Earth 2 via the associated 47kΩ resistor. This earth

is at 0V for plus and minus supply rails and at half-supply (0.5Vcc) for a single supply.

IC1a's output is fed to either HP filter IC2a or to LP filter IC3a, depending on the input jumper location in the Selection Matrix. This works exactly as indicated previously in the description for the block diagram (Fig.3).

Both the high-pass and low-pass filter stages (IC2a, IC2b, IC3a and IC3b) use a multiple feedback (MFB) 2-pole arrangement. This was used in preference to the unity-gain Sallen-Key style of filter because the MFB response is less affected by component value variations due to manufacturing tolerances.

Note that 10Ω stopper resistors are included in series with the HP filter

inputs. This is done in each case to prevent instability (oscillation) in the preceding stage. IC2a's output is fed to the second HP filter stage IC2b (ie, the stages are cascaded), while IC3a drives the second LP filter stage IC3b.

For an HP filter, IC2b's output is fed to level potentiometer VR1 by linking 'HPout' to 'OUT' in the Selection Matrix. Alternatively, for an LP filter, the output from IC3b is connected to level potentiometer VR1 using a jumper to link 'LPout' to 'OUT'. Again, this functions exactly as described for block diagram Fig.3.

Finally, for a bandpass arrangement, HP filter IC2b's output is fed to LP filter IC3a via a jumper link between 'HPout' and 'LPin'. IC3b's output is then fed to VR1 via a jumper link between 'LPout' and 'Out'.

## Minimising noise

As stated earlier, the signal from IC1a is normally fed to the HP filter stages first ('IN' linked to 'HPin'), so that the LP filter stages can then minimise noise. Alternatively, the LP stages can be placed first by linking 'IN' to 'LPin', 'LPout' to 'HPin' and 'HPout' to 'OUT'.

The resulting audio signal on VR1's wiper is fed directly to the non-inverting input (pin 5) of IC1b. As previously stated, this amplifier has a gain of 2, but this gain reduces to 1 for frequencies above 72kHz due to the 220pF capacitor across the feedback resistor. IC1b's output appears at pin 7, and is coupled to the output terminals via a 150Ω isolating resistor and a 4.7μF NP (non-polarised) capacitor and 150Ω isolating resistor.

## Power Supply

In operation, the Multi-Function Active Filter would typically be powered from the supply rails of the amplifier. As stated previously, options are available to power the module from dual DC supply rails or from an AC source.

The unit can also be powered from a single supply rail, such as +25V, +15V or +12V. The 12V option enables it to be used in a car.

In summary, the three options for powering the module are as follows:

- 1) A dual-rail (plus and minus) supply of between ±15V and ±60V (this connects to the '+' and '-' supply inputs of the terminal block)
- 2) A single DC supply rail, ranging from 12V to 60V (this connects

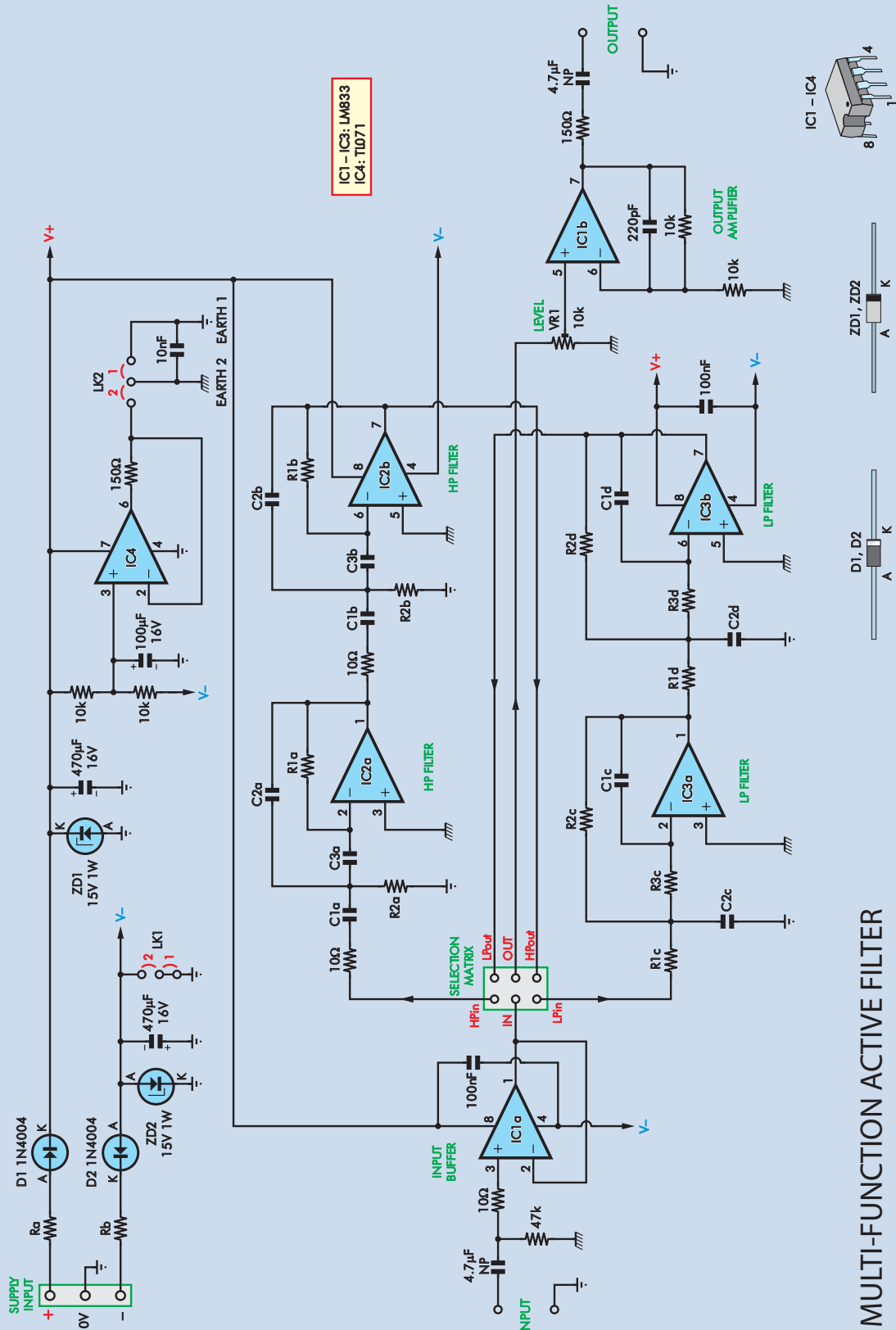


Fig.7: the complete circuit for the Multi-Function Active Filter. IC1a serves as an input buffer stage, while op amp IC1b is the output amplifier. Cascaded op amp stages IC2a and IC2b together form the high-pass filter, while IC3a and IC3b make up the low pass filter. IC4 is used to provide a half-supply reference if the unit is powered from a single-rail power supply.



# Constructional Project

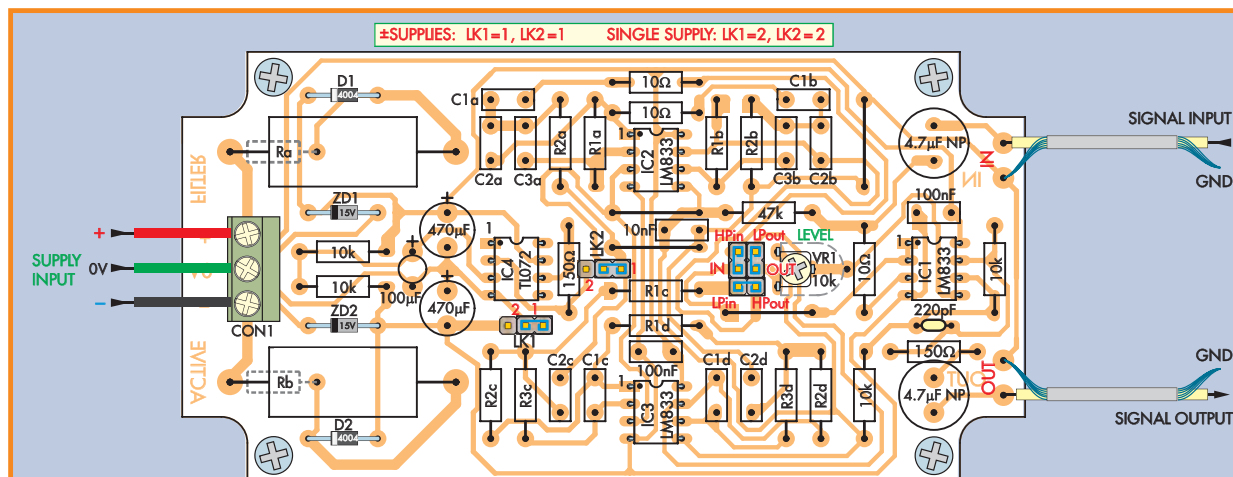


Fig.8: follow this parts layout diagram to build the PC board. The various tables show the values for resistors Ra and Rb and for the filter components (R1-R3 and C1-C2), while the linking options for the selection matrix are shown on the right. Links LK1 and LK2 go in position 1 for a dual-rail supply (or for an AC supply), but must be moved to position 2 for a single-rail supply.

HPin	LPout	HPin	LPout	HPin	LPout
IN	OUT	IN	OUT	IN	OUT
LPin	HPout	LPin	HPout	LPin	HPout
LOW PASS FILTER	HIGH PASS FILTER	BANDPASS FILTER			

between the '+' and '0V' supply inputs)

- 3) An AC supply, ranging from 12-43V AC (here, the '+' and '-' inputs are tied together and the AC supply is connected between these commoned inputs and the 0V input).

In the case of a dual supply, diodes D1 and D2 (1N4004) protect the circuit against reverse polarity connection. Zener diodes ZD1 and ZD2 then regulate the supply to provide  $\pm 15V$  rails, which are then used to power op amps IC1 to IC3. Two  $470\mu F$  capacitors decouple the  $\pm 15V$  supply rails.

Resistors Ra and Rb are used to limit the current into ZD1 and ZD2. The values of these two resistors depend on the input voltage (see Table 3 for the required values).

In addition, for a dual supply, Earth 1 and Earth 2 are connected together by installing jumper link LK2 in position 1 (LK1 must also be in position 1 or left out). With no signal, this sets op amps IC1, IC2 and IC3 so that their outputs sit at 0V.

For a single supply, IC1 to IC3 need to be biased at half-supply so that the signal can swing symmetrically without clipping. This half-supply rail is provided by op amp IC4. As shown, a half-supply voltage is derived using two  $10k\Omega$  resistors in series across the positive supply rail. This is decoupled by a  $100\mu F$  capacitor and then buffered by IC4 to drive Earth 2 when LK2 is in the '2' position.

In addition, for a single supply, the negative supply pins for IC1 to IC3 are connected to the 0V supply

rail by placing link LK1 in position 2.

Note that when LK2 is in position 2, the half-supply output from IC4 is bypassed to earth (0V) via a  $10nF$  capacitor. This prevents oscillation in the filter op amps. The  $150\Omega$  resistor at pin 6 of IC4 isolates the op amp's output from the capacitance in the shielded output leads.


Finally, for an AC supply, diodes D1 and D2 function as half-wave rectifiers to derive positive and negative supply rails. The circuit then functions exactly the same as for a dual-rail DC supply.

## Construction

All parts for the Multi-Function Active Filter are mounted on a single-sided PC board, coded 812, measuring  $123mm \times 63mm$ . This board is available from the

Table 1: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	1	$47k\Omega$	yellow violet orange brown	yellow violet black red brown
□	1	$15k\Omega$	brown green orange brown	brown green black red brown
□	1	$13k\Omega$	brown orange orange brown	brown orange black red brown
□	1	$12k\Omega$	brown red orange brown	brown red black red brown
□	4	$10k\Omega$	brown black orange brown	brown black black red brown
□	2	$6.2k\Omega$	blue red red brown	blue red black brown brown
□	2	$5.6k\Omega$	green blue red brown	green blue black brown brown
□	2	$4.7k\Omega$	yellow violet red brown	yellow violet black brown brown
□	2	$150\Omega$	brown green brown brown	brown green black black brown
□	3	$10\Omega$	brown black black brown	brown black black gold brown

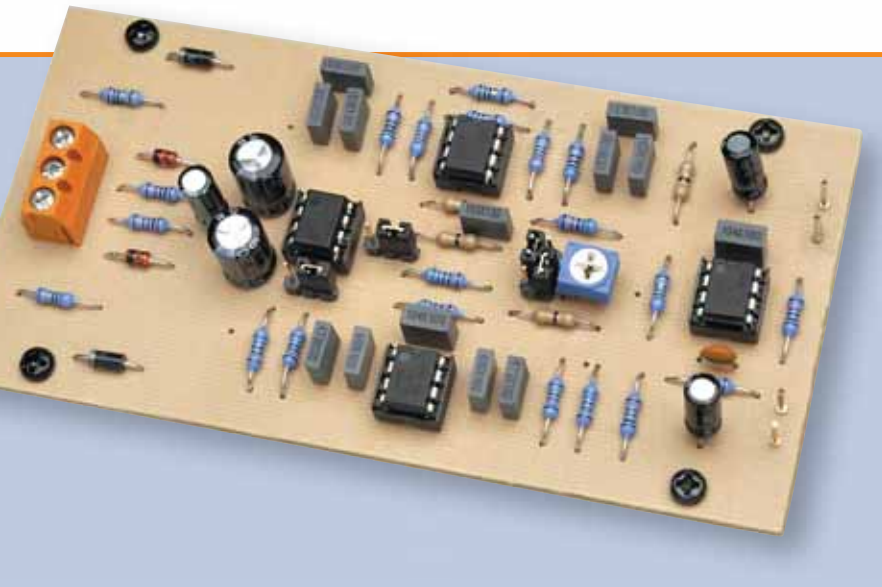

**Table 2: Filter type configuration**

Low-Pass Filter	High-Pass Filter	Bandpass Filter
Link IN to LPin; Link LPout to OUT	Link IN to HPin; Link HPout to OUT	Link IN to HPin; Link HPout to LPin; Link LPout to OUT

**Table 3: Power supply configuration**

Input Voltage	Ra	Rb	Links
±60VDC, 43VAC	1.2kΩ 5W	1.2kΩ 5W	LK1 position 1, LK2 position 1
±55VDC, 40VAC	1kΩ 5W	1kΩ 5W	LK1 position 1, LK2 position 1
±50VDC, 35VAC	820Ω 5W	820Ω 5W	LK1 position 1, LK2 position 1
±45VDC, 30VAC	680Ω 5W	680Ω 5W	LK1 position 1, LK2 position 1
±40VDC, 28VAC	560Ω 5W	560Ω 5W	LK1 position 1, LK2 position 1
±35VDC, 25VAC	470Ω 5W	470Ω 5W	LK1 position 1, LK2 position 1
±30VDC, 20VAC	390Ω 5W	390Ω 5W	LK1 position 1, LK2 position 1
±25VDC, 18VAC	270Ω 5W	270Ω 5W	LK1 position 1, LK2 position 1
±20VDC, 15VAC	120Ω 1W	120Ω 1W	LK1 position 1, LK2 position 1
±15VDC, 11VAC	10Ω 0.5W	10Ω 0.5W	LK1 position 1, LK2 position 1
+30V	390Ω 5W	NA	LK1 position 2, LK2 position 2
+25V	270Ω 5W	NA	LK1 position 2, LK2 position 2
+20V	120Ω 1W	NA	LK1 position 2, LK2 position 2
+15V	10Ω 1/2W	NA	LK1 position 2, LK2 position 2
+12V	10Ω 1/2W	NA	LK1 position 2, LK2 position 2

*EPE PCB Service.* The board can either be housed inside a UB3-size plastic case, measuring 130mm × 68mm × 44mm, or installed within an amplifier case. Note that corner cutouts will be required if mounting the board in the specified case, to clear the integral mounting posts.

Fig.8 shows the parts layout on the PC board. However, before starting the assembly, you have to decide on the power supply to be used, the type of filter arrangement and the cutoff frequency.

Table 3 shows the resistors (Ra and Rb) required for various power supply voltages, plus the LK1 and LK2 linking options. The filter component values are selected from Table 4 and Table 5 (see also the panel titled 'Calculating The Filter Component Values').

Note that for the single supply option, Rb, D2, ZD2 and C5 can be omitted. However, it does not matter if they are installed. Alternatively, for a dual rail supply option, IC4, R4, R5 and C6 are not required. Note also that either 5W or 0.5W resistors can be used for

**POSCOPE MEGA1+**

- .....it's oscilloscope.....
- .....it's spectrum analyzer.....
- .....it's datalogger.....
- .....it's recorder.....
- .....it's logic analyzer.....
- .....it's pattern generator.....
- .....it's signal generator.....

**POKEYS**



- .....it's keyboard emulator.....
- .....it's joystick emulator.....
- .....it's USB or Ethernet.....
- .....it's ModBus and TCP.....
- .....can drive LCDs, LED matrixes.....
- .....can read encoders, keyboard matrixes.....
- .....can handle more than 300 I/Os.....
- .....matlab, Labview, C#, VB.NET, VB6.0 and Delphi examples.....

[www.poscope.com](http://www.poscope.com)



### Using The FilterPro Software From TI

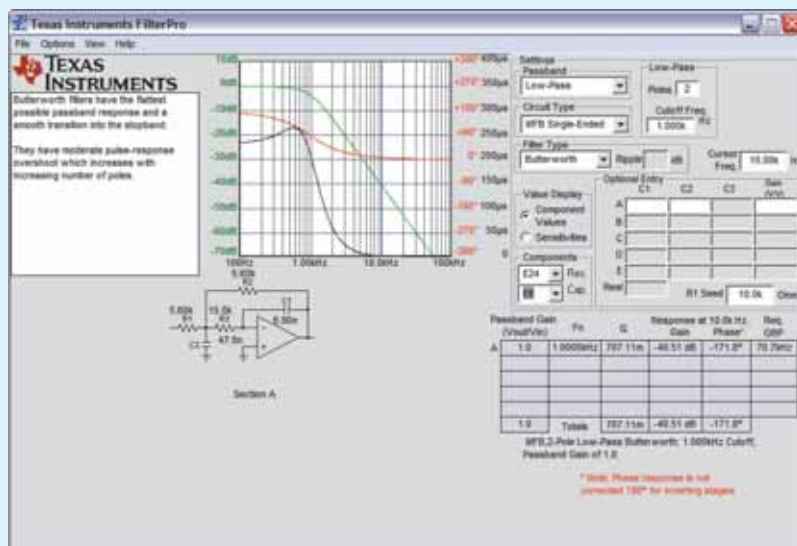


Fig.9: this is how FilterPro should look when set up to calculate values for a low-pass 2-pole Butterworth filter.

The first step here is to download the 2.848MB zipped file (available from <http://focus.ti.com/docs/toolsw/folders/print/filterpro.html>) and run the FilterProSetup.exe file. That done, navigate to C:\ProgramFiles\TI Analog Design Centre\Filterpro and create a shortcut on your desktop for FilterPro.exe

When you launch FilterPro, the program will show a screen with a graph, the filter circuit and various settings (see Fig.9). The graph shows the frequency response of the filter using an amplitude versus frequency plot. The actual rolloff can be seen, as well as any excursions in the response across the passband or at the cutoff frequency.

### Calculating The Filter Component Values

**C**HOOSING THE CROSSOVER FREQUENCIES for loudspeaker drivers requires careful consideration. You will need the data sheet for each driver in order to make a decision as to where the crossover frequency should lie. Ideally, the crossover frequency should be well away from the driver's resonance frequency and the adjacent drivers should be a good match to ensure a smooth frequency response across the audio band.

Many books have been written on the subject and a good reference is 'The Loudspeaker Speaker Design Cookbook' by Vance Dickason. This is available from Jaycar, Cat. BA-1400.

Once you have decided on the crossover frequencies, the filter component values can be calculated. Table 4 and Table 5 show the recommended values for a range of common frequencies.

For other frequencies, you can download software off the net to make the calculations easier. Our recommendation is to use 'Filter Pro' from Texas Instruments. You can download it from <http://focus.ti.com/docs/toolsw/folders/print/filterpro.html>

If this site becomes unavailable, do a search for 'TI filter software' or for 'FilterPro'. Information on how to use FilterPro and other useful information on filters is available at <http://focus.ti.com/lit/an/sbfa001a/sbfa001a.pdf>

An alternative on-line program is also available from Okawa Electric – see the section entitled 'Using the FilterPro Software From TI'.

Two other responses are also shown on the graph: the phase response and the group delay. The phase response plots the phase variations in the filter output as a function of frequency. By contrast, the group delay shows the slope (or rate of change) in the phase response, and is ideal for displaying the filter response to a pulse signal.

Several different filter types can also be selected – ie, Bessel, Butterworth and Chebychev. Each has a different 'Q' value and so the filter response differs from one to the other.

Each filter type has its own advantages and disadvantages. For example, a Bessel filter has a Q of 0.577 ( $1/\sqrt{3}$ ) and has a smooth but drooping amplitude response across the passband. It has very little pulse response overshoot and its roll off is not as steep as for a Butterworth filter.

Butterworth filters have a 'Q' of 0.7071 ( $1/\sqrt{2}$ ) and have the flattest possible (maximally flat) amplitude response in the passband and a moderate pulse response rise (or overshoot) at the cutoff frequency.

A Chebychev filter has a higher Q again. This filter has ripple in the passband, a steeper cutoff rate and higher pulse response overshoot compared to the two lower Q filters. The Q value depends on the amount of ripple that can be tolerated and is 0.956 for a 1dB passband ripple and 0.863 for a 0.5dB passband ripple.

A filter with a 'Q' of 0.5 is critically damped and shows no pulse response overshoot. The Bessel, Butterworth, and Chebychev filters are all under-damped and so each show some degree of overshoot in its response. An over-damped filter would have a 'Q' of less than 0.5.

#### Butterworth filters

For audio work, the best compromise filter type is the Butterworth, especially when two filters are cascaded, as in our Multi-Function Active Filter. So, in FilterPro, select

Ra and Rb, as the PC board accepts both types.

For an LP filter only, there is no need to install the HP components. These include IC2, R1a, R2a, C1a, C2a, C3a, R1b, R2b, C1b, C2b and C3b. The two 10Ω stopper resistors can also be left out (but not the one on pin 3 of IC1a).

Similarly, for an HP filter only, you can leave out LP components IC3, R1c, R2c, R3c, C1c, C2c, R1d, R2d, R3d, C1d and C2d.

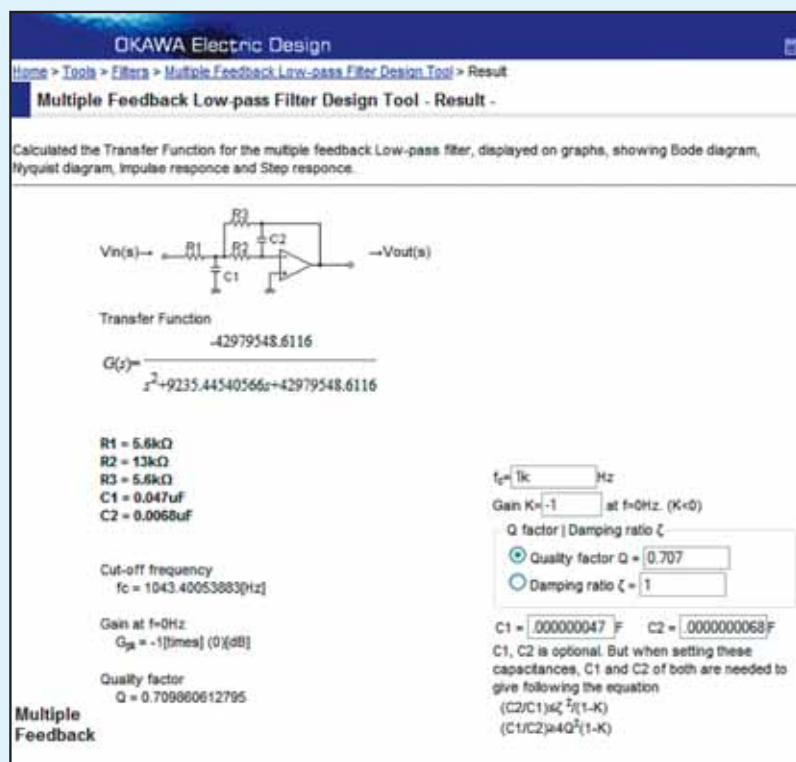


Fig.10: the low-pass filter design software from Okawa Electric shows the circuit values and filter responses in a similar way to FilterPro. A high-pass filter design tool is also available from Okawa Electric – see text.

‘Butterworth’ as the filter type and select ‘2’ for the number of poles. The circuit type should be set to ‘MFB single ended’ and the set display value should be ‘component values’.

For components, select ‘E24’ series for the resistors and either ‘E6’ or ‘E12’ for the capacitors (these ‘E’ series values select the number of values available in a decade range). The relevant resistor and capacitor values will then be calculated, based on readily available components.

Note: some component suppliers may not have the full E12 capacitor series. In

that case, a recalculation may have to be made using the E6 series instead if using the E12 series gives components values that are unavailable.

The next step is to enter the cutoff frequency, select either LP or HP and then click on an unused section of the screen to start calculating the values.

Note that the circuit for the multiple feedback 2-pole filter shows the values for a single 2-pole filter section. These same values are also used in the second 2-pole filter stage of the Multi-Function Active Filter.

FilterPro provides values for the resistors and capacitors using R1, R2 and R3 and C1, C2 and C3 component designations. These are easily equated with the component designations on the circuit diagram (Fig.7) and parts layout diagram (Fig.8). Note: the a, b, c and d designations on Fig.7 are there simply to distinguish one filter circuit from another.

## Bandpass filter

A bandpass filter is made by designing two separate cascaded HP and LP circuits. For example, if you want a bandpass filter with roll offs at 500Hz and 2kHz, you simply use FilterPro to design independent 500Hz high-pass and 2kHz low-pass stages.

Do not select a bandpass design in FilterPro – the calculations are not applicable to the Multi-Function Active Filter module described here.

## Alternative software

If you want to use an alternative program to FilterPro, or if you want to check the predicted response of your filter using the values given by FilterPro, a good online program is one from Okawa Electric. For the low-pass filter, go to <http://sim.okawa-denshi.jp/en/OPtazyuLowkeisan.htm> For the high-pass filter navigate to <http://sim.okawa-denshi.jp/en/OPtazyuHikeisan.htm>

These sites not only allow you to calculate filter components, but also allow you to input component values. The program will then show the actual cutoff frequency, filter Q and other features. These calculations can sometimes give a better result (ie, closer to the required Q and cutoff frequency) than FilterPro.

Note, however, that the R1, R2, R3, C1, C2 and C3 labelling is a little different to that of the FilterPro and our circuit, so make sure you transpose the labelling correctly. Also, do not forget to tick the Q value field at 0.707 rather than using the ticked damping ratio field of 1 for the calculation.

## Board assembly

Start the assembly by carefully inspecting the board for any defects in the copper tracks, then install the four wire links. Alternatively, 0Ω resistors can be used instead of the wire links. These look similar to a 0.25W resistor, but have just one single black band around the centre of the body.

Next, install four PC stakes at the input and output positions, then install the resistors and trimpot VR1. Table

1 shows the resistor colour codes, but a digital multimeter (DMM) should also be used to check values, just to make sure.

Follow these with the diodes, Zener diodes and the ICs. These parts must all be installed with the correct orientation. Note that IC4 is a different type to IC1, IC2 and IC3, so don’t get it mixed up. We used IC sockets for the ICs and these sockets also have an orientation notch at one end – see Fig.8.

The electrolytic capacitors are next on the list and these must also be oriented correctly. The only exceptions here are the two 4.7μF NP (non-polarised) types which can go in either way around.

Once these parts are in, install the two 3-way SIL (single in-line) headers for links LK1 and LK2. The two jumpers can then be fitted to these headers. They both go in position 1 for a dual-rail supply (or if you are using an AC supply) – see Table 3.


# Constructional Project

**Table 4: High-pass filter component values (Butterworth response)**

Frequency	C1 (IEC Code) (EIA Code)	C2 (IEC Code) (EIA Code)	C3 (IEC Code) (EIA Code)	R1	R2
50Hz	330nF (334)	330nF (334)	330nF (334)	20k $\Omega$	4.3k $\Omega$
100Hz	150nF (154)	150nF (154)	150nF (154)	22k $\Omega$	5.1k $\Omega$
120Hz	150nF (154)	150nF (154)	100nF (104)	24k $\Omega$	4.7k $\Omega$
150Hz	100nF (104)	100nF (104)	100nF (104)	22k $\Omega$	5.1k $\Omega$
200Hz	68nF (683)	68nF (683)	100nF (104)	20k $\Omega$	4.7k $\Omega$
300Hz	47nF (473)	47nF (473)	68nF (683)	20k $\Omega$	4.7k $\Omega$
500Hz	33nF (333)	33nF (333)	33nF (333)	20k $\Omega$	4.3k $\Omega$
1kHz	15nF (153)	15nF (153)	15nF (153)	22k $\Omega$	5.1k $\Omega$
1.5kHz	10nF (103)	10nF (103)	10nF (103)	22k $\Omega$	5.1k $\Omega$
2kHz	6.8nF (6n8) (682)	6.8nF (6n8) (682)	10nF (103)	20k $\Omega$	4.7k $\Omega$
3kHz	6.8nF (6n8) (682)	6.8nF (6n8) (682)	6.8nF (6n8) (682)	20k $\Omega$	4.7k $\Omega$
5kHz	3.3nF (3n3) (332)	3.3nF (3n3) (332)	3.3nF (3n3) (332)	20k $\Omega$	4.3k $\Omega$
10kHz	1.5nF (1n5) (152)	1.5nF (1n5) (152)	1.5nF (1n5) (152)	22k $\Omega$	5.1k $\Omega$
20kHz	680pF (681)	680pF (681)	1nF (102)	20k $\Omega$	4.7k $\Omega$

**Table 5: Low-pass filter component values (Butterworth response)**

Frequency	R1	R2	R3	C1 (IEC Code) (EIA Code)	C2 (IEC Code) (EIA Code)
50Hz	5.6k $\Omega$	5.6k $\Omega$	12k $\Omega$	150n (154)	1 $\mu$ F (105)
100Hz	5.6k $\Omega$	5.6k $\Omega$	15k $\Omega$	68nF (683)	470nF (474)
120Hz	4.7k $\Omega$	4.7k $\Omega$	12k $\Omega$	68nF (683)	470nF (474)
150Hz	5.6k $\Omega$	5.6k $\Omega$	13k $\Omega$	47nF (473)	330nF (334)
200Hz	6.2k $\Omega$	6.2k $\Omega$	15k $\Omega$	33nF (33)	220nF (224)
300Hz	6.2k $\Omega$	6.2k $\Omega$	13k $\Omega$	22nF (223)	150nF (154)
500Hz	5.6k $\Omega$	5.6k $\Omega$	12k $\Omega$	15n (153)	100nF (104)
1kHz	5.6k $\Omega$	5.6k $\Omega$	15k $\Omega$	6.8nF (6n8) (682)	47nF (473)
1.5kHz	5.6k $\Omega$	5.6k $\Omega$	13k $\Omega$	4.7nF (4n7) (472)	33nF (333)
2kHz	6.2k $\Omega$	6.2k $\Omega$	15k $\Omega$	3.3nF (3n3) (332)	22nF (223)
3kHz	6.2k $\Omega$	6.2k $\Omega$	13k $\Omega$	2.2nF (2n2) (222)	15nF (153)
5kHz	5.6k $\Omega$	5.6k $\Omega$	12k $\Omega$	1.5n (1n5) (152)	10nF (103)
10kHz	5.6k $\Omega$	5.6k $\Omega$	15k $\Omega$	680pF (681)	4.7nF (4n7) (472)
20kHz	6.2k $\Omega$	6.2k $\Omega$	15k $\Omega$	330pF (331)	2.2nF (2n2) (222)

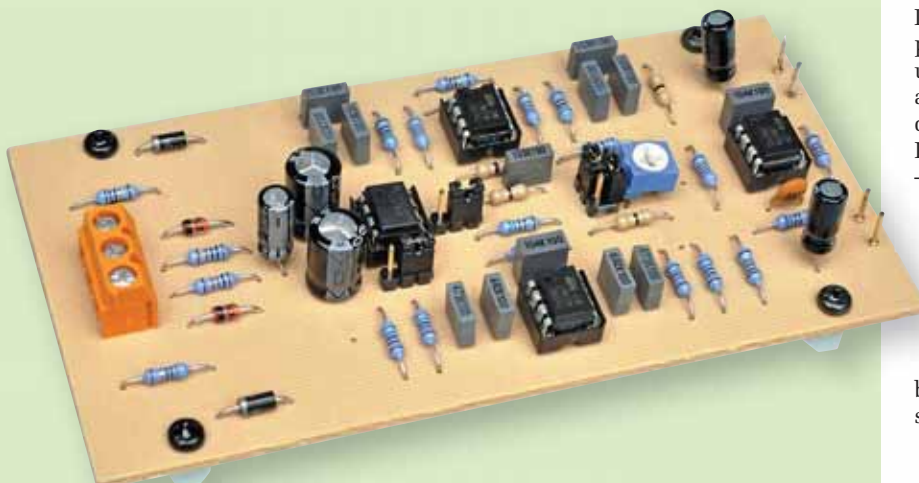

Be sure to choose the correct filter component values when building the PC board – see Tables 4 and 5. In this case, the board has been configured as a high-pass filter, and is set up to accept dual supply rails.

Alternatively, install them both in position 2 if you intend using a single rail supply.

The selection matrix requires a 3-way DIL (dual in-line) pin header and this should now be installed – it goes in just to the left of trimpot VR1. Once it's in, install the jumpers on this header to select your filter type (ie, LP, HP or bandpass).

The assembly can now be completed by installing the 3-way terminal block.

## Power supply checks

Before applying power, check that the supply link options are correct (see Table 3) and that the correct values have been installed for resistors Ra and Rb. Check also that you've installed the correct link options for the filter type.

Next, connect one probe of your DMM to the 0V supply input, apply power and use the other probe to measure the supply voltages on the ICs. For a dual ( $\pm$ ) or AC supply arrangement, check that there is +15V on pin 8 of IC1 to IC4. Similarly, there should be –15V on pin 4 of IC1 to IC3, while pin 4 of IC4 (if installed) should be at 0V.

For the single supply arrangement, check for +15V on pin 8 of ICs1-3 and on pin 7 of IC4 (if installed).

Note that the measured voltage will be lower if the supply voltage is less than 15V. Pin 6 of IC4 should be at half-supply (eg, 7.5V for a 15V supply).

**EPE**

Reproduced by arrangement  
with SILICON CHIP  
magazine 2011.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)




# Win a CAN Development Kit Using New Microchip PIC18F 'K80' MCUs

EPE  
EXCLUSIVE

**E**VERYDAY PRACTICAL ELECTRONICS is offering readers the chance to win a **Microchip** complete development kit for engineers wishing to add CAN (Control Area Network) communication to their designs.

The kit features the recently announced PIC18F 'K80' 8-bit CAN microcontrollers (MCUs). They feature 1.8V to 5.5V operation and eXtreme Low Power (XLP) technology, for the industry's lowest sleep current consumption of less than 20nA. The kits include a PIC18 Explorer Board (DM183032), plus plug in modules of the 44-pin PIC18F46K80 MCU (MA180031), and the 64-pin PIC18F66K80 (MA180032). For CAN implementation and evaluation, Microchip's CAN/LIN PICtail™ (Plus) Daughter Board (AC164130-2), will also be included.

The new 'K80' MCUs also feature an on-chip 12-bit analogue-to-digital converter (ADC) and a peripheral which enables mTouch™ capacitive touch-sensing user interfaces. The new MCUs are ideal for automotive applications, such as body control modules, lighting, door/seat/steering/window and HVAC controls; automation applications such as elevators and escalators, lighting, sensors and air conditioning controls; as well as industrial applications, including security systems, alarm controls and remote monitors.

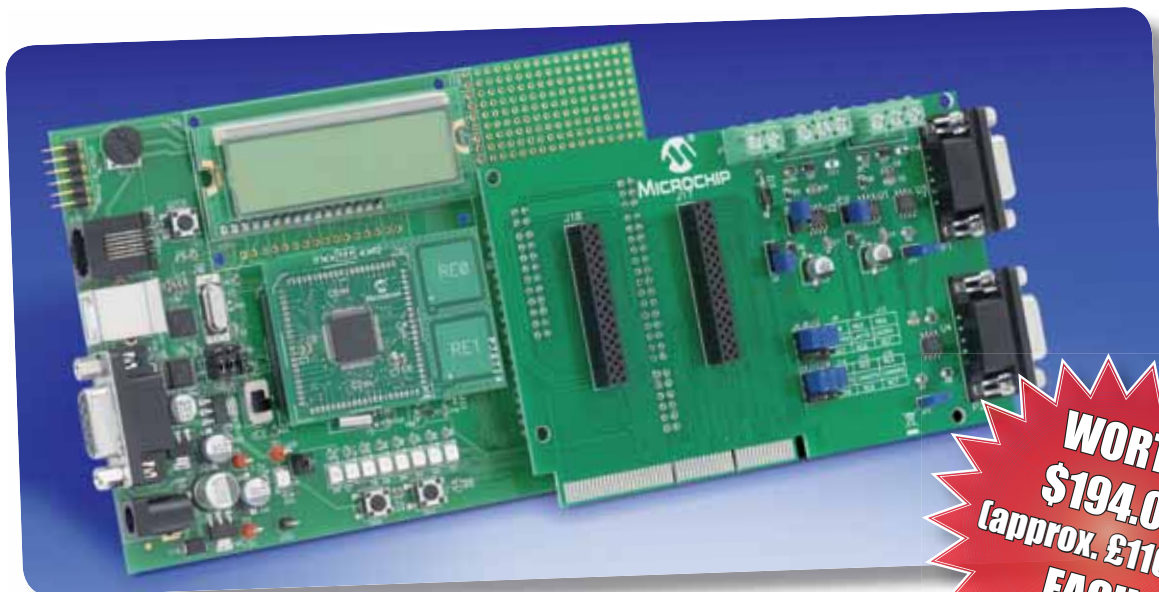


**WORTH  
\$194.00  
(approx. £116.00)  
EACH**

## CLOSING DATE

The closing date for this offer is 30 August 2011
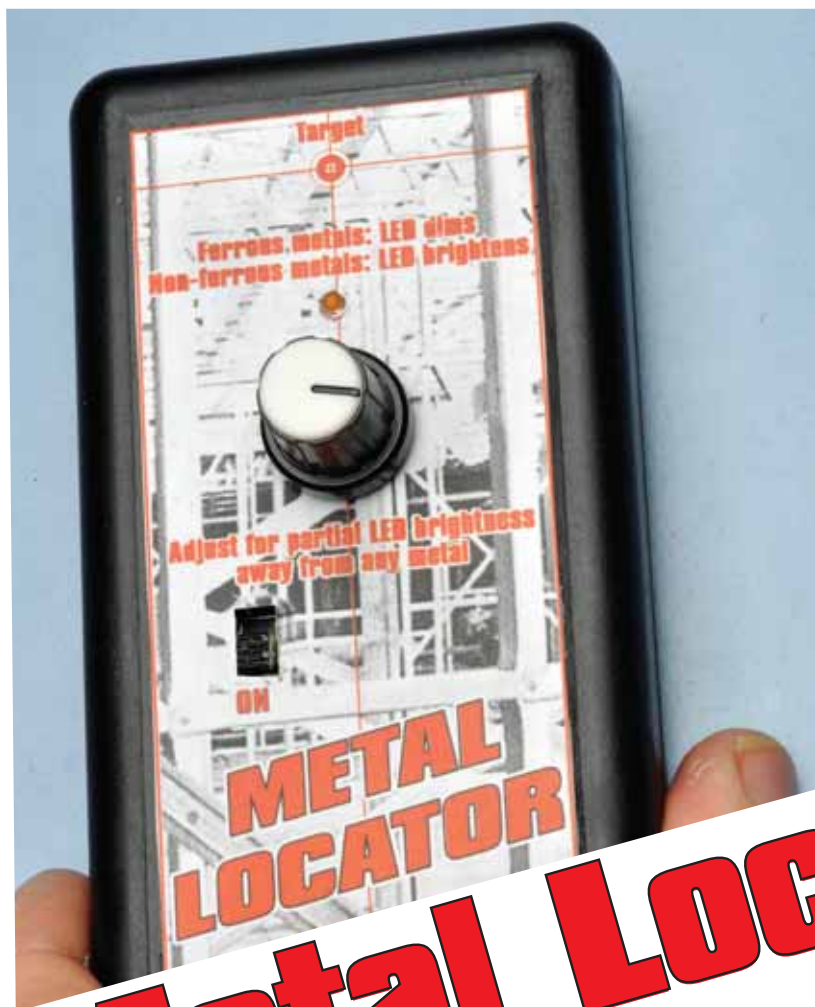
## HOW TO ENTER

For your chance to win a **Microchip CAN Development Kit**, visit [www.microchip-comps.com/epe-can](http://www.microchip-comps.com/epe-can)



***Ideal for finding steel frames and studs, steel bracing and nails in plaster walls, this Metal Locator can also show the length of the tang in knife handles, screwdrivers and other tools. Plus, it can discriminate between ferrous and non-ferrous metals.***

# Metal Locator

By JOHN CLARKE

**I**F YOU want to hang pictures, shelving or mirrors on a plaster wall in a steel-framed building it is useful to find where the metal studs are.

You may wish to secure your screws to the stud or alternatively, you may wish to avoid the stud and attach directly to the plaster wall using suitable fasteners. There are also other hidden items within the wall that should be located before drilling, such as metal bracing straps, screws and nails.

### **Metal locator**

With the *Metal Locator* you can find the metal stud positions as well as

any steel bracing, screw heads and nails. That is, provided the metal is no deeper than 25mm inside the wall. For small nails in wooden studs, it can detect them provided that the heads are within 10mm of the wall surface. Naturally, this device does not locate the timber studs themselves, nor can it find steel frames in walls that have a cladding thicker than 25mm (a very unusual wall, especially inside). Nor can it detect power cables inside walls.

The Metal Locator can distinguish between ferrous and non-ferrous metals. Ferrous metals include mild steel,

stainless steel (both magnetic and non-magnetic), wrought iron, high tensile steel, galvanised iron, tin-plated steel (steel cans or tinplate), passivated steels and cast iron. Non-ferrous metals include copper, brass, zinc, aluminium, gold, silver, lead and tin.

In the presence of ferrous metals, the LED on the Metal Locator dims. Conversely, the LED brightens in the presence of non-ferrous metal. For ferrous metals, the sensitivity knob is adjusted so that the LED is reasonably bright in the absence of the metal. The LED then dims in the presence of ferrous metal.


To detect non-ferrous metals, the sensitivity is adjusted so that the LED is dim in the absence of the metal. The LED will then brighten in the presence of the non-ferrous metal. Greater sensitivity can be had with the LED just glowing in the absence of metal for detection of either metal type.
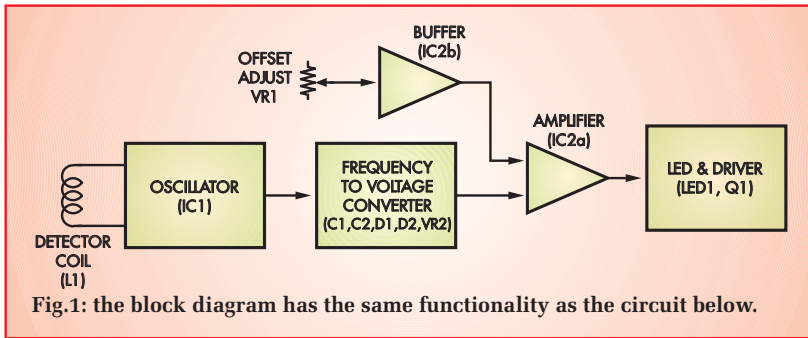
### **Specifications**

**Detection range:** up to 25mm from the underside of the case

**Current drain:** <20mA with LED fully lit





The Metal Locator is housed in a compact plastic case that includes a 9V battery compartment. On the lid are the on/off switch, sensitivity control and the indicating LED.

## How it works

The block diagram of the Metal Locator is shown in Fig.1. It is based on an astable oscillator controlled by the detector coil, L1. The oscillation frequency changes with the presence of metal. For ferrous metals, the frequency decreases, while for non-ferrous metals the frequency increases.

The oscillator's output is fed to a frequency-to-voltage converter. Small frequency changes are then detected as voltage changes that can easily be

amplified before driving the LED. The LED brightness varies with a change in frequency from the oscillator.

An offset adjustment using VR1 allows the LED brightness to be set at a very low level to brighten with non-ferrous metals. The LED can be set at a higher level to detect ferrous metals where the LED begins to dim.

The buffer stage (IC2b) between the offset control and the amplifier is there to ensure there is no gain change with adjustment of potentiometer VR1.

## Circuit details

The full circuit diagram in Fig.2 is based on just two ICs. One is a CMOS version of the 555 timer (IC1) and the


other is a general-purpose LM358 dual op amp (IC2a and IC2b).

IC1 operates as an unconventional astable oscillator. To explain how it works, we will compare it to a conventional 555 astable oscillator, as shown in Fig.3. This has resistor R1 between its output at pin 3 and both the trigger and threshold inputs at pins 2 and 6. Capacitor Cx is connected between pin 2, pin 6 and ground.

Initially, when power is first applied, the capacitor is discharged and the trigger input at pin 2 is at 0V. At this stage, the timer is triggered and the output at pin 3 goes high to equal the positive supply rail voltage.


The capacitor now charges via R1. When the capacitor charges to the pin 6 threshold voltage (2/3 supply), the pin 3 output goes low (to 0V) and the capacitor now discharges via R1. When the capacitor voltage discharges to the trigger level voltage at pin 2 at 1/3 the supply, the pin 3 output goes high again to recharge the Cx capacitor. The process continues, and so pin 3 produces a square wave output with the frequency determined by R1 and Cx.

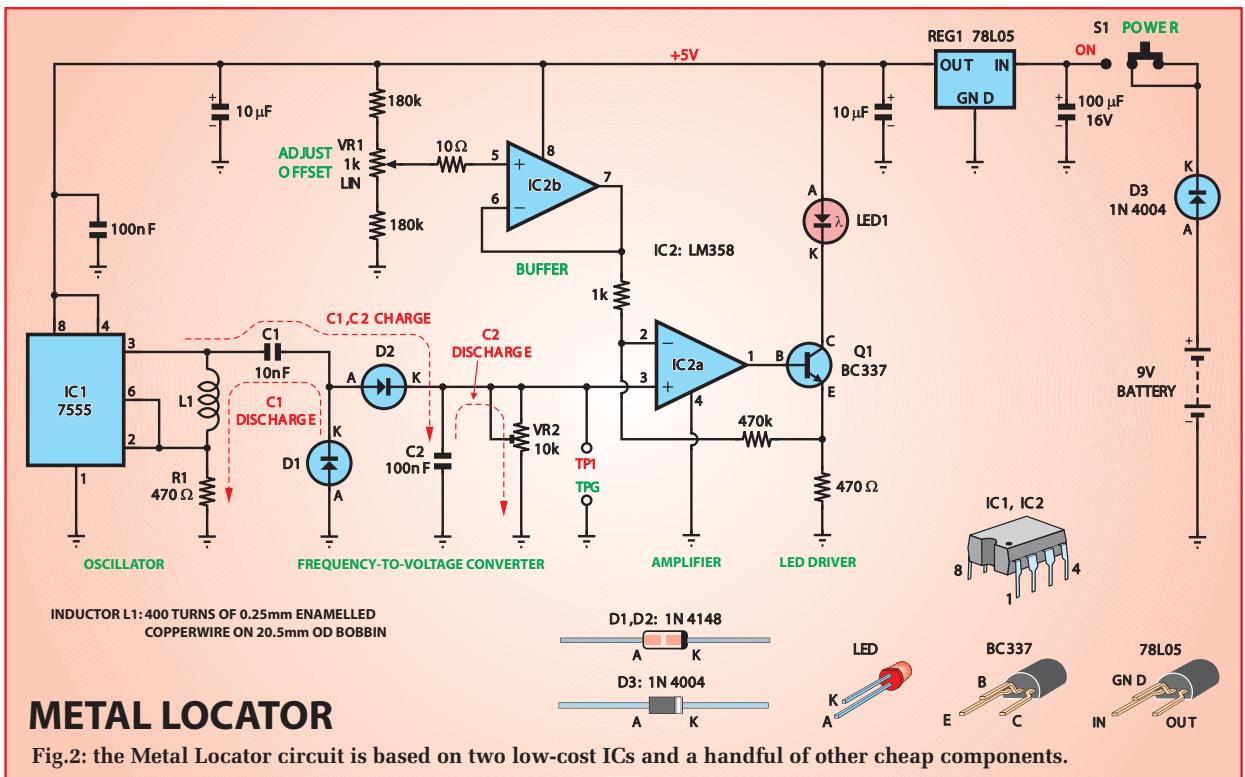In the circuit of Fig.2, we substitute inductor L1 for R1 and R1 (470Ω) for capacitor Cx. It now operates as follows.






## Constructional Project

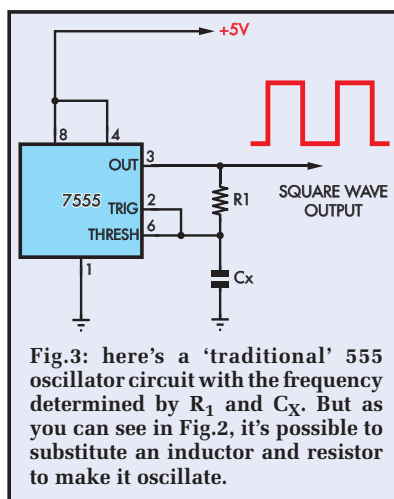

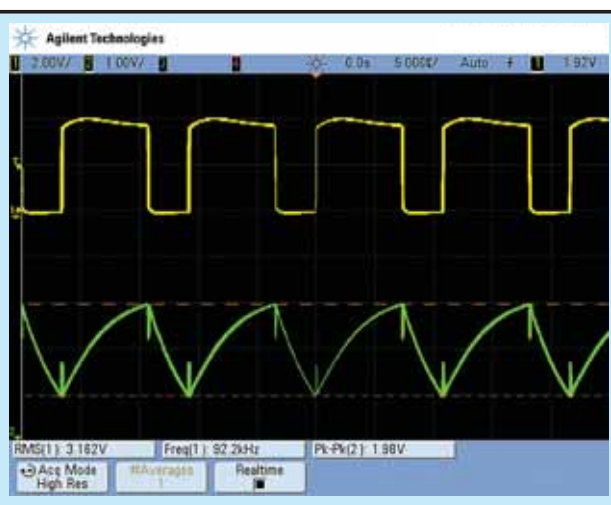And here's the proof! The top trace is the waveform at pin 3, while the green trace shows the waveform at pin 6. The waveform at pin 6 is the voltage across  $R_1$ , and this shows that the current through  $R_1$  does not reverse; it merely varies between about 3.5mA and 7mA. Note the spikes generated each time the 555 changes state.



At the instant of power being applied, inductor  $L_1$  is effectively a high impedance and resistor  $R_1$  pulls the pin 2 input below the 1/3 supply threshold to trigger the pin 3 output to go high.

Current then begins to flow through  $L_1$  and  $R_1$ . As the current rises, the voltage across  $R_1$  increases until it reaches the 2/3 supply voltage threshold. This changes the state of the oscillator so that pin 3 goes low. The current through  $L_1$  does not change direction, but ramps down until the voltage across  $R_1$  drops below the 1/3 supply threshold to retrigger the timer and pin 3 goes high again.

### Oscillator frequency

The frequency is dependent upon the inductance of  $L_1$  and the resistance of

$R_1$  (which is fixed at 470 $\Omega$ ). Inductor  $L_1$  is an air-cored coil of wire. If metal comes close to this coil its inductance will change and this will alter the frequency of oscillation. For ferrous metals, the inductance will increase and the frequency of oscillation will fall. For non-ferrous metal, the inductance will decrease and the oscillation frequency will increase. The frequency is around 94kHz and changes by up to 2kHz with metal near the coil.

The output from IC1 is fed to a diode pump comprising capacitors  $C_1$  and  $C_2$ , preset VR2 and diodes D1 and D2. It functions as a frequency-to-voltage converter by dint of the size of  $C_1$ , which is fairly small at only 10nF. This means that the DC voltage developed

across  $C_2$  will vary as the frequency varies; it will be higher as the frequency increases and this allows the circuit to discriminate between ferrous and non-ferrous metals as the apparent inductance of  $L_1$  is changed.

The DC voltage across  $C_2$  is amplified by op amp IC2a. This has a gain of about 470 (471 to be precise), set by the 1k $\Omega$  and 470k $\Omega$  feedback resistors. IC2a is buffered by transistor Q1 to provide a higher current drive for LED1.

### Offset control

Op amp IC2a has an offset control (VR1) to enable adjustment of the LED brightness. In effect, the operating point of IC2a can be shifted up or down by varying the voltage applied to its inverting input. The varying voltage comes from IC2b, a unity-gain buffer that is fed by the wiper (moving contact) of the 1k $\Omega$  potentiometer VR1. Combined with the 180k $\Omega$  divider resistors, the range amounts to about 14mV.

The buffer stage of IC2b ensures the gain of IC2a is kept at 471 and is not affected by the resistance at the wiper of VR1. Any voltage change in VR1 is amplified in IC2a by 471, so the 14mV variation allows the IC2a output to be shifted over its full output range, from very close to 0V up to about 3.5V.

This adjustment allows the LED to be set at the required brightness for metal detection. In effect, VR1 operates as a sensitivity control for the circuit.

Trimpot VR2 provides a further range of adjustment. For optimum operation of VR1, VR2 is adjusted so the voltage at TP1 is at about half supply, or



## Why Not Use A Stud Finder?

Most readers know that stud finders are cheaply available from hardware outlets and even from bargain stores. They often have three functions: stud, nail and power.

While they are cheap and readily available, they can give misleading results when looking for screws or metal studs in walls.

Nor can they discriminate between ferrous and non-ferrous metals and their sensitivity cannot be adjusted.



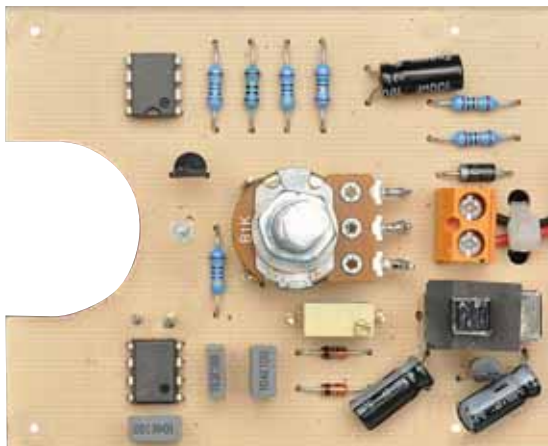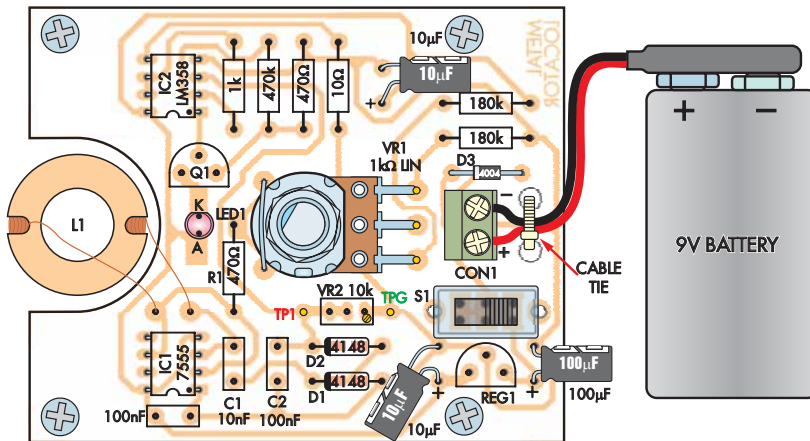

**Fig.4 (top):**  
the component layout for the Metal Locator, with the same-size photo prior to mounting in the case at left. Note the electrolytic capacitors need to be mounted folded over so they are flat on the PC board.

+2.5V. This matches the nominal 2.5V available from the wiper of VR1 at its centre position.

The circuit is powered from 5V, derived from a 9V battery and a 5V regulator (REG1). Diode D3 prevents damage to the 100 $\mu$ F capacitor and the 5V regulator if the battery is connected the wrong way around. The 5V supply is decoupled with a 10 $\mu$ F capacitor at REG1's output and another 10 $\mu$ F

capacitor at the supply rails for IC2. IC1 has a 100nF supply bypass capacitor.

## Construction

Construction involves mounting all parts, except coil L1, on a single PC board. This is coded 810, measures 78mm x 64mm and is housed in a remote control case measuring 135mm x 70mm x 24mm. This board is available from the *EPE PCB Service*.

## Checking Handles: Knives or Screwdrivers

The handles on some kitchen knives are unsafe because they have a very short tang. The Metal Locator can show just how long the metal tang goes into the handle of a kitchen knife or screwdriver. Many professional knives have the tang extending the whole length of the handle, and this tang can be seen running between the two handle sections that are riveted to the outside of the tang.

But some low cost knives only have a tang that enters part way into a plastic moulded handle. They can even have imitation rivets along the handle to give the impression that the tang runs along the whole handle length. A short tang means that if a large amount of stress is applied to the handle when using the knife it is liable to break. This can be dangerous, especially when doing heavy work such as cutting up pumpkins. Make sure you use a knife that is safe for the job.

The component overlay diagram is shown in Fig.4. Begin construction by checking the PC board for shorted tracks or breaks in the copper. Check the hole sizes as well. The corner mounting holes should be 3.5mm (9/64 inch) diameter, as can the two holes to anchor the battery snap leads with the cable tie. Power switch S1 also mounts on the board – before assembly, check that its holes are large enough and if not, enlarge slightly.

Now you can begin the assembly. Install the seven resistors first. We show their colour codes in a table, but it is a good idea to also check the values using a digital multimeter before installing each onto the PC board. Make sure you don't mix up the side-by-side 470Ω and 470kΩ resistors. Doing so may not let any smoke out, but it certainly won't work when completed.

Next, install the five PC solder stakes for VR1, the two stakes to terminate inductor L1 and the two stakes for test points TP1 and TP GND. Install diodes D1 to D3 and take care to orient these correctly. IC1 and IC2 can now be installed, making sure that the 7555 timer is placed in the IC1 position and LM358 in IC2. Each IC must be oriented with the notch as shown on the overlay diagram. You might find some ICs don't have a notch, but will have a small dimple marking pin 1.

Transistor Q1 and voltage regulator REG1 can now be installed, but make sure each is placed correctly, as they look very similar to each other.

Next, LED1 can be installed, again taking care to get the orientation correct. The top of the LED should be 15mm above the PC board. The capacitors can also be installed. The three electrolytic types need to be oriented with the polarity shown, but they also need to lie down to provide clearance in the box – see photo above.

Trimpot VR2 can be installed either way around. Switch S1 is mounted as high as possible on the PC board, but with about 1mm of pin length under the PC board to allow soldering. Screw terminal block CON1 can now be installed.

Cut the shaft of the 1k $\Omega$  potentiometer (VR1) to a length of 12mm. VR1 sits vertically with its back on the PC board surface and is secured in place by soldering the potentiometer case to the associated PC stakes. To be certain solder will adhere to the surface, the



# Constructional Project

## Parts List – Metal Locator

- 1 PC board, code 810, available from the *EPE PCB Service*, size 78mm × 64mm
- 1 remote control case 135mm × 70mm × 24mm (Jaycar HB 5610 or equivalent)
- 1 front panel label 50mm × 115mm
- 1 9V battery, with clip and leads
- 1 DPDT PC mount slider switch (S1)
- 1 coil bobbin 20.5mm OD × 13mm ID × 10.5mm high
- 1 13m length of 0.25mm enamelled copper wire
- 1 knob to suit potentiometer
- 1 2-way screw terminal with 5.08mm pin spacing
- 4 T0-220 insulating bushes (used as spacers)
- 4 M3 × 4mm screws
- 1 20mm diameter × 12mm heat-shrink tubing
- 1 100mm cable tie
- 9 PC stakes

### Semiconductors

- 1 7555, LMC555CN CMOS timer (IC1)
- 1 LM358 dual op amp (IC2)
- 1 78L05 three terminal 5V low-power regulator (REG1)
- 1 BC337 NPN transistor (Q1)
- 1 1N4004 1A diode (D3)
- 2 1N4148 signal diodes (D1,D2)
- 1 3mm high brightness red LED (LED1)

### Capacitors

- 1 100µF 16V PC electrolytic
- 2 10µF 16V PC electrolytic
- 2 100nF MKT polyester
- 1 10nF MKT polyester

### Resistors (1% 0.25W)

- 1 470kΩ      2 180kΩ      1 1kΩ
- 2 470Ω      1 10Ω
- 1 1kΩ linear 16mm potentiometer (VR1)
- 1 10kΩ 25-turn top-adjust trimpot (3296W type) (VR2)




Here's the completed PC board screwed into the plastic 'remote control' case. The coil is not attached to the PC board – it is glued in place to the case in the cutout provided in the PC board.

passivated coating on the pot case must be removed by scraping with a knife or file where the PC stakes are positioned. The potentiometer terminals are soldered to the remaining three PC stakes.

The 9V battery leads pass through one of the battery compartment holes in the plastic case before inserting them into the screw terminals. A cable tie secures the wires in position.

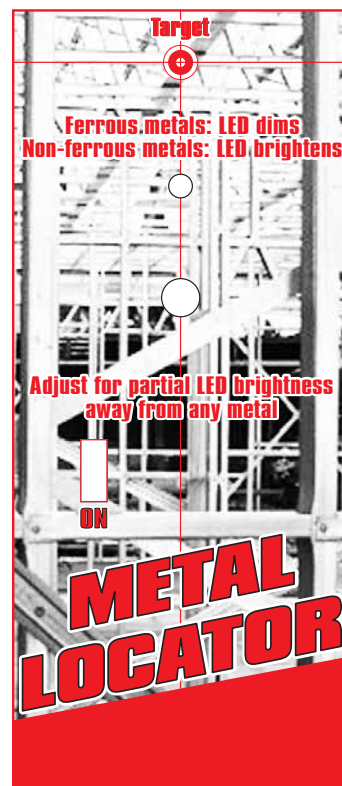The PC board is raised by about 1mm by placing a TO-220 bush into each mounting hole from the underside of the PC board. This raises the PC board sufficiently so that the



This full-size front panel artwork fits into the recess on the top of the remote control case.

switch slider is above the top of the case lid.

Secure the PC board to the case with four M3 screws that go into the integral support bushes of the case.

### Winding the inductor

Inductor L1 is wound with 400 turns of 0.25mm enamelled copper wire on a plastic bobbin. The windings are jumble wound. This means windings do not have to be placed neatly side-by-side, layer-by-layer.

The winding is held in place with a 12mm length of 20mm heatshrink tubing over the outside of the bobbin. There is no need to shrink the tubing down.

The bobbin is secured to the base of the case in the cut-out area reserved for it at the front of the PC board. We used silicone sealant to glue the bobbin in place.

Scrape off the enamel coating on each wire end with some fine grade abrasive paper and then solder them to the two PC stake terminals – it doesn't matter which way around.

**Table 1: Resistor Colour Codes**

No.	Value	4-Band Code (1%)	5-Band Code (1%)
1	470kΩ	yellow violet yellow brown	yellow violet black orange brown
2	180kΩ	brown grey yellow brown	brown grey black orange brown
1	1kΩ	brown black red brown	brown black black brown brown
2	470Ω	yellow violet brown brown	yellow violet black black brown
1	10Ω	brown black black brown	brown black black gold brown





A close-up of the coil (L1). It's about 400 turns of wire on a plastic bobbin.

### Test and set-up

Apply power and check that there is 5V between TP GND and pin 4 and pin 8 of IC1, and 5V between TP GND and pin 8 of IC2. Depending on the regulator, the voltage could be anywhere between 4.85 and 5.15V.

Connect your multimeter between TP GND and TP1 and adjust trimpot VR2 for a reading of about 2.5V. Now set VR1 to its centre position and adjust VR2 until the LED just lights.

### Using it

When the Metal Locator is first switched on and the LED is adjusted so that it glows dimly, there is a start up drift over about 10 seconds. During this period, the adjustment will have to be altered to track the change in LED brightness. It is best to wait for the warm up period before using the Metal Locator.

The sensitive area is directly under the target printed on the top side of the case (which, of course, lines up with the middle of coil L1). So, for detecting metal in a plaster wall, the case is slid over the wall to detect a change in the LED brightness.

The adjust knob will need to be set to show some LED brightness in the absence of metal objects. The sensitivity to metal is dependent on this adjustment.

If the LED brightness is set too high then there will not be a noticeable change in brightness with the unit in proximity to a metallic object.

The LED will dim for ferrous and brighten for non-ferrous metals. **EPE**

Reproduced by arrangement  
with SILICON CHIP  
magazine 2011.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)

THE NEW PICOSCOPE 3000 SERIES




pico  
Technology

## PicoScope® 3000 Series

THE HIGHEST-PERFORMANCE USB-POWERED OSCILLOSCOPES AVAILABLE

Power and portability. Why compromise?

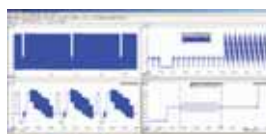200 MHz bandwidth  
HUGE 128 MS buffer size  
500 MS/s real-time sampling  
10 GS/s repetitive sampling  
Advanced digital triggers  
200 MHz spectrum analyzer  
Built-in function generator/AWG  
USB-connected and powered




128 MSample buffer  
memory



Serial decoding



200 MHz spectrum  
analyzer

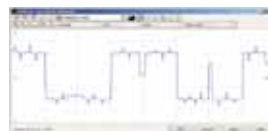

Arbitrary waveform  
generator

High-end features as standard. Why compromise?

Serial decoding Mask limit testing Segmented memory

[www.picotech.com/scope3108](http://www.picotech.com/scope3108)

# The electronics of earthquakes

## TechnoTalk

Mark Nelson

**The law of unexpected consequences certainly applies to earthquakes. Mark reports on some of the odd discoveries following the disastrous seismic activity in New Zealand.**

**H**ERE in Britain, we can feel grateful that we do not suffer the kind of dreadful earthquakes and tsunamis that New Zealand and Japan have been suffering. Actually, we do, but they occur extremely infrequently and on a smaller scale. Nevertheless, in January 1607, the land around the Bristol Channel was inundated by what Prof. Simon Haslett of Bath Spa University states was a tsunami.

Accounts tell of 'huge and mighty hills of water' advancing 'faster than a greyhound can run' that swept away villages and drowned more than 2000 people. The book *Earthquake in England* by John Thomas records numerous historical earthquakes in Britain too, including one in 1938 that even rocked Broadcasting House in London and the television tower at Alexandra Palace.

### Humour in Christchurch

Last September's earthquake in New Zealand was the most damaging in 80 years and many home and business owners have had to come to terms with the fact that there will be no compensation for 'loss of value', and it may not be possible to insure new buildings. Rent and mortgages still have to be paid on useless buildings.

Our practical electronicist in Christchurch has retained his sense of humour and reports that a woman, who thought she was doing the right thing, rang her electric power supplier to disconnect the supply because she thought it might be hazardous. She was told that they would have to read the meter and that there would be a \$40 charge.

No problem with that she told them, although she was a bit put out by having to pay for a meter reading. 'You'll find the meter under a ton of rubble.'

### Spooky stuff

Our New Zealand friend continues that several people reported seeing blue or blue-green lights in the sky shortly before the quake struck. A National Geographic television programme aired earlier this year stated that lights in the sky were reported before the big Kobe earthquake of 1995 – the biggest to hit Japan for 47 years – and have also been reported in Peru prior to large quakes.

Here we move into one of the strangest and more controversial electronic phenomena. The popular name for these apparitions is 'earth

(or earthquake) lights', which are seemingly electromagnetic. Observed only by night and close to the ground, they take on glowing, polymorphous forms, the result of seismic pressures associated with the constantly rising and falling tectonic stress in the earth's crust, creating plasma electricity above the ground.

It has to be admitted that earth lights are a fringe science, rather like UFOs, and attract a lot of interest from non-scientific people who revel in the mysterious and unexplained. The International Earthlight Alliance (IEA) is an organisation of technical professionals (scientists and engineers) who are dedicated to the scientific investigation of earth lights. Their website explains that glowing balls of light have been reported far back into history.

Until recently, stories and observations of lights from all over the world were considered superstitious lore, scientists writing them off. In the last 25 years, however, the development of high speed film and low-light digital photography have enabled observers to document the existence of these glowing lights as a valid physical phenomenon.

### How they work

What is it that causes the air to glow at certain locations? Does it require a large amount of energy either below or above the ground? Could this energy be harnessed as an alternative energy source? Could a better understanding of the mechanism of the lights give an insight into earthquake forecasting?

It's hard to tell, but some sightings obviously have explainable causes, such as vehicle or aircraft lights, fires and marsh gas. One of the most plausible explanations suggests the lights come from strain building up in the earth's crust through various processes, such as tectonic activity, tidal action and human activity, dams and reservoirs.

Dr. Michael Persinger and Dr. John Derr have both hypothesised that strain fields within the earth's crust may produce electromagnetic discharges that can manifest by becoming visible as a moving body of light. The geophysicist Marsha Adams has observed fluctuations in extremely low frequency (ELF) electromagnetic emissions prior to earthquakes.

Reports of light observations have been made over a large radius from the epicentre of large earthquakes before they occur, although not in all seismically active areas. Moreover, these lights are also seen in areas of low seismic activity, meaning that the strain theory is not a universal explanation.

### Another theory

Volcanic activity is at the root of another explanation. Many observations of earth lights have been made around volcanoes, for instance in Mexico. It is suggested that ultra low frequency (ULF) electromagnetic waves may trigger a process that causes light.

Significant anomalous changes in the ULF range (around 0.01Hz) have been recorded in both geoelectric and geomagnetic fields before major volcano-seismic activity. One hypothesis is that these anomalous electromagnetic discharges may trigger a process that causes a visible moving body of light, similar to the tectonic strain theory.

### Earth lights in the UK

Do earth lights occur in the UK? Paul Devereux, who coined the term in 1982, is convinced they do. In an article he cites numerous historical reports, although the majority appear to relate to marsh gas or ball lightning. On the other hand, Harlech (which is adjacent to one of Britain's most active seismic zones) was, in 1984, the epicentre of a significant earthquake that measured 5.5 on the Richter scale.

A resident told Devereux that he saw, the evening before the quake, a brilliant white light the size of a small car float in from the sea and dissolve in sand dunes. Other reports from Harlech are recounted in the online article.

Unfortunately there appear to be few opportunities for electronics enthusiasts to record, let alone observe, earth lights, but the underlying theory is a fascinating subject to follow.

### Further reading

- Wikipedia article: [http://en.wikipedia.org/wiki/Earthquake\\_light](http://en.wikipedia.org/wiki/Earthquake_light)
- International Earthlight Alliance: [www.earthlights.org](http://www.earthlights.org)
- Paul Devereux's article: [www.forteanimes.com/features/articles/58/unidentified\\_atmospheric\\_phenomena.html](http://www.forteanimes.com/features/articles/58/unidentified_atmospheric_phenomena.html)

# JOIN THE FUN!

## Visual TFT software

Bringing together worlds of design and programming, this software will start a small revolution in ways we build TFT GUIs. Just **focus on design**, and let the software write the code for you.


## MULTIMEDIA BOARDS

New line of multimedia boards can really **get your creativity sparks going**. You can build all sorts of cool applications that come to your mind. They are ready to meet your demands. They are supported in **Visual TFT software**, so you can **easily build great GUIs** for your applications or games in minutes, and **have lots of fun** along the way.



**mikroMMB  
for PIC18FJ**

price:  
**\$99**

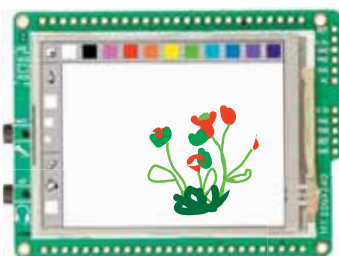

**mikroMMB  
for PIC32**



**mikroMMB  
for PIC24**

## COMPILERS

**VisualTFT software** and **Multimedia boards** are best supported with mikroElektronika compilers: **mikroC**, **mikroBasic**, and **mikroPascal**. Having intuitive and fast IDE, powerful compilers and lots of tools, you'll really feel great spending your time programming. **Lots of libraries and examples**, comprehensive help file and **free product lifetime tech support** ensure that you get the job done quickly.



**\$199**



**\$149**



**\$149**



# LOOP ANTENNA AND AMPLIFIER

## for long-distance AM radio reception

Design by Branko Justic\*  
Words by Ross Tester

- Listen in to AM radio stations you only dreamed existed!
- Separate close stations
- Suits upper AM broadcast band
- Small enough for flats and home units

\* Oatley Electronics



**O**NCE upon a time, listening to long-distance radio signals (whether on the broadcast or shortwave bands, or even the amateur bands) was a popular hobby.

Hours upon hours were spent, listening for that elusive station... the ability to bring very weak stations 'out of the mud' was the ultimate thrill.

In the 21<sup>st</sup> century (and at the risk of earning the ire of diehard shortwave listeners) those days have all but gone. Today, there is little interest in the big, high-performance communications receivers of last century. A lot of gear came out of WWII, perhaps modified, but there was also an enormous amount of commercial receiver equipment on the market, reflecting the popularity of 'listening'.

Who can forget (if you were around 50 years ago) the Marconis, Hallicrafters or Gecos, the Nationals, Eddystones, Collinses or the build-it-yourself Heathkits?

Those who still indulge in the art of 'listening' are these days just as likely to use WinRadio in/on their PCs – which in many ways outperforms even the best of the communications receivers of yore.

In fact, the vast majority of receivers today have little more than the AM and FM broadcast bands.

### The aerial

There are three things which make a receiver 'good'. Two are fixed (at the whim of the designer or manufacturer).

First, the receiver's sensitivity, which is its ability to resolve very weak stations. Second, the receiver's selectivity, which is its ability to separate stations whose transmit frequencies are very close. Note that NO receiver, on its own, can separate stations which are on the same frequency.

However, the third factor, which can often help a receiver distinguish between stations on adjacent frequencies (and even sometimes the same frequency) is the aerial or antenna.

Even though the terms are virtually interchangeable these days, no self-respecting old-timer would ever call his aerial an antenna. Antennas were those small flimsy things designed to pick up TV!

### Black art

Unless you have made an in-depth study of aerial/antenna theory, most



Here's the top PC board mounted inside a low-cost weatherproof case. The two cables entering at left are for the loop antenna above (you can just see the loops behind the case lid). All four wires in this cable are soldered to the underside of the board together. The cable entering in the middle is the downlink – this cable has all four wires individually soldered to the underside of the PC board.

people (many electronics hobbyists included) view it as a 'black art'.

Sure, everyone knows aerials/antennas are the 'inductor' part of a tuned circuit which, depending on the antenna length, resonates at a particular frequency, according to the formula:  $1/2\pi\sqrt{LC}$  where  $L$  is the inductance in henries and  $C$  is the capacitance in farads.

Wanted frequencies (ie, the station you want to listen to) can pass virtually unhindered, but (at least theoretically) all other frequencies are rejected.

If you make the frequency of the tuned circuit variable, then you have a means of tuning over a specific band of frequencies.

Well, at least that's the way it's supposed to work. Old timers will tell you they used to use another aerial formula: 'as long and as high as possible'. You'd see many a length of wire stretched on poles 'down the backyard' – or further. But not everyone these days has the room (or the neighbours) to allow this to happen. You need something smaller.

# Constructional Project

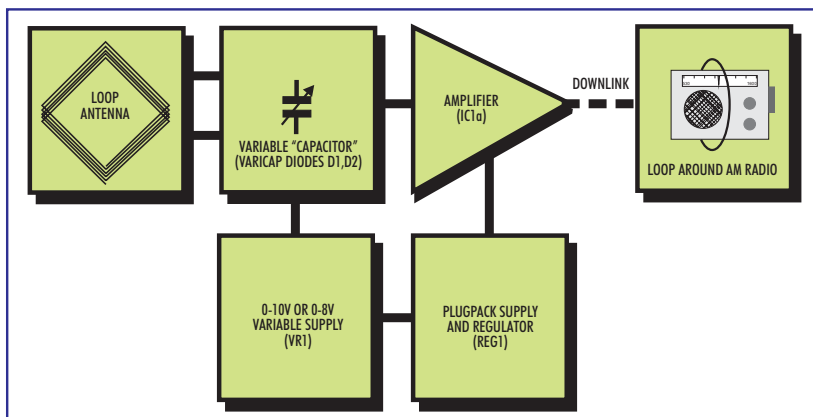


Fig.1: block diagram of the Active AM Loop Antenna. The first two blocks are connected in parallel to form a tuned circuit.

## Back to the future

This project is specifically intended for those who want to listen to distant, weak or interference-prone AM radio stations, particularly those in the upper portion of the band. This tends to be where the weaker stations are located – most country commercial AM stations are about 2kW; some are even less. Compare that with city commercial stations or national broadcasting, which can be up to about 50kW.

We mentioned before that the aerial/antenna (let's standardise on the word

'antenna') can make a great deal of difference to the performance of a receiver.

Modern receivers are often quite reasonable in the selectivity and sensitivity department, so all that's left for us to play with is the antenna. Even if the receiver has provision for an external antenna and earth, you might be quite disappointed with the performance. That's because a random-length antenna is unlikely to be impedance-matched to the receiver and unlikely to be resonating anywhere near the required frequencies.

## Loop antenna

A far better approach is to use the one we've gone for here – a loop antenna with an in-built amplifier. Moreover, a loop antenna exhibits reasonably good directivity – if you're trying to pick up a distant station and another station is swamping it, you can rotate the loop to 'null out' the unwanted one.


Coupling the loop antenna to the receiver is made simple because no physical connection is required. A second, single-turn loop couples the signal into the radio's in-built ferrite rod antenna. The distance between the loop antenna and the receiver can usually be as much as you require – up to several tens of metres, in fact.

**Note: this project will NOT work on any AM radio which does not have an in-built ferrite rod antenna – this is the only way the received signal is coupled to the radio.**

## How it works

Take a look now at the block diagram (Fig.1). It shows the operation of the loop antenna.

Countless electromagnetic waves passing through the wire loops – generated by anything from lightning to electric motors to radio and television

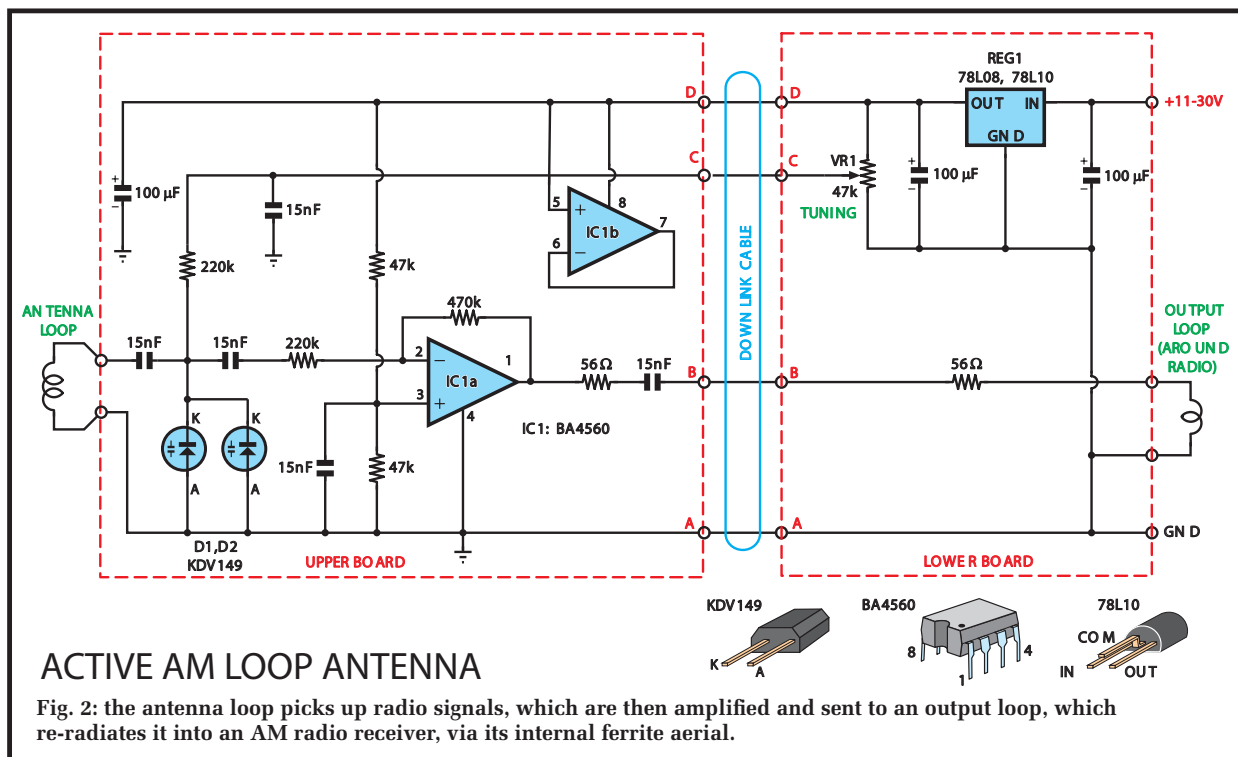



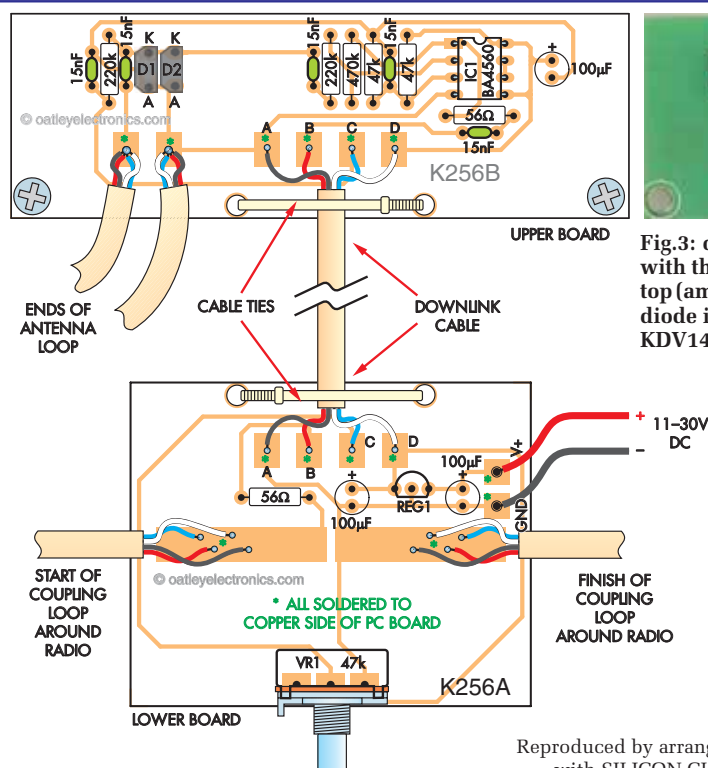


Fig.3: component overlays for the top and bottom PC boards, with their same-size photos alongside. Note that the prototype top (amplifier) board shown here used a single SR1060 Schottky diode in the tuning circuit, whereas the final version uses two KDV149 varicap diodes in parallel.



Reproduced by arrangement  
with SILICON CHIP  
magazine 2011.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)

stations – induce tiny electric currents at numerous frequencies.

The tuned circuit, consisting of X-frame-mounted coil loops, in parallel with a variable capacitance (we'll explain how this is achieved in a moment), effectively filters out almost all of these currents, except for the ones which correspond to the resonant frequency. The resulting narrow band of signals is then fed into an amplifier, based on op amp IC1a.

The amplified signals are then fed to another coil, this one designed to wrap around the AM receiver. This loop re-radiates the signal so that the ferrite rod aerial coil inside the radio can receive it again and process the signal, just as it would any other radio signal it receives.

What we are doing, therefore, is essentially 'preconditioning' the signal, so that the radio itself doesn't have to try hard to extract the wanted signal.

Remember those three things we mentioned earlier which determine a receiver's performance? Well, this circuit not only boosts the signal level, making the receiver more sensitive to

weak signals, but also adds another stage of filtering, making the receiver more selective. As a result, the performance must be better – and in fact can be markedly better!

To keep interference to a minimum, the X-frame loop antenna itself should be mounted outside the home, well away from motors, switches or other sources of interference.

## Variable tuned circuit

As you probably know, you can make a tuned circuit's basic frequency variable by varying either the inductance or capacitance (remember that formula earlier?).

In general, it's a lot easier to adjust the capacitance, although many multi-band radio receivers do change coils (inductance) when switching bands.

We could use a small variable tuning capacitor, but these are not only hard to get, they're also getting rather expensive. The miniature ones commonly sold these days are incredibly fiddly to use and not at all conducive to tracking down weak radio signals!

But there is another way to obtain a variable 'capacitor'. Many semiconductors exhibit a change in capacitance when the voltage across them is changed. Varicap diodes are one such device, and in this circuit, we have

## Modifications and an alternative antenna configuration

The original circuit (developed by Oatley Electronics) used a single SR1060 Schottky diode as the variable capacitance diode, and this covered just the 900kHz to 1600kHz end of the broadcast band. This device is shown in the photos, but was subsequently replaced by two KDV149 varicap diodes, enabling the entire broadcast band to be covered.

Note, if you don't want to build a large wooden antenna mast, you can achieve similar results by winding 10 turns of wire (spaced about 10mm apart) on a plastic hobby storage box (or crate) measuring about 350 × 350 × 260mm deep

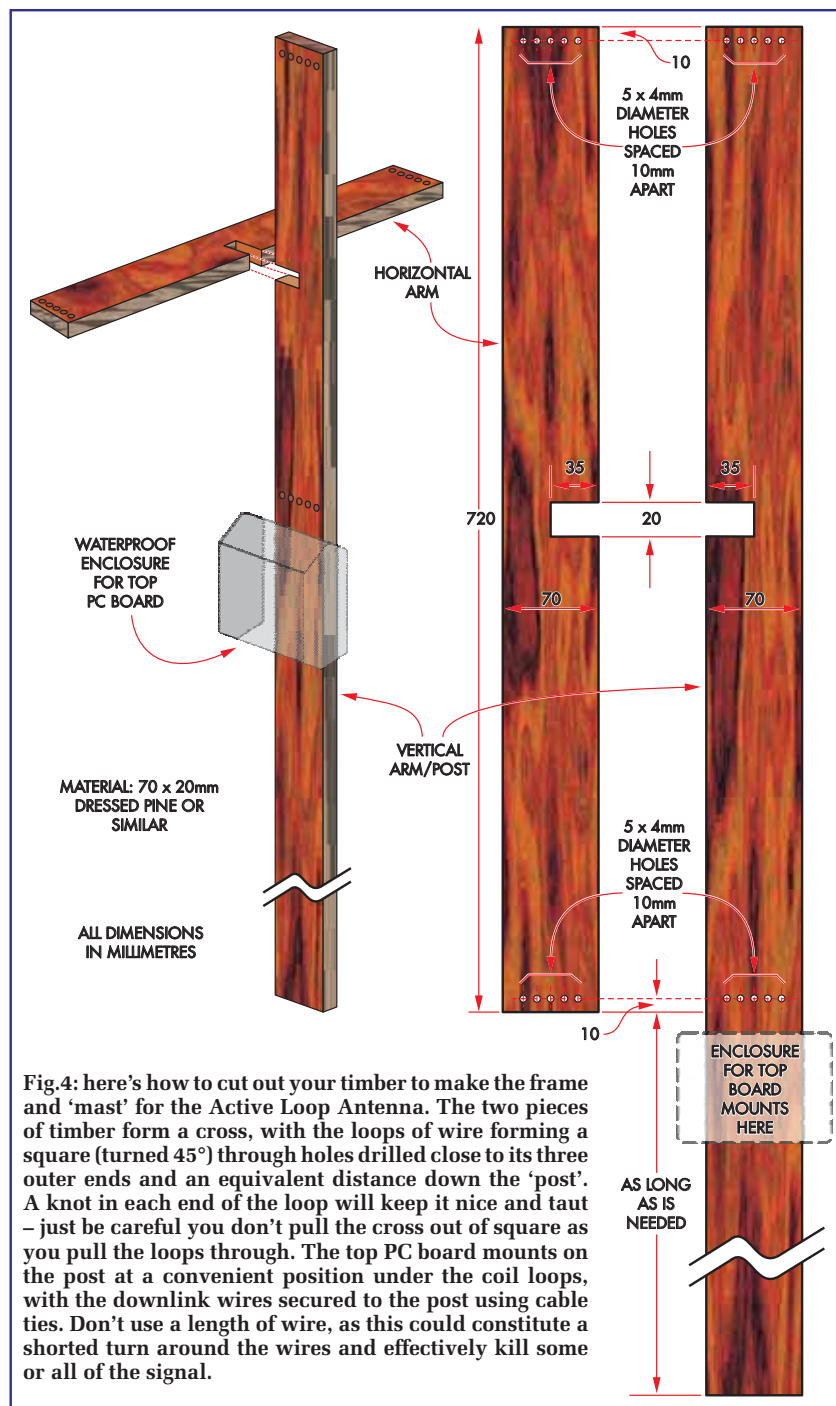


Fig.4: here's how to cut out your timber to make the frame and 'mast' for the Active Loop Antenna. The two pieces of timber form a cross, with the loops of wire forming a square (turned 45°) through holes drilled close to its three outer ends and an equivalent distance down the 'post'. A knot in each end of the loop will keep it nice and taut – just be careful you don't pull the cross out of square as you pull the loops through. The top PC board mounts on the post at a convenient position under the coil loops, with the downlink wires secured to the post using cable ties. Don't use a length of wire, as this could constitute a shorted turn around the wires and effectively kill some or all of the signal.

used two such diodes in parallel to achieve the required tuning range (ie, right across the AM broadcast band).

## Circuit details

The complete circuit diagram for the *Active AM Loop Antenna* is shown in Fig.2.

The supply voltage for this project can be quite wide – from about 11V to

30V DC. A nominal 12V plugpack, for example, will usually give about 16V to 18V unloaded and would be fine.

This voltage is regulated to either 8V or 10V DC by REG1, depending on the regulator used (either a 78L08 or a 78L10). The resulting power rail supplies the amplifier IC directly and is also fed to a 47kΩ potentiometer (VR1). VR1's wiper (moving contact) is

in turn connected to the cathodes (K) of the paralleled varicap diodes (D1 and D2) via a 220kΩ resistor.

At the top of its travel, the wiper will have the full 8V or 10V connected to the varicap diodes, while at the bottom, it will, of course, be near enough to 0V.

The antenna coil is coupled into the varicap diodes via a 15nF capacitor. This prevents the DC voltage, which is applied to the varicap diodes, from being shorted to ground via the quite low resistance of the antenna coil.

Similarly, the output from the tuned circuit is coupled to the input of op amp IC1a via another 15nF capacitor, so it cannot introduce DC into the amplifier circuit.

Finally, we should point out that only one of the two op amps in the BA4560 package is used. The other has one of its inputs connected to the positive supply and its other input to its output to ensure that it doesn't become unstable.

## Construction

There are three parts to the construction of this project – two PC boards, plus the 'X'-shaped timber antenna support that houses the turns of telephone cable forming the antenna.

On one board, we have the amplifier section and the terminations for the loop antenna. The second board carries the power supply plus the connections for the loop to place around the AM radio receiver. Between the two boards is the downlink wiring.

Start construction by making your timber 'X' frame, using Fig.4 as a guide. You can use just about any scrap timber that you can find (but we wouldn't use Pyneboard or other composites if the antenna is to be erected out in the weather). Any timber used should have generous coatings of paint applied to weatherproof it.

Don't forget to drill all the holes for the 4-core telephone cable (antenna loop) before you glue and screw the sections together – it's a lot easier to drill flat timber!

Wind the five turns for the coil through the holes, starting with an outside hole closest to where the top PC board will be mounted – leave yourself about 200mm or so of cable to work with past the position where the PC board goes. Tie a single-loop knot in the cable as it passes through the first hole.

## Parts List – Active Loop Antenna

- \*1 PC board, code 813 (Ant Loop) 31mm × 94mm
- \*1 PC board, code 814 (Rad Loop) 58mm × 48mm
- 1 Weatherproof plastic box (eg Oatley HB4)
- 1 30 × 54 × 83mm plastic box
- 1 8-pin IC socket
- \* Available from the *EPE PCB Service*

### Semiconductors

- 1 BA4560 dual op amp (IC1)
- 1 78L08 or 78L10 voltage regulator (REG1)
- \*2 KDV149 varicap diodes (D1, D2)

### Capacitors

- 3 100µF 16V electrolytic
- 5 15nF disc ceramic

### Resistors (0.25W 5%)

- 1 470kΩ (code yellow purple yellow gold)
- 2 220kΩ (code red red yellow gold)
- 2 47kΩ (code yellow purple orange gold)
- 2 56Ω (code green blue black gold)
- 1 47kΩ linear potentiometer (and knob to suit).

**Miscellaneous** (not included in Oatley Electronics kit)  
Timber, screws and mounting hardware as required  
40m of 4-wire telephone cable or equivalent

Continue to pass the cable through the other three outside holes, then the next across, and so on until the coil is complete. As you go, keep the turns of the coil nice and taut but not so taut as to pull the timber out of the 'X' shape.

When completed, tie a single-loop knot in the last hole so that it keeps the wire loops taut. Again, leave yourself 200mm or so of cable underneath where the PC board will mount, and then cut the remainder off. Hang onto that – you'll need it shortly for the downlink!

### PC board construction

The printed circuit boards component layouts and interwiring are shown in Fig.3. These two boards (together with two Varicaps) are available as a pair from the *EPE PCB Service*, codes 813 (Ant Loop) and 814 (Radio Coupling).

It doesn't matter which board you start with – both are quite simple and should only take an hour or so to complete. On the loop antenna board, the only polarised components are the amplifier IC, the electrolytic capacitor alongside it and the varicap diodes.

Start by installing the smallest components – the resistors and non-polarised capacitors, then install the semiconductors and the electrolytic capacitor. Don't worry about the loop or downlink wiring at the moment.

On the power supply board, three of the five components are polarised, so make sure you get them in the right way. The potentiometer will only go in one way (otherwise the shaft points inwards).

### Loop and downlink wiring

In the prototype, 4-wire telephone cable was used because this happened to be on hand – even though the loop antenna does not use the four individual wires (however, the downlink does).

Therefore you could just as easily use single-conductor wire for the loop if you wished. Note that telephone cable is quite a lot tougher than single

wire and so offers some protection from, for example, birds sitting on it or even pecking at it!

If you use telephone cable for the loop antenna wiring, simply connect all four wires in parallel as you solder them to the PC board. The same applies for the output loop – the one which goes around your radio. The wires can be twisted together to make this easier. Note that all connecting wires solder to the pads on the underside of the PC board.

You might be wondering why each single wire of the telephone cable was not connected in series with its mate and terminated as such on the PC board. Wouldn't this create a significantly greater inductance (ie, four times greater)?

Oatley Electronics originally had exactly the same idea. Unfortunately, when they tried it out, they found that the capacitance of the closely-spaced wires within the cable started to create its own problems.

They found that by paralleling all four wires in the cable, this problem was eliminated. More importantly, they found that the overall performance of the antenna was better!

In the downlink, all four wires in the telephone cable are used independently and are connected to the

points A, B, C and D on the PC boards.

With coloured wiring in the cable (black, red, blue and white), it's not easy to get it wrong!

This downlink wiring can be quite long – the prototype had 20m between the two PC boards, and there didn't appear to be any loss of signal compared to a 5m separation. If you need more distance, give it a go – you have nothing (except signal) to lose.

### In use

If possible, make a complete turn around the radio receiver with the output loop (remember, the radio *must* have a ferrite rod for this antenna to work). How do you know if it has a ferrite rod antenna? If you can turn it on and it works without anything connected, it's a pretty fair bet that it has one. Virtually all small AM radios have a ferrite rod antenna inside.

Tune the radio to the weak station you want to listen to. Now adjust the potentiometer slowly – at one point, you should find a significant increase in the level of that station (or a decrease in any other stations that are interfering with it).

Also, recall what we said before about the antenna being able to turn so that it faces the wanted station – by facing, we mean broadside on, or if you take a line across the X frame the wanted station should be perpendicular to that line.

The antenna will work equally well from both sides. However, if you turn the antenna through 90°, you should find that its performance decreases significantly. Conversely, any other stations that are now broadside-on will be much better.

*EPE*

### WHERE FROM, HOW MUCH?


This project was designed by Oatley Electronics who retain the copyright. A kit for this project (K256), which includes both PC boards, on-board components and cases (as listed above) is available from Oatley Electronics, for about £15. The kit does not include the 4-wire telephone cable nor any timber or mounting hardware. Contact Oatley Electronics via their website: [www.oatleyelectronics.com](http://www.oatleyelectronics.com)





By JIM ROWE

# A Beam-Break Flash Trigger

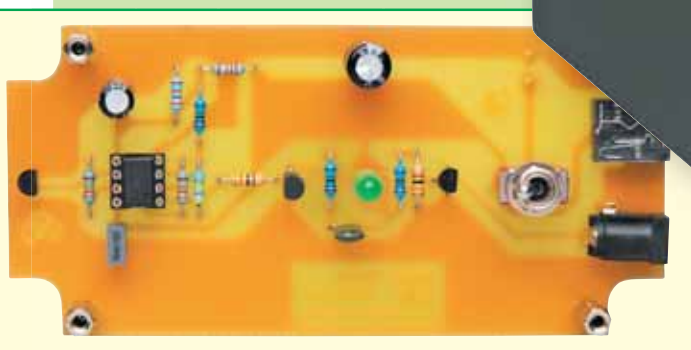

Here's an easy-to-build accessory for the Time Delay Photoflash Trigger described in our February 2011 issue. It triggers the delay unit and your photoflash in response to an object interrupting an invisible beam of infrared (IR) light. Alternatively, it can be used on its own to directly trigger a photoflash.

**A** FEW months ago (in February 2011), we described a *Time Delay Photoflash Trigger*. This unit was triggered by a sudden sound picked up by an electret microphone insert. It then immediately opened the camera's shutter and then fired the photoflash shortly after, depending on the delay period programmed into the unit.

Using sound pick-up in this manner is a popular and effective method of triggering a flash for 'stop motion' and other kinds of special effects photography. However, in addition to the electret mic input, we also gave the delay unit a second 'contact closure' input, so that it could be triggered using other techniques. Which was just as well, because as soon as the delay unit was

published, we started getting requests for a light beam trigger.

### Flash trigger


This simple *Beam-Break Flash Trigger* is the result of those requests. It's mainly intended as an alternative triggering front-end for the Time Delay Photoflash Trigger and is connected to the latter's 'contacts' input. However, it can also be used to trigger a photoflash unit directly if you don't need the programmable time delay capabilities.

Note, however, that using the unit to directly trigger the flash has one important limitation. Unlike the Time Delay Photoflash Trigger, it doesn't also trigger the shutter. This means that you have to open the shutter manually before the

infrared beam is interrupted (eg, at night or in a darkened studio).

This new project is in two parts: (1) an IR Source unit, which produces the IR beam and (2) a Detector unit, which monitors the IR beam and closes its output trigger contacts briefly if the beam is interrupted. These two units are linked with an interconnecting cable, which supplies the Source unit with power.

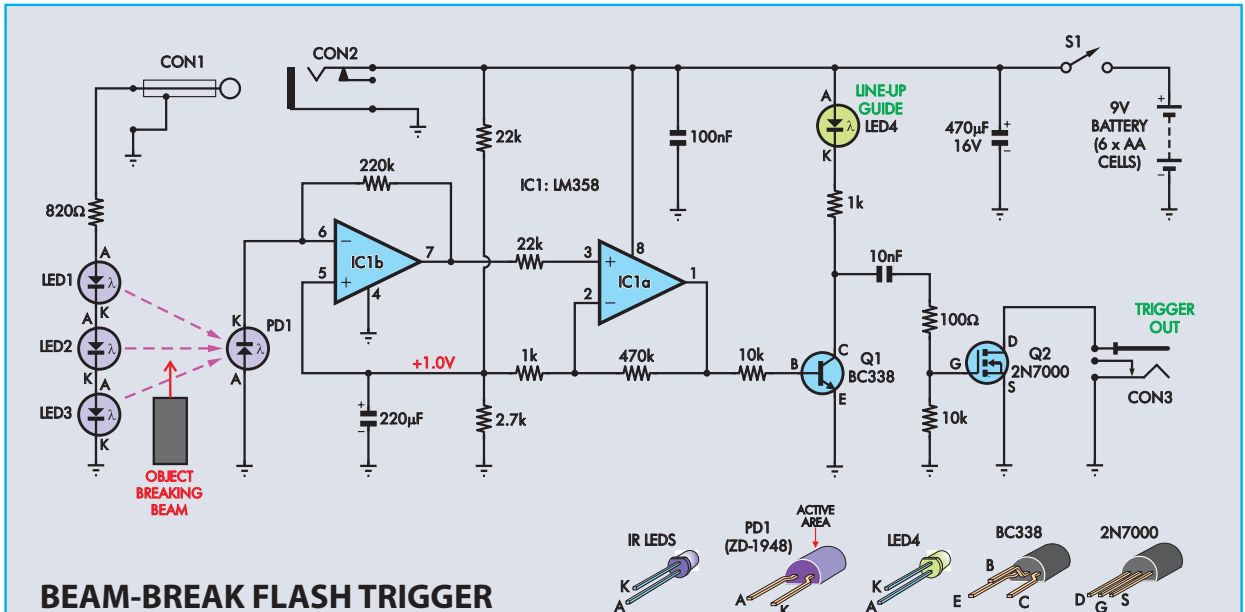If you're already wondering how you accurately line up the Source and Detector units when the IR light beam is invisible to the human eye, wonder no more. That problem has been solved by providing the detector unit with a visible green LED, which lights when the IR beam is being received. This makes the lining-up process easy.



## BEAM-BREAK FLASH TRIGGER

Fig.1: the infrared beam is generated by LED1 to LED3 and picked up by photodetector diode PD1. Op amp IC1b functions as a current-to-voltage converter, while IC1a is wired as a non-inverting amplifier. The latter drives transistor Q1 and MOSFET Q2 to briefly switch the trigger output when the IR beam is interrupted.

Both parts of the project run from a 9V battery fitted inside the Detector unit's box. The total current drain is about 15mA, which means that the battery should be either a set of six AA (1.5V) alkaline cells or a single high-energy 9V lithium battery. A standard 9V zinc-carbon or alkaline battery is not up to the job, as its life would be too short.

### Circuit details

The complete circuit diagram for the *Beam-Break Flash Trigger* is shown in Fig.1. There's really not a great deal in either part of the circuit. In fact, the IR Source unit is nothing more than three IR LEDs connected in series, plus an 820Ω series resistor. This resistor limits the current from the 9V supply (and thus the current through the IR LEDs) to about 7.5mA.

Power is derived from the battery in the Detector unit via a cable fitted with a 3.5mm jack plug (CON1). This mates with CON2 on the detector unit.

In the Detector unit, the IR beam from the Source unit normally falls on PD1, an IR photodetector diode. This photodetector is connected between ground and the inverting input (pin 6) of op amp IC1b (an LM358).

Op amp IC1b is connected as a current-to-voltage converter. Its pin 7

output sits somewhere between +1.7V and +4.0V when the IR beam is present, but rests close to +1.0V when no IR light is falling on PD1. This 'dark' output voltage of +1.0V is basically set by the voltage divider formed by the 22kΩ and 2.7kΩ resistors, with the 220μF capacitor providing filtering. This is used to directly bias pin 5 of IC1b and to bias pin 2 of IC1a via a 1kΩ resistor.

The output at pin 7 of IC1b is fed to the non-inverting input (pin 3) of IC1a, which is configured as a non-inverting amplifier with a voltage gain of 471. Because of this very high gain, IC1a acts very much like a comparator. Its pin 1 output sits at over +8V when the IR beam is present, but falls to 0V when there is no IR light falling on PD1 (ie, the IR beam is interrupted).

IC1a's output in turn drives the base of transistor Q1 via a 10kΩ resistor. As a result, Q1 is turned on or off depending on whether the IR beam is present or not. When the IR beam is present, Q1 is on and when the beam is interrupted, Q1 turns off.

LED4 and its series 1kΩ resistor form the collector load of Q1. This means that LED4 lights when Q1 is on and turns off when Q1 is off. This allows LED4 to be used as a guide when lining-up the

Source's IR beam with PD1, as described previously.

### Switching the trigger output

Because Q1 is switched on when the IR beam falls on PD1, its collector voltage is normally held down to about 0.4V. However, if the beam is interrupted, Q1 turns off and its collector voltage rises to nearly +9V.

This sudden voltage change is used to switch on Q2, a 2N7000 MOSFET, which is used as an output switch across triggering output CON3. As shown, a 10nF coupling capacitor and Q2's 10kΩ gate resistor form a simple differentiating circuit. This results in Q2 being switched on only briefly when Q1's collector voltage rises when the beam is interrupted. The 100Ω resistor in series with the coupling capacitor is there to suppress any possible oscillation during switch-on or switch-off.

That's about it, apart from power switch S1 and the 470μF and 100nF capacitors, which decouple the supply rail voltage to keep it constant. The current drain of the detector circuit varies between about 7.5mA when the IR beam is present and 1.5mA when it is interrupted, so the total battery drain for both sections varies between 15mA (beam present) and 9mA (beam interrupted).

# Constructional Project

## Parts List

### IR Source Unit

- \* 1 PC board, code 808, size 57mm × 26mm
- 1 UB5-size box, 82mm × 53mm × 31mm
- 4 6mm long untapped spacers
- 4 M3 × 12mm screws, counter-sink head
- 4 M3 hex nuts
- 1 nylon cable tie, 75mm long
- 1 2m length of figure-8 cable
- 1 3.5mm mono jack plug, cable type (CON1)
- 3 5mm IR LEDs (LED1 to LED3)
- 1 820Ω resistor

### Detector Unit

- \* 1 PC board, code 809, size 122mm × 58mm
- 1 UB3-size box, 129mm × 68mm × 44mm
- 1 SPDT mini toggle switch (S1)
- 1 PC-mount 3.5mm stereo jack socket (CON2)
- 1 PC-mount 2.5mm concentric power plug (CON3)
- 4 M3 × 15mm tapped spacers
- 8 M3 × 6mm machine screws, pan head
- 2 1mm PC board terminal pins
- 1 9V battery clip lead
- 1 8-pin DIL IC socket
- 1 30mm length of 12mm to 15mm diameter black PVC conduit or brass tubing
- 1 piece of IR-transparent red film, approx. 16mm square
- 1 9V battery snap connector OR 1 x 4-way AA cell holder plus 1 x 2-way AA cell holder

### Semiconductors

- 1 LM358 dual op amp (IC1)
- 1 BC338 NPN transistor (Q1)
- 1 2N7000 N-channel MOSFET (Q2)
- 1 IR photodetector (PD1)
- (Jaycar ZD-1948 or similar)
- 1 5mm green LED (LED4)


### Capacitors

- 1 470μF 16V radial elect.
- 1 220μF 16V radial elect.
- 1 100nF metallised polyester
- 1 10nF metallised polyester
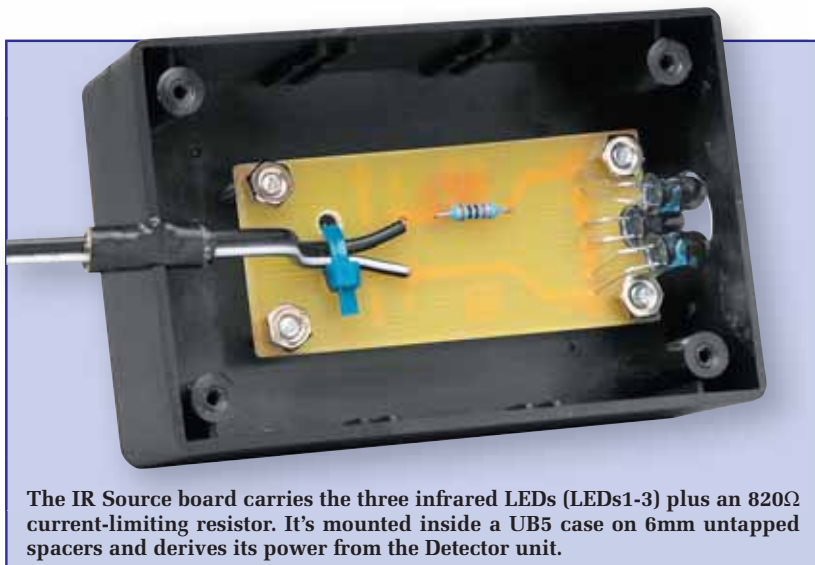
### Resistors (0.25W 1%)

- 1 470kΩ      1 2.7kΩ
- 1 220kΩ      2 1kΩ
- 2 22kΩ      1 100Ω
- 2 10kΩ

- \* Available as a pair from the EPE PCB Service



The IR Source board carries the three infrared LEDs (LEDs1-3) plus an 820Ω current-limiting resistor. It's mounted inside a UB5 case on 6mm untapped spacers and derives its power from the Detector unit.

## Construction

You can see from the photos that the two units which make up the Beam-Break Flash Trigger are each housed in a small plastic box. The IR Source circuit is built on a small PC board coded 808 (57mm × 26mm), while the Detector parts are installed on a larger PC board coded 809 (122mm × 58mm). These boards are available as a pair from the *EPE PCB Service*.

Start the assembly by building the IR Source board – see Fig.2. This should take you just a few minutes, since there are only four components to install – the three infrared LEDs and the 820Ω current-limiting resistor.

Be sure to orient the three IR LEDs correctly, as shown in Fig.2. **In addition, these three LEDs must be fitted with their leads bent down by 90°, so they face out of the end of the box when the board is mounted inside.**

In particular, note that the centre LED (LED2) is fitted with its body relatively low down near the board,

while the two outer LEDs are fitted higher and with their leads bent inwards towards LED2. This is done so that they form a triangular group, to provide a relatively compact beam source (see photo above).

Once these parts are in, install the power cable by soldering its leads to the +9V and 0V pads. The cable is then anchored using a small nylon cable tie that passes through the two 3mm holes on either side.

Having completed the board, it can be mounted inside its plastic box on four 6mm untapped spacers, and secured using four M3 × 12mm countersunk head screws and nuts. As shown in the photos, the IR LEDs face outwards through a 10mm hole in one end of the box, while the power cable exits via a small notch filed in the top at the opposite end. Fig.3 shows where to drill the holes in both boxes.

Finally, complete the IR Source unit by attaching the front panel label to the lid. A full-size artwork is shown

## Table 1: Resistor Colour Codes

No.	Value	4-Band Code (1%)	5-Band Code (1%)
1	470kΩ	yellow violet yellow brown	yellow violet black orange brown
1	220kΩ	red red yellow brown	red red black orange brown
2	22kΩ	red red orange brown	red red black red brown
2	10kΩ	brown black orange brown	brown black black red brown
1	2.7kΩ	red violet red brown	red violet black brown brown
2	1kΩ	brown black red brown	brown black black brown brown
1	820Ω	grey red brown brown	grey red black black brown
1	100Ω	brown black brown brown	brown black black black brown





An infrared transparent filter is fitted to the inside of the case at the receiving (PD1) end of the UB3 box, while a 30mm × 12mm-diameter 'light-hood' (eg, brass or plastic tubing) is attached to the outside of the case.



Follow this photo and the parts layout diagram Fig.2 to build the Detector PC board.

in Fig.3. A photocopy can be taken and cut out and glued on the case lid.

## Detector board assembly

There are more components on the Detector board, but its construction is still straightforward – see Fig.2. Install the resistors first, taking care to use the correct value at each location. Table 1 shows the resistor colour codes, but it's also a good idea to check each one using a digital multimeter before soldering it in place.

Follow these parts with the metallised polyester capacitors, then fit the two electrolytic capacitors. The latter are polarised, so be sure to orient them as shown. Next, the two PC board terminal pins, used to make the battery connections, can be fitted. **Note that both pins are fitted on the copper side of the board, to make it easier to solder the battery clip leads to them.**

Switch S1 and connectors CON2 and CON3 are next on the list, followed by an 8-pin socket for IC1. Be sure to orient the socket with its notched end towards the adjacent 100nF capacitor, to guide you when plugging in IC1 itself later on.

Transistor Q1, photodetector PD1, MOSFET Q2 and LED4 can now all go in, again taking care to orient them correctly. Note that PD1 is mounted vertically with its curved side facing outwards, and with the centre of its body about 5mm above the PC board. LED4 should also be mounted vertically, with the bottom of its body about 12mm above the board (this ensures that it will protrude slightly from its matching hole in the box lid after assembly).

The Detector board can now be completed by plugging IC1 into its socket (take care with the orientation).

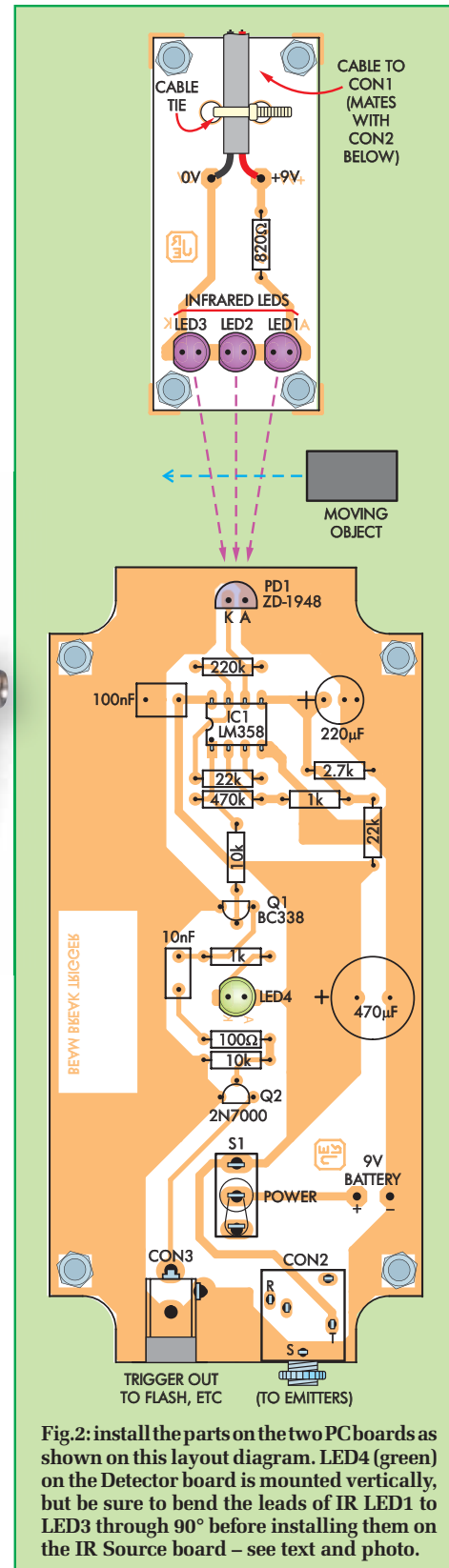


Fig.2: install the parts on the two PC boards as shown on this layout diagram. LED4 (green) on the Detector board is mounted vertically, but be sure to bend the leads of IR LED1 to LED3 through 90° before installing them on the IR Source board – see text and photo.

# Constructional Project

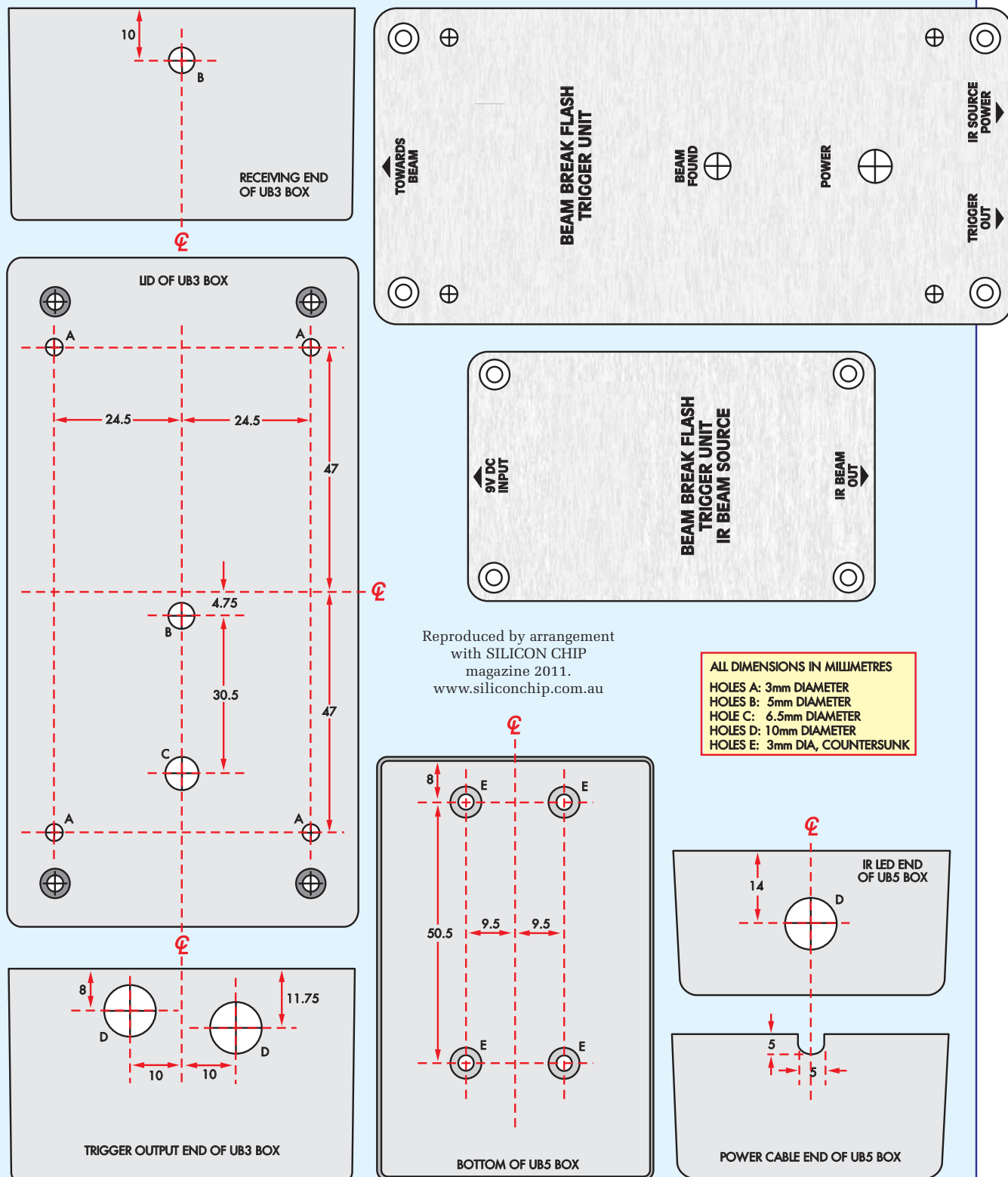


Fig.3: these drilling diagrams for the UB3 and UB5 boxes can be copied and used directly as templates, or you can mark the holes out manually using the measurements indicated. Also shown are the two front panel artworks. They can be photocopied, cut out and glued on the boxes.

The detector board is then ready to be mounted behind the lid of the UB3-size plastic box.

The first step is to drill and ream out the various holes in the lid and ends of the box, as shown in Fig.3. That done, fit a photocopy of the front panel label and cut out the holes using a sharp hobby knife, then secure the board to the lid using four M3 × 15mm tapped spacers and eight M3 × 6mm machine screws.

Note that you'll need to remove the upper nut from the ferrule of switch S1 before doing this, so the ferrule can pass up through its matching hole in the lid. Once the board is in place, the nut can be replaced and threaded down against the top of the lid. The lower nut and lockwasher can then be threaded up against the underside of the lid, using a small spanner.

The next step is to fit a small square of red 'IR transparent' film inside the box behind the single 5mm hole at the IR photodetector diode PD1 end. It can be held in place using a couple of narrow strips of transparent tape, one on either side.

A short 'light hood' is now attached to the photodetector (PD1) end of the box. This must cover the 5mm hole and be as close as possible to concentric with it.

The hood itself can be fashioned from a 30mm length of 12mm diameter brass tubing (see photos) or from a similar length of opaque (preferably black) PVC conduit. Whichever you use, it's simply glued to the end of the box using five-minute epoxy cement.

Now for the final assembly. First, solder the battery-snap leads to the terminal pins on the underside of the board, then place the battery in the bottom of the box and fasten it in place using either a small aluminium 'U' bracket or a strip of gaffer tape. Finally, lower the lid and PC board assembly into the box before fitting the screws to hold everything together.

### Trying it out

No adjustments are required, so you can try it out simply by plugging the power cable from the IR Source into CON2 on the Detector unit and turning on power switch S1.

If the Detector's light hood is now aligned with the output from the IR Source (or any other source of IR radiation), LED4 should immediately begin glowing. If it does, block the end of the hood with your thumb or a small piece



▲ Above: the Detector board is secured to the lid of the UB3 case using four M3 × 15mm tapped spacers and eight M3 × 6mm machine screws

◀ Left: a 'light hood' is fitted to the end of the Detector unit to prevent interference from stray IR light sources.

of opaque material and check that the LED immediately switches off.

The same thing should happen if you turn the IR Source away from the Detector, or if you simply block the beam with your hand or some other small opaque object. If this happens, then your Beam-Break Flash Trigger is probably working correctly and is ready for use.

If you're going to be using it in conjunction with the Time Delay Photoflash Trigger unit, all that remains is to make up a suitable cable to connect

the two together. This simply involves connecting the Detector's trigger output to the 'external trigger contacts' input (CON4) of the delay unit.

The Beam-Break Flash Trigger should give reliable triggering with the IR Source unit placed up to a metre or so from the Detector box in normal room lighting. This 'beam length' range can be extended considerably in dark (eg, night-time) conditions, but in bright sunlight it will be shortened due to the relatively high level of IR in the ambient light. **EPE**

### Direct flash triggering: making the cable

**A**s mentioned in the article, the Beam-Break Flash Trigger can also be used to trigger an electronic flash directly, rather than via the Time Delay Photoflash Trigger. To do this, trigger output CON3 is simply connected to the photoflash via a suitable cable.

However, when you're making up this cable, make sure that the positive side lead from the flash input is connected to the centre contact of the plug that goes to CON3. If the polarity is reversed, MOSFET Q3 in the Beam-Break Flash Trigger could be damaged.

The procedure is to first use your DMM to check the polarity of the voltage at the end of the cable that's plugged into the flash unit (ie, with the flash unit powered up and ready for triggering). Once that's done, you'll then know which way round to connect the cable to the plug that goes to CON3 on the Detector unit.

While you're checking the polarity of the cable leads, make a note of the actual voltage itself. If it is below 60V, that won't be a problem. Conversely, if it's higher than 60V, you'll need to replace the 2N7000 MOSFET with one having a higher voltage rating – such as an IRF540N.




# CONVERTING UNIDEN SCANNERS FOR AIS

THESE well-priced, wide-coverage and very popular handheld scanners offer a valuable 'close call' feature and have become well respected for general VHF/UHF work.

The discriminator tap access is straightforward and fitting an external socket should make for a neat and professional enhancement to the set. However, your scanner warranty may become invalid!

All variants of the UNIDEN UBC72/73 and 92/93 use the 24-pin TOKO TK10931 discriminator IC, with base-band audio output at pin 12 (LND7). This accesses the unfiltered audio. A resistor soldered to a convenient pad on the PC board provides the tap without otherwise affecting scanner operation. In most cases, a 10kΩ resistor suffices, but with some sound cards we've had to go as high as 220kΩ to avoid overload. You could also use a 220kΩ trimpot in series with a 10kΩ resistor to make adjustment easier.

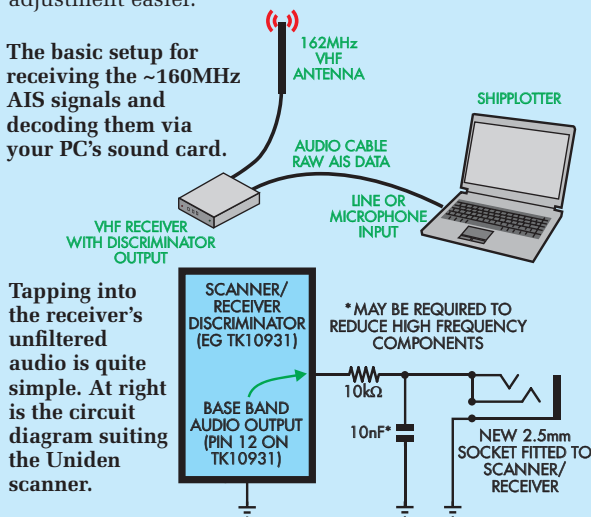The basic setup for receiving the ~160MHz AIS signals and decoding them via your PC's sound card.



Tapping into the receiver's unfiltered audio is quite simple. At right is the circuit diagram suiting the Uniden scanner.



Undoing six Phillips-head screws readily dismantles the Uniden scanner and the revealed circuit boards simply clip apart. Neatly solder the 10kΩ resistor and outlet wire at LND7, perhaps sliding fine heat shrink tubing over the wire joint to prevent circuit board shorts.

The resistor's other end is wired to a 2.5mm mono chassis socket mounted on the back of the scanner. There is sufficient space between the stacked PCBs and case for this.

A short wire for the ground lead can be run to the antenna's ground terminal – a 10nF capacitor between the resistor's far end and ground may help remove residual higher frequency portions.

A 2-wire external lead then connects to a stereo 3.5mm plug to suit the PC soundcard's line-in or mic input socket. The scanner squelch must be wide open ('hissing') but the scanner's internal speaker volume can be turned right down.

### The antenna

Unlike 2.4GHz WiFi, VHF marine signals are not so influenced by nearby obstructions, but the best AIS reception will still be gained with clear line-of-sight (LOS) coverage.

The supplied 'rubber ducky' whip antenna on most scanners should allow open-terrain AIS reception to perhaps 6nm (nautical miles) (~10km), but either elevation or a better antenna (or both) will greatly assist – it really depends on your proximity to nearby shipping.

The BNC socket on most scanners readily allows modest coax runs to rooftop Yagi beams, but a simpler and more portable antenna may be better – especially if AIS signals come from a wide arc.



To prevent confusion with the scanner's fitted 3.5mm headphone socket, the output socket to the computer sound card should be an open-type 2.5mm mono socket (eg, Jaycar PS-0105), as modern enclosed types are slightly too long for the most suitable rear case hole position.

## ... and a cheap 'Slim Jim' antenna to make By Stan Swan

### A DIY 'Slim JIM'

One of the most appealing antennas for such work is the so called 'Slim Jim' (an acronym for 'J-type Integrated Match') – invented in 1978 by the late Fred Judd, G2BCX.

Any parallel conductors could be used (some diehards swear by HO-scale model train track!), but such an antenna can be quickly and cheaply made from a length of 300Ω impedance TV ribbon.

This is becoming rather difficult to get, having largely given way to 75Ω coaxial cable (which is, of course, entirely *unsuitable*).

Although cheap, this ribbon rapidly deteriorates in the wind and sun if left unprotected, so housing inside a vertically supported plastic conduit (eg, mains conduit) is almost essential for outside use. Plastic conduit will not degrade performance at all.

Considerable variation on the basic design can be tolerated, as aspects such as the gap space, conductor spacing, velocity factor (VF) of the wire and even nearby metallic objects influence performance.

At 162MHz, an open-space wavelength = speed/frequency =  $3 \times 10^8 / 1.62 \times 10^8 = 1850\text{mm}$ . However, slower signals within the TV ribbon decrease this by ~0.9 (known as the velocity factor) giving a working AIS wavelength of 1665mm.

The Slim Jim is  $\frac{3}{4}$ -wavelength long (although only the upper half-wave portion receives), so a 1250mm antenna length should suffice. 'Cut and try' experimentation is encouraged – cut slightly longer initially and trim to suit for best performance.

Almost any TV-grade (ie 75Ω) coax suits Slim Jim connection to the VHF receiver's BNC antenna socket, and use of light-grade flexible coax makes a roll-up version feasible.


Unless you're making a very long run from antenna to receiver, losses should not be too much of a problem. Of course, if your run is long (ie, greater than, say 10m), go for one of the better (low-loss) cables.

To construct a Slim Jim, simply follow the diagram at top right. You'll need a length of ribbon cable about 1280mm long, to allow the two ends to be stripped and shorted, as shown.

The wires at each end of the cable are bared, twisted together and soldered (don't ignore the last part, especially if you are going to erect the antenna outside). In fact, a short length (30mm or so?) of heatshrink tubing over each end will further protect the copper wire from corrosion.

The exact position for the coax feed connection is not all that important for a receiving antenna – between 30 and 100mm up from the bottom is the range. The centre wire of the coax is soldered to the  $\frac{3}{4}$  wavelength side (don't cut the wire, just remove the insulation) while the braid connects to the matching stub opposite the centre wire connection point.

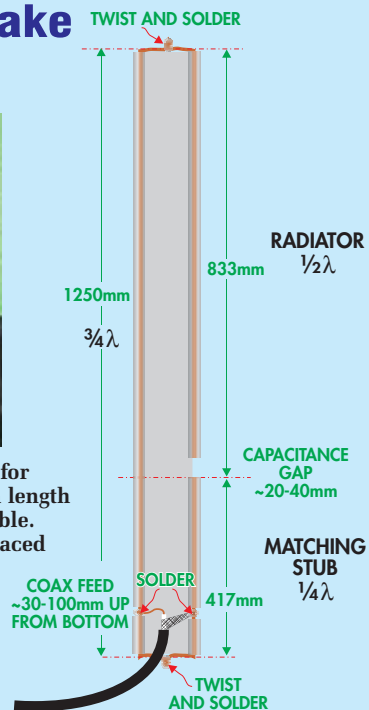The capacitance gap, on the 'earthy' side only, can be anywhere from about 20mm to 40mm. Don't simply cut the cable; the short length of wire needs to be removed.




A 'Slim Jim' antenna for 162MHz made from a length of 300Ω TV ribbon cable. This would best be placed inside a length of plastic conduit and mounted outside, as high as possible and away from metal (such as a mast or roof).

Apart from putting it inside a suitable length of conduit (say 1.3m) with a plug on the top end (the bottom end could be filled with silicone sealant to stop insects and spiders calling the Slim Jim home), your antenna is now complete and ready for use.

Slim Jim low angle performance is legendary, as the design best handles signals received near parallel to the ground – forget it for near-overhead aircraft and satellites!

Unless you're tracking flying boats (or live on a hilltop), vessels are naturally going to be near-horizontal anyway. Slim Jim AIS reception out to 20nm (~30km) could be expected when the antenna is well elevated, perhaps by being hoisted up a tree (inside a conduit) with a nylon line.

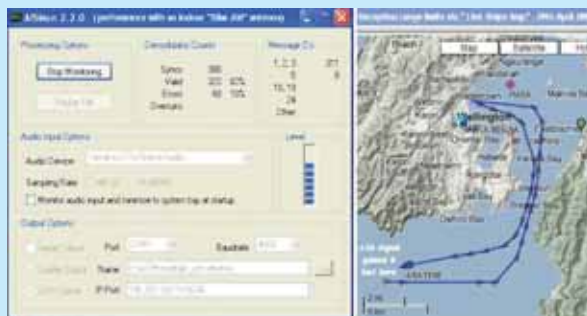Reproduced by arrangement with SILICON CHIP magazine 2011.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)



Stan, monitoring at Eastbourne (green symbol) tracks two vessels using VHF radio AIS into and out of Wellington harbour. This gives a good idea of the type of performance to expect using the modified scanner and Slim Jim antenna described here and AISMon software running on your PC.

# Ingenuity Unlimited

Readers' Circuits

**Our regular round-up of readers' own circuits**

**WIN A PICO PC-BASED OSCILLOSCOPE WORTH £799**

- 200MHz Analogue Bandwidth Dual Channel Storage Oscilloscope
- Spectrum Analyser • Frequency Meter • Multimeter • USB Interface.

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC-based oscilloscope could be yours. After every 20 published IU circuits, Pico Technology will be awarding a PicoScope 3206 digital storage oscilloscope for the best IU submission. In addition a PicoScope 2105 Handheld 'Scope worth £199 will be presented to the runner up.

We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas must be the reader's own work and **must not have been published or submitted for publication elsewhere.**

The circuits shown have NOT been proven by us. **Ingenuity Unlimited** is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: Ingenuity Unlimited, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Email: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk). **Your ideas could earn you some cash and a prize!**



## PCB Track Probing unit – *On track*

I RECENTLY purchased from *EPE* the Version 3 PICmicro MCU development board. Unfortunately, this unit comes without any instructions, circuit diagram or even block diagram. As I wish to use this versatile looking piece of equipment to develop PIC circuits of my own design, I needed to ascertain where connectors and plugs and sockets were connected in the circuit.

I have used the idea I am about to describe many times before in lash-up form, but felt that I ought to make this one as a completed unit, calibrated and mounted in a convenient box and having suitable probes. I then realised that it could be of interest to other readers of *EPE*, hence this letter/IU.

### On track

The requirement was to be able to trace printed circuit tracks between components, IC pins, and sockets, even while components populate the PCB, but without power being connected. This probing should not cause any junctions that are connected between the probes to turn 'on' and should show unambiguous connections, while possibly being able to measure track resistance at the same time.

The finished circuit will allow the measurement of resistance, up to two hundred ohms in my case. This figure could be changed if required, but for my intended use this is adequate. If a track reading is below the calibrated set point on the dial, an audible sound is heard.

### Circuit details

I decided to use a low voltage of about 0.3V to power the probes, and a variable trip point on a comparator to sense the connections and its

resistance between pins and tracks. The low voltage is derived by using a resistor chain from both the positive supply and also the negative supply (a single 9V battery) with a 1N4002 'dropper' diode, as may be observed from the circuit diagram Fig.1.

As the circuit around the 'dropper' diode is a DC Wheatstone bridge, the trip point could be used to infer low values of resistance of track. The bridge detector is the high gain (open loop) differential circuit, the output of which triggers an audible warning output stage.

The circuit is powered with a single 9V battery. The low probe voltage is derived from the voltage drop across D1, a 1N4002 silicon rectifier. It is tapped down using a couple of 1.5k $\Omega$  resistors in the upper arms, and 1k $\Omega$  in the lower arms, with a 250 $\Omega$  variable resistor (pot.) shunting one of the arms as shown. The probes connect across

the other lower arm. These resistors form the Wheatstone bridge circuit, with the probe as the unknown value.

When the 'test' PCB is probed, if track exists between the probe points, then the voltage across the probe falls, depending upon the resistance of the track. This drop in voltage is sensed by a comparator (IC1a) with an adjustable reference voltage, also derived from the potted down voltage from the D1.

The output from the comparator turns on an oscillator (IC1b) driving a piezo sounder. I use an audible warning instead of an LED, as this means that I do not have to switch my eyes back and forth while probing. By adjusting the trip point, an indication may be had of the resistance of the track, in the classic Wheatstone bridge manner. In a normal Wheatstone bridge a null indicator is used, but this unit uses a 'go-nogo' indication, or high/low change at the resistance

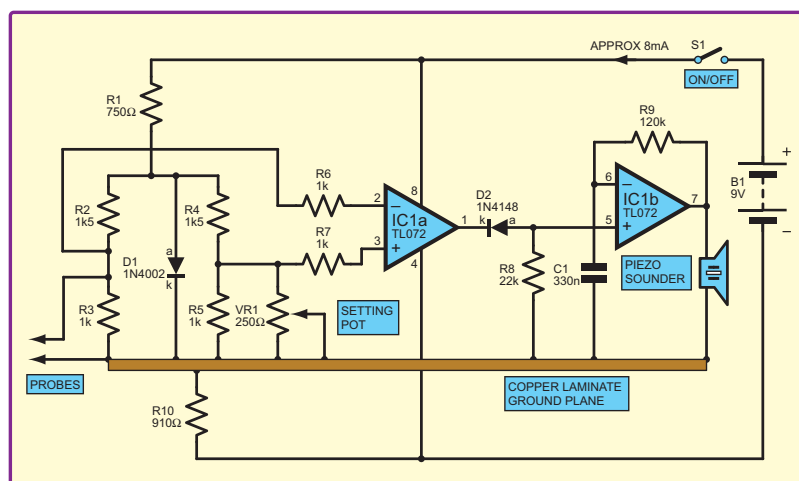


Fig.1. Circuit diagram for the PCB track probe



value across the probes. An audible output indicates track resistance below the Setting Pot calibrated value, while no audible output indicates high resistance between the probes.

I made my probes using two largish sewing needles soldered to the probe wires, and mounted with hot melt glue inside two old Biro cases, cheap as chips!

#### Calibration and construction

Calibration may be done using a number of known low value resistors

in series, adjusting the trip at each point to trigger the acoustic sounder, and marking the panel accordingly. Of course, this Wheatstone bridge method is used in old fashioned instruments to determine resistor values very accurately, but my requirement here is only to a few percent in resistance value at best. My unit works very well.

I made my unit using a form of construction that I favour for prototype and one off construction. This uses copper laminate as a base and 'ground'

connection, and gluing on pieces of stripboard, cut to suitable size and shape to mount IC's and other components.

It is similar to 'ugly' construction, but I find it easy and convenient, even when cannibalising old prototypes on stripboard that I have made over the years, to supply the small pieces of board required, so the cost is quite low.

Ivan J Eamus,  
Rutland

**Light Weight  
Compact  
Thin...!**

for diy /  
hobby /  
beam solar  
Robotics



www.shreyanshindia.com  
email: deopal@vsnl.com,  
shreyansh1093@yahoo.co.in

**Resin Laminated Micro Solar cell Modules**  
from 0.5/1/1.5/2/3/4/5/6/9 Volts to 80/100/200/300/450ma



**Why tolerate when you can automate?**



**Home Automation**



**C-Bus Shop**  
C-Bus and  
C-Bus Wireless



**KAT5 AV transmission  
and IR control system**



**Barix Ethernet based  
MP3, communications  
and control systems**

[www.laser.com](http://www.laser.com)

*Integrators, Installers, Trade  
and Retail customers welcome*

[www.cbushop.com](http://www.cbushop.com)

**Laser Business Systems Ltd**  
Tel: +44 (0) 20 8441 9788  
Fax: +44 (0) 20 8449 0430  
Email: [info@laser.com](mailto:info@laser.com)  
16 Garthland Drive, EN5 3BB



**CRICKLEWOOD  
ELECTRONICS**  
Established 1981



Frustrated with your supplier?  
Visit our component packed  
website for a vast range of  
parts - old and new,  
many unavailable elsewhere!  
[www.cricklewoodelectronics.com](http://www.cricklewoodelectronics.com)

**1000's OF PRICES REDUCED!**

Alternatively phone us on  
020 8452 0161 with your  
requirements.



**Visit our Shop, Call or Buy online at:**  
[www.cricklewoodelectronics.com](http://www.cricklewoodelectronics.com)  
**020 8452 0161**

Visit our shop at:  
40-42 Cricklewood Broadway  
London NW2 3ET

**Technobots**  
Electronic & Mechanical Components

With over 5,100 products available to order online, Technobots provides one of the widest range of components for the electronics and engineering enthusiast

  
Opto Electronics

  
Battery Products  
Chargers & PSU's

  
Controller Boards  
Including Arduino

  
Passives,  
Semiconductors  
Sensors  
connectors  
etc..

  
Gears, Pulleys  
& Cams

  
Breakout Boards  
from Sparkfun

  
Pneumatics

  
Bearings from 1mm bore

  
Chain & sprockets

  
Projects & kits

  
160+ dc model  
motors + speed  
controllers

  
Switches &  
Relays

  
LCD displays

  
Cable, Fuses & etc..

  
Tools

  
Robotics & Wheels

Education Accounts  
Welcome


Get our 120 page A4 catalogue free with your  
next order by quoting 'discount coupon code'  
EPE05 at the checkout

[www.technobotsonline.com](http://www.technobotsonline.com)

Shop callers welcome: Technobots Ltd, 60 Rumbridge Street,  
Totter, Hampshire SO40 9DS Tel: 023 8086 4891

# TEACH-IN 2011
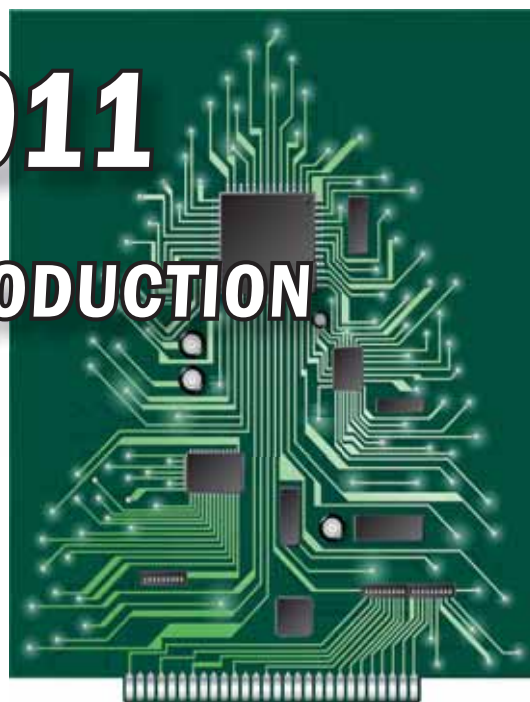
## A BROAD-BASED INTRODUCTION TO ELECTRONICS



### Part 9: Digital-to-Analogue and Analogue-to-Digital Conversion

By Mike and Richard Tooley

Our Teach-In series is designed to provide you with a broad-based introduction to electronics. We have attempted to provide coverage of three of the most important electronics units that are currently studied in many schools and colleges in the UK. These include Edexcel BTEC Level 2 awards, as well as electronics units of the new Diploma in Engineering (also at Level 2). The series will also provide the more experienced reader with an opportunity to 'brush up' on specific topics with which he or she may be less familiar.

Each part of our Teach-In series is organised under five main headings; Learn, Check, Build, Investigate and Amaze. Learn will teach you the theory, Check will help you to check your understanding, and Build will give you an opportunity to build and test simple electronic circuits. Investigate will provide you with a challenge which will allow you to further extend your learning, and finally, Amaze will show you the 'wow factor'!

IN THIS instalment of *Teach-In 2011*, we introduce some combined applications of analogue and digital circuits in the form of digital-to-analogue and analogue-to-digital converters (DAC, ADC). In **Learn** we explore the circuits and techniques used in DAC and ADC. **Investigate** extends this further with a look at a popular DAC, which is available from several semiconductor manufacturers.

**Build** looks at some further applications of digital circuits using both combinational and sequential logic techniques. Finally, in **Amaze** we look at the way that very large numbers are handled in digital systems.

## Learn

### Quantisation

Because signals in the real world exist in both digital (*on/off*) and analogue (*continuously variable*) forms, digital and computer systems need to be able to accept and generate both types of signal as inputs and outputs respectively. Because of this, there is a need for devices that can convert signals in analogue form to their equivalent in digital form, and vice versa.

This chapter introduces digital-to-analogue and analogue-to-digital conversion. We shall begin by looking at the essential characteristics of analogue and digital signals and the principle of *quantisation*.

In order to represent an analogue signal using digital codes, it is necessary to approximate (or quantise) the signal into a set of discrete voltage levels, as shown in Fig.9.1 The sixteen quantisation levels for a simple analogue-to-digital converter using a four-bit binary code are shown in Fig.9.2. Note that, in order to accommodate analogue signals that have both positive and negative polarity we have used the two's complement representation to indicate negative voltage levels.

Thus, any voltage represented by a digital code in which the MSB (most significant bit) is logic 1 will be negative. Fig.9.3 shows how a typical analogue signal would be quantised

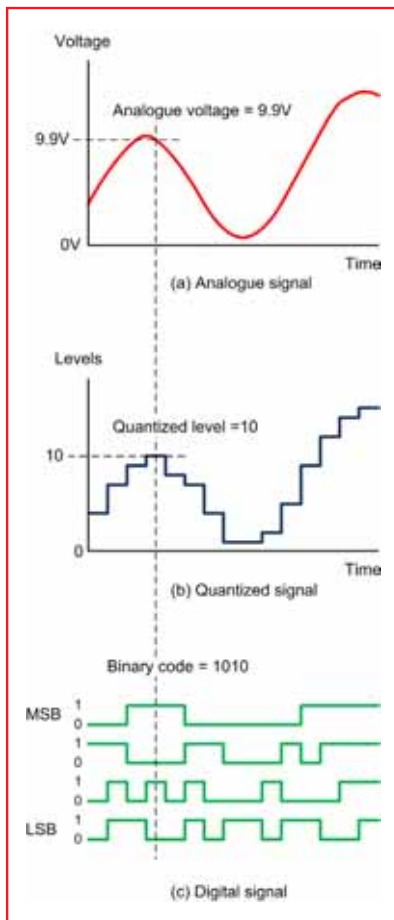


Fig.9.1. The process of quantising an analogue signal into its digital equivalent

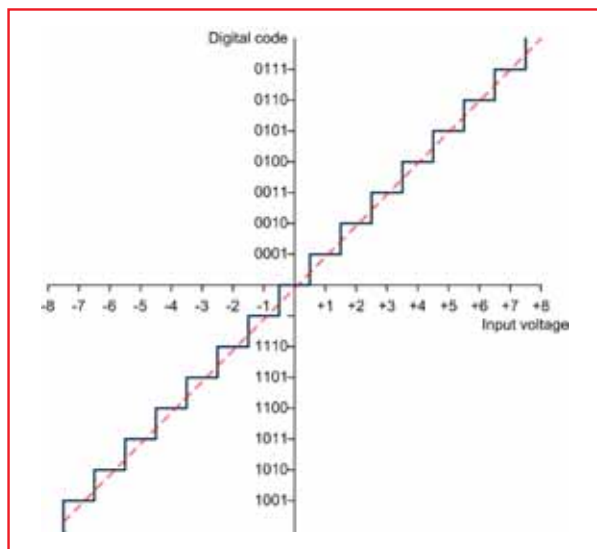


Fig.9.2. Quantisation levels for a simple ADC that uses a four-bit binary code

into voltage levels by sampling at regular intervals ( $t_1, t_2, t_3$ , etc).

## Digital-to-analogue conversion

The basic digital-to-analogue converter (DAC) has a number of digital inputs (often 8, 10, 12, or 16) and a single analogue output, as shown in Fig.9.4. The simplest form of DAC shown in Fig.9.5(a) uses a set of binary-weighted resistors to define the voltage gain of an operational summing amplifier and a four-bit binary latch to store the binary input while it is being converted.

Note that, since the amplifier is connected in inverting mode, the analogue output voltage will be negative rather than positive. However, a further inverting amplifier stage can be added at the output to change the polarity if required.

The voltage gain of the inputs to the operational amplifier (determined by the ratio of feedback to input resistance and taking into account the inverting configuration) is shown in Table 9.1. If we assume that the logic levels produced by the four-bit data latch are 'ideal' (such that logic 1 corresponds to +5V and logic 0 corresponds to 0V), we can

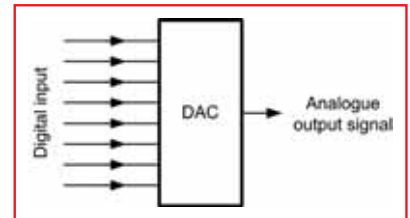


Fig.9.4. Basic DAC representation

determine the output voltage corresponding to the eight possible input states by summing the voltages that will result from each of the four inputs taken independently.

For example, when the output of the latch takes the binary value 1010 the output voltage can be calculated from:

$$V_{\text{out}} = (-1 \times 5) + (-0.5 \times 0) + (-0.25 \times 5) + (-0.125 \times 0) = -6.25V$$

Similarly, when the output of the latch takes the binary value 1111 (the maximum possible) the output voltage can be determined from:

$$V_{\text{out}} = (-1 \times 5) + (-0.5 \times 5) + (-0.25 \times 5) + (-0.125 \times 5) = -9.375V$$

Table 9.1. Table of voltage gains for the simple DAC shown in Fig.9.5(a)

Bit	Voltage gain
3 (MSB)	$-R/R = -1$
2	$-R/2R = -0.5$
1	$-R/4R = -0.25$
0 (LSB)	$-R/8R = -0.125$

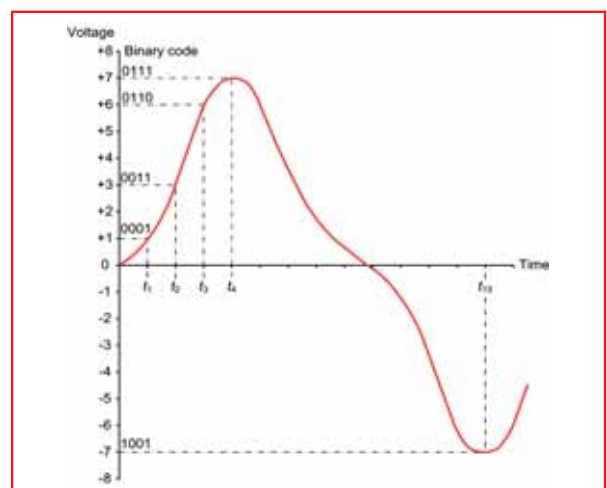


Fig.9.3. An analogue signal quantised into voltage levels by sampling at regular intervals ( $t_1, t_2, t_3$ , etc.)



The complete set of voltages corresponding to all eight possible binary codes is given in Table 9.2.

## Binary-weighted DAC

An improved binary-weighted DAC is shown in Fig.9.5(b). This circuit operates on a similar principle to that shown in Fig.9.5(a), but uses four analogue switches instead of a four-bit data latch. The analogue

switches are controlled by logic inputs so that a switch's output is connected to the reference voltage ( $V_{ref}$ ) when its respective logic input is at logic 1, and to 0V when the corresponding logic input is at logic 0.

When compared with the previous arrangement, this circuit offers the advantage that the reference voltage is considerably more accurate and stable than using the logic level to


define the analogue output voltage. A further advantage arises from the fact that the reference voltage can be made negative, in which case the analogue output voltage will become positive. Typical reference voltages are  $-5V$ ,  $-10V$ ,  $+5V$  and  $+10V$ .

Unfortunately, by virtue of the range of resistance values required, the binary-weighted DAC becomes increasingly impractical for higher resolution applications. Taking a 10-bit circuit as an example, and assuming that the basic value of  $R$  is  $1k\Omega$ , the binary weighted values would become:

- Bit 0  $1k\Omega$
- Bit 2  $2k\Omega$
- Bit 3  $4k\Omega$
- Bit 4  $8k\Omega$
- Bit 5  $16k\Omega$
- Bit 6  $32k\Omega$
- Bit 7  $64k\Omega$
- Bit 8  $128k\Omega$
- Bit 9  $256k\Omega$

**Table 9.2. Output voltages produced by the simple DAC shown in Fig.9.5(a)**

Bit 3	Bit 2	Bit 1	Bit 0	Output voltage
0	0	0	0	0V
0	0	0	1	-0.625V
0	0	1	0	-1.250V
0	0	1	1	-1.875V
0	1	0	0	-2.500V
0	1	0	1	-3.125V
0	1	1	0	-3.750V
0	1	1	1	-4.375V
1	0	0	0	-5.000V
1	0	0	1	-5.625V
1	0	1	0	-6.250V
1	0	1	1	-6.875V
1	1	0	0	-7.500V
1	1	0	1	-8.125V
1	1	1	0	-8.750V
1	1	1	1	-9.375V

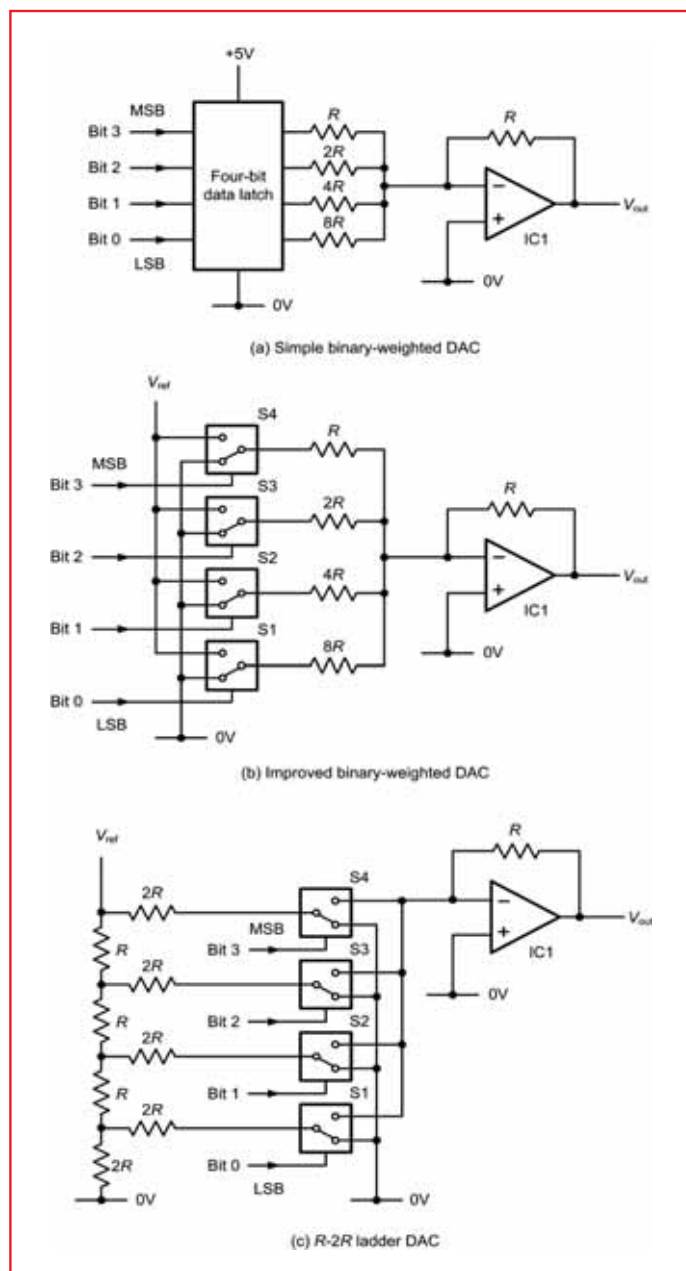

*Fig.9.5. Simple DAC arrangements*

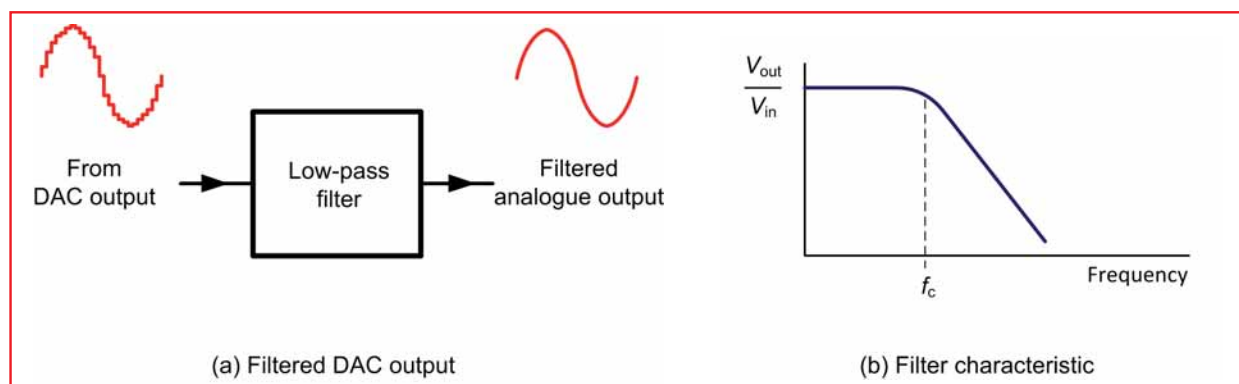


Fig.9.6. Filtering the output of a DAC

In order to ensure a sufficiently high degree of accuracy, all of these resistors would need to be close-tolerance types (typically  $\pm 1\%$ , or better). A more practical arrangement uses an operational amplifier in which the input voltage to the operational amplifier is determined by means of an  $R$ - $2R$  ladder, as shown in Fig.9.5(c).

Note that only two resistance values are required and that they can be any convenient value provided that one value is double the other (it is relatively easy to manufacture matched high-stability resistances of close tolerance on an integrated circuit chip).

### Accuracy and resolution

The accuracy of a DAC depends not only on the values of the resistance used, but also on the reference voltage used to define the voltage levels. Special band-gap references (similar to precision Zener diodes) are normally used to provide reference voltages that are closely maintained over a wide range of temperature and supply voltages. Typical accuracies of between 1% and 2% can be achieved using most modern low-cost DAC devices.

The resolution of a DAC is an indication of the number of increments in output voltage that it can produce and it is directly related to the number of binary digits used in the conversion. The two simple four-bit DACs that we met earlier can each provide sixteen different

output voltages, but in practice we would probably require many more (and correspondingly smaller) increments in output voltage.

This can be achieved by adding further binary inputs. For example, a DAC with eight inputs (ie, an 8-bit DAC) would be capable of producing 256 (ie,  $2^8$  or two raised to the power eight) different output voltage. A 10-bit device, on the other hand, will produce 1024 (ie,  $2^{10}$  or two raised to the power ten) different voltage levels. The resolution of a DAC is generally stated in terms of the number of binary digits (ie, bits) used in the conversion.

### Please note!

The *resolution* of a DAC depends on the number of bits used in the conversion process—the more bits the greater the resolution. Typical DACs have resolutions of 8, 10 or 12 bits.

### Please note!

The *accuracy* of a DAC depends on the accuracy of the resistance values used, as well as the accuracy of the reference voltage. Typical DACs have accuracies of 1% or 2%

### Filters

As we have seen, the output of a DAC consists of a series of quantised voltage levels. The presence of these levels on the output signal can be undesirable for some applications, and hence they are removed in order to 'smooth' the output voltage.

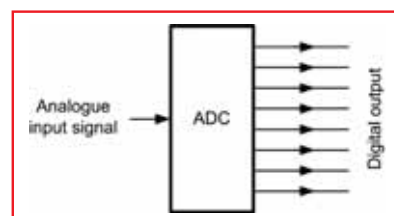


Fig.9.7. Basic ADC representation

This can be easily accomplished by passing the output signal through a low-pass filter, as shown in Fig.9.6. The filter is designed so that the residual sampling frequency components (ie, those that cause the 'steps' in the analogue signal) are well beyond the cut-off frequency of the filter and are subject to an appreciable amount of attenuation.

### Analogue-to-digital conversion

The basic analogue-to-digital converter (ADC) has a single analogue input and a number of digital outputs (often 8, 10, 12, or 16 lines), as shown in Fig.9.7.

Various forms of analogue-to-digital converter are available for use in different applications, including multi-channel ADCs with up to 16 analogue inputs. The simplest form of ADC is the flash converter shown in Fig.9.8(a). In this type of ADC the incoming analogue voltage is compared with a series of fixed reference voltages using a number of operational amplifiers (IC1 to IC7 in Fig.9.8). When the analogue input voltage exceeds the reference

voltage present at the inverting input of a particular operational amplifier stage, the output of that stage will go to logic 1. So, assuming that the analogue input voltage is 2V, the outputs of IC1 and IC2 will go to logic 1 while the remaining outputs will be at logic 0.

The *priority encoder* is a logic device that produces a binary output code that indicates the value of the most significant logic 1 received on one of its inputs. In this case, the output of IC2 will be the most significant logic 1 and hence the binary output code generated will be 010 (as shown in Fig.9.8(b)).

Flash ADC are extremely fast in operation (hence the name), but they become rather impractical as the resolution increases. For example, an 8-bit flash ADC would require 256 operational amplifier comparators while a 10-bit ADC would need a staggering 1024 comparator stages!

Typical conversion times for a flash ADC lie in the range 50ns to 1 $\mu$ s, so this type of ADC is ideal for 'fast' or rapidly changing analogue signals. Due to their complexity, flash ADC are relatively expensive.

## Successive approximation

A successive approximation ADC is shown in Fig.9.9. This shows an 8-bit converter that uses a DAC (usually

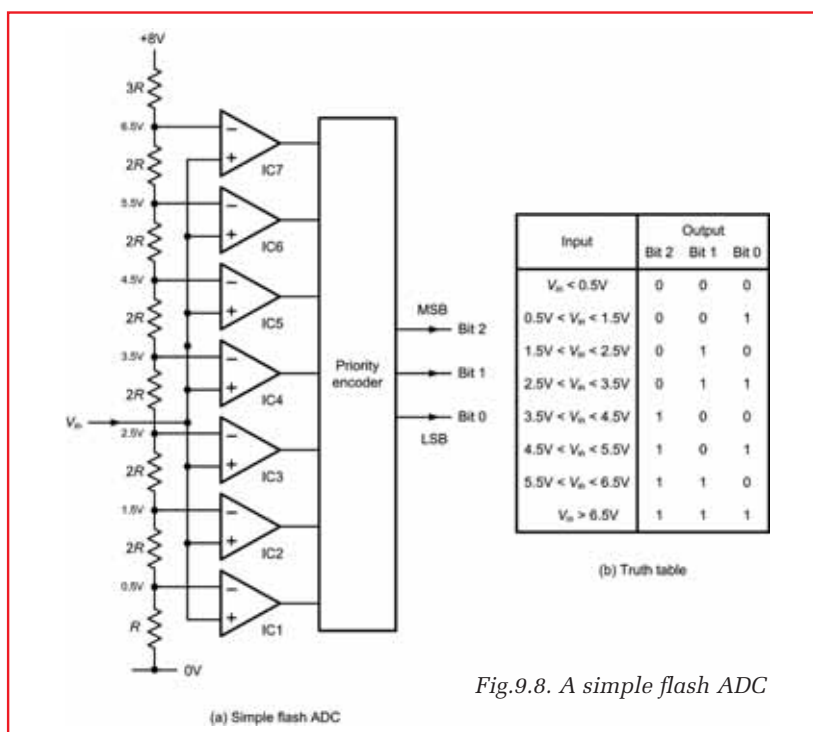


Fig.9.8. A simple flash ADC

based on an  $R$ - $2R$  ladder) together with a single operational amplifier comparator (IC1) and a successive approximation register (SAR).

The 8-bit output from the SAR is applied to the DAC and to an 8-bit output latch. A separate end of conversion (EOC) signal (not shown in Fig.9.9) is generated to indicate that the conversion process is complete and the data is ready for use.

When a start conversion (SC) signal is received, successive bits

within the SAR are set and reset according to the output from the comparator. At the point at which the output from the comparator reaches zero, the analogue input voltage will be the same as the analogue output from the DAC and, at this point, the conversion is complete. The end of conversion signal is then generated and the 8-bit code from the SAR is read as a digital output code.

Successive approximation ADCs are significantly slower than flash

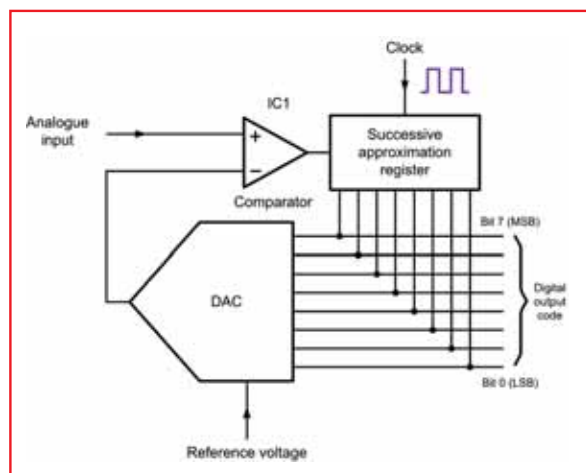


Fig.9.9. A successive approximation ADC

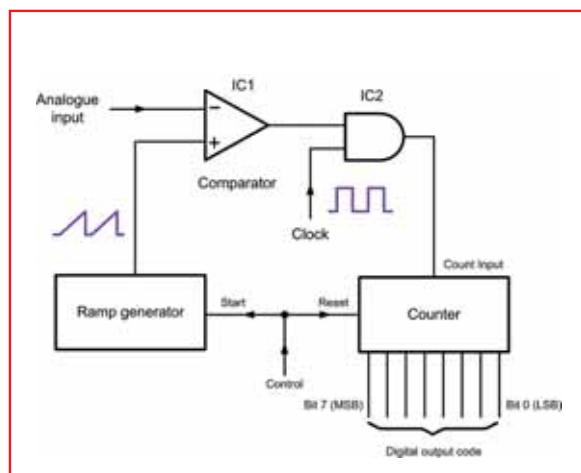


Fig.9.10. A ramp-type ADC



types and typical conversion times (ie, the time between the SC and EOC signals) are in the range  $10\mu\text{s}$  to  $100\mu\text{s}$ . Despite this, conversion times are fast enough for most non-critical applications, and this type of ADC is relatively simple and available at low-cost.

## Ramping it up

A ramp-type ADC is shown in Fig.9.10. This type of ADC uses a ramp generator and a single operational amplifier comparator, IC1.

The output of the comparator is either a 1 or a 0 depending on whether the input voltage is greater or less than the instantaneous value of the ramp voltage. The output of the comparator is used to control a logic gate (IC2) which passes a clock signal (a square wave of accurate frequency) to the input of a pulse counter whenever the input voltage is greater than the output from the ramp generator.

The pulses are counted until the voltage from the ramp generator exceeds that of the input signal, at which point the output of the comparator goes low and no further pulses are passed into the counter. The number of clock pulses counted will depend on the input voltage and the final binary count thus gives a digital representation of the analogue input. Typical waveforms for the ramp-type waveform are shown in Fig.9.11.

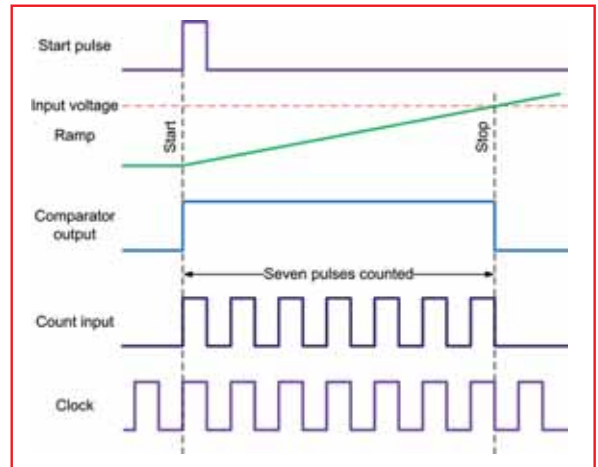


Fig.9.11. Waveforms for a single-ramp ADC

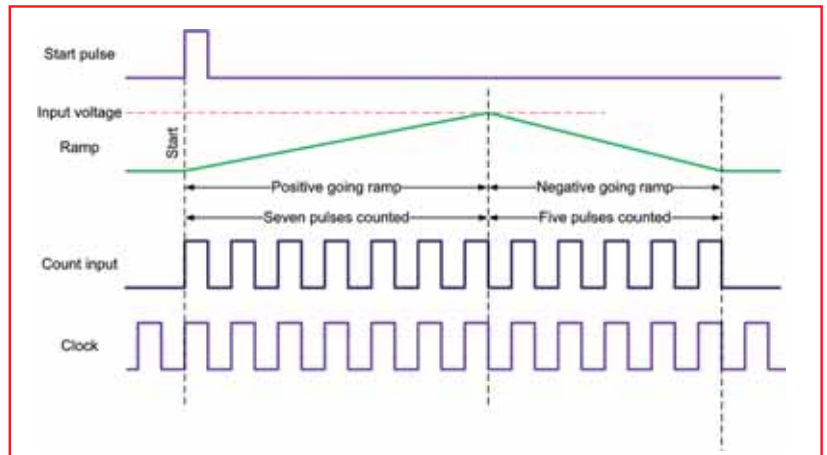


Fig.9.12. Waveforms for a dual-ramp ADC

## Dual-slope ADC

Finally, the dual-slope ADC is a refinement of the ramp-type ADC, which

## Check – How do you think you are doing?

**9.1.** Explain with the aid of a sketch what is meant by quantisation.

**9.2.** A DAC can produce 256 different output voltages. What is the resolution of the DAC?

**9.3.** How many discrete voltage levels can be produced by a 10-bit DAC?

**9.4.** Explain the advantage of an  $R-2R$  ladder DAC compared a binary-weighted DAC.

**9.5.** State the advantage of a flash ADC and suggest an application in which it can be used.

**9.6.** The binary codes produced by a four-bit bipolar analogue-to-digital converter (see Fig.9.2 and Fig.9.3) sampled at intervals of 1ms, have the following values:

Time (ms)	Binary code
0	0101
1	0100
2	0011
3	0010
4	0001
5	0000
6	1111
7	1110

If the ADC uses two's complement to represent negative values (ie, 1111 represents -1, 1110 represents -2, and so on) sketch and identify the waveform of the analogue voltage.

**For more information,  
links and other resources  
please check out our  
Teach-In website at:  
[www.tooley.co.uk/  
teach-in](http://www.tooley.co.uk/teach-in)**

involves a similar comparator arrangement, but uses an internal voltage reference and an accurate fixed slope negative ramp which starts when the positive going ramp reaches the analogue input voltage. The important thing to note about this type of ADC is that, while the slope of the positive ramp depends on the input voltage, the negative ramp falls at a fixed rate.

Hence, this type of ADC can provide a very high degree of accuracy and can also be made so that it rejects noise and random variations present on the input signal. The main disadvantage, however, is that the process of first ramping up and then ramping down requires some considerable time, and hence this type of ADC is only suitable for 'slow' signals (ie, those that are not rapidly changing). Typical conversion times lie in the range  $500\mu\text{s}$  to  $20\text{ms}$ .

**I**N this edition of **Build** we will try out some of the DAC circuits that we introduced in **Learn** (Fig.9.5). As we have seen, these can be constructed using operational amplifiers with cleverly arranged arrays of input resistors.

## Binary-weighted DAC

First enter the simple binary-weighted DAC circuit shown in Fig.9.13. This is a practical circuit based on the one shown in **Learn** Fig.9.5(a). We have used a series of logic input toggles to simulate standard logic level inputs, with the output voltage shown on a virtual voltmeter instrument.

Set various input bit patterns and monitor the resulting output voltage. Using your theory from **Learn** to calculate the expected output voltage for two different input bit patterns and then test your answers using the simulation. Take readings of the output voltage for the binary coded decimal inputs from 0 (0000) to 15 (1111) and produce a graph of your results. Fig.9.14 shows our example results plotted using Microsoft Excel.

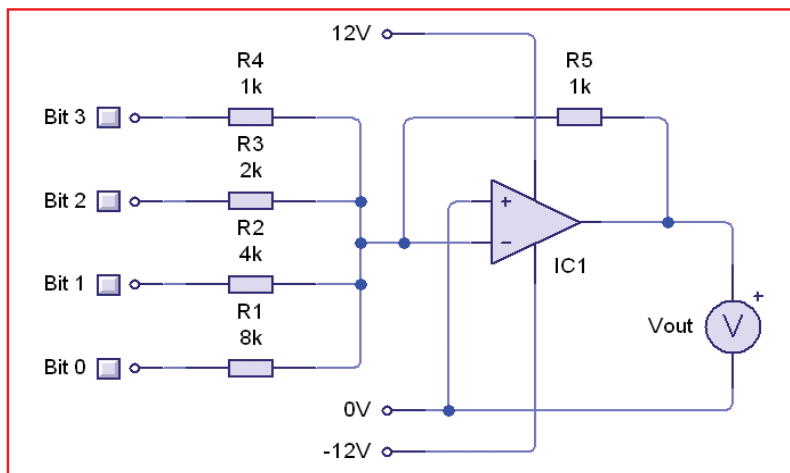


Fig.9.13. A simple four-bit binary-weighted DAC

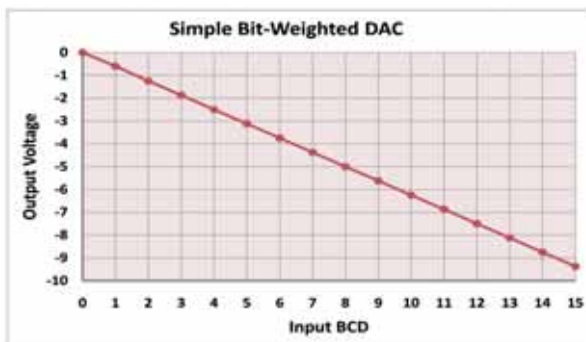


Fig.9.14. Graph of results for the simple four-bit binary-weighted DAC

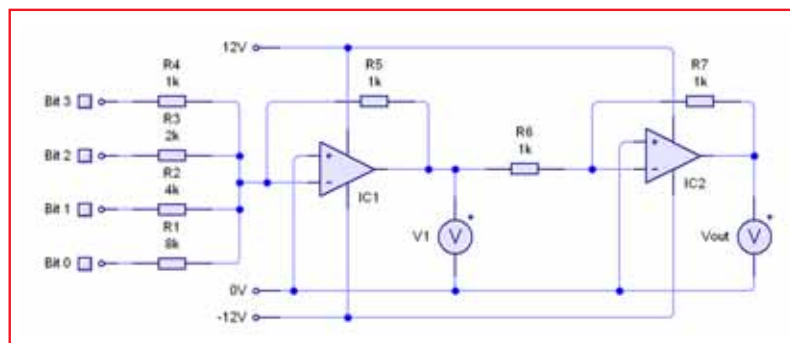


Fig.9.15. The modified four-bit binary-weighted DAC

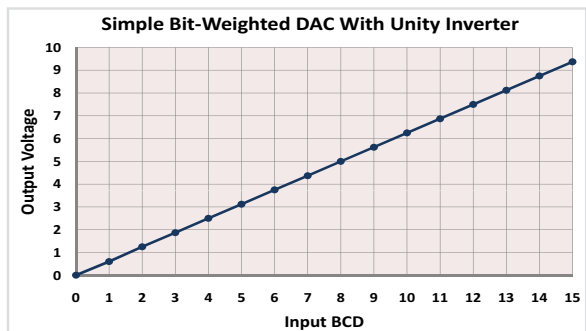


Fig.9.16. Graph of results for the modified four-bit binary-weighted DAC shown in Fig. 9.15

## Build – The Circuit Wizard way

One of the drawbacks to the simple DAC circuit is the fact that by using an operational amplifier in an inverting configuration the output is negative. A common way of dealing with this issue is to add an additional inverting amplifier with a gain of -1. This is often referred to as a *unity gain inverter*.

Modify your binary-weighted DAC circuit (Fig.9.13) to that shown in Fig.9.15 below, and experiment with changing the input bits. Notice that the output of the first operational amplifier (V1) is equal in magnitude to the output voltage ( $V_{out}$ ) but opposite in polarity. Plotting  $V_{out}$  against BCD input for this new arrangement should now look as shown in Fig.9.16.

A further modification to the binary-weighted DAC is shown in Fig.9.17. Here the output voltage is taken across the outputs of the two operational amplifiers. In this way the output voltage is effectively doubled. In fact, this method is commonly employed in many commercial DAC integrated circuit devices.

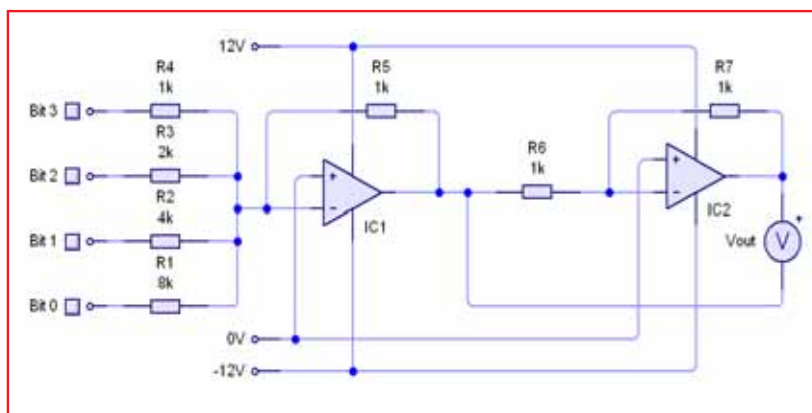


Fig.9.17. Improved binary weighted DAC with differential output

### A switch in time

In Fig.9.5(b) we described an improved DAC circuit using analogue switches. We can model this quite simply for simulation purposes using single-pole double-throw (SPDT) switches, as shown in Fig.9.18. Note that in a real circuit these would be controlled by logic inputs.

Simulate the circuit by changing the binary input patterns by toggling switches SW1 to SW4. Notice that by having a negative reference voltage we achieve a positive output voltage. Experiment by changing the

reference voltage ( $V_{ref}$ ) and note how this affects the output voltage range.

### On the ladder

Finally, we will try out a third type of DAC circuit that utilises a so called *R-2R* resistor ladder arrangement, like that shown earlier in Fig.9.5(c). As we discussed in **Learn**, there are practical advantages to this type of circuit; for example, only requiring one matched pair of resistor values. Construct the circuit shown in Fig.9.19 and experiment with the simulation.

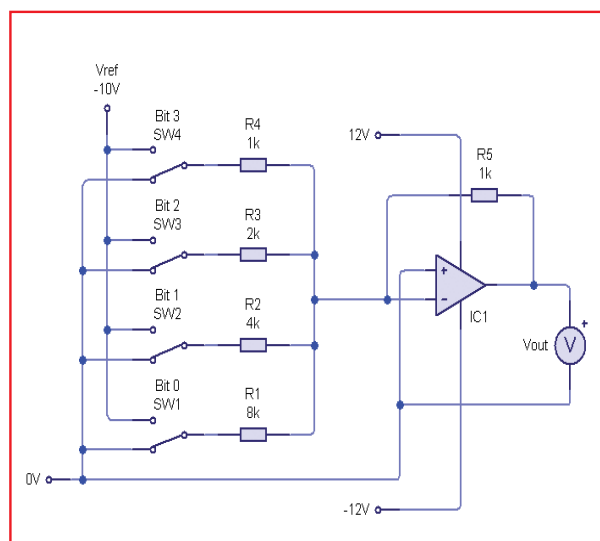


Fig.9.18. Binary-weighted DAC using analogue switches and a negative voltage reference

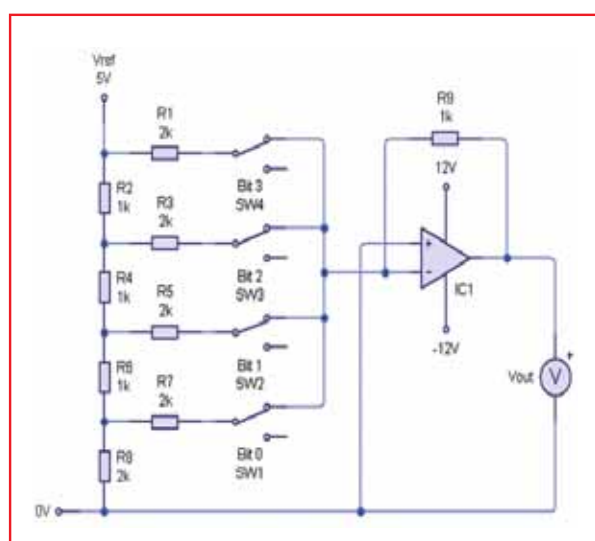


Fig.9.19. Four-bit DAC using an R-2R ladder arrangement



## Investigate

ADCs and DACs invariably take the form of integrated circuit devices. Obtain data sheets for a DAC0800 digital-to-analogue converter (these can be freely downloaded from the websites of semiconductor manufacturers like National Semiconductor and Motorola) and use them to answer each of the following questions:

1. How many data bits are used?
2. What range of supply voltages can be used with this device?
3. What package styles are used for

the device and how many connecting pins do the packages have?

4. What is the typical power consumption of the device when used with a  $\pm 10\text{V}$  supply?
5. What is the absolute maximum power dissipation for the device?
6. Which pins are used for (a) the LSB input and (b) the MSB input?
7. On what principle does the DAC operate?
8. What is the typical time taken for the output voltage to settle in response to a change at the input?

## Amaze

As you have seen, the resolution of a DAC or ADC is determined by the number of data bits that it uses. The simple four-bit DAC that you met in **Build** was only capable of generating sixteen different voltage states. By increasing the number of bits we can gain a corresponding increase in the resolution. So, a five-bit DAC can produce 32 different output voltages, a six-bit DAC is able to produce 64 different output levels, and so on.

In many applications, the digital output of an ADC is processed using a computer or some form of embedded processor (such as those used in the engine control and management systems of motor vehicles). The unit of data in a computer (ie, the number of bits that can be handled

by its processing unit as one single entity) is referred to as a *word*. So, ultimately, the digital output of an ADC must be converted into words that the computer or embedded system's processor can operate on. The number of bits in a word is an important characteristic of a particular processor family or computer architecture. This, in turn, has an impact on the size and range of the quantities that it can manipulate.

Early computers, such as the IBM PC and Commodore Amiga, as well as early console systems, such as the Sega Genesis, Super Nintendo, Mattel Intellivision, used a word length of 16-bits. This allowed them to manipulate integer numbers having a total of 65,536 different values.

## CIRCUIT WIZARD – featured in this Teach-In series

Circuit Wizard is a revolutionary new software system that combines circuit design, PCB design, simulation and CAD/CAM manufacture in one complete package. Two versions are available, Standard and Professional.

By integrating the entire design process, Circuit Wizard provides you with all the tools necessary to produce an electronics project from start to finish – even including on-screen testing of the PCB prior to construction!

\* Circuit diagram design with component library  
(500 components Standard, 1500 components Professional)

\* Virtual instruments (4 Standard, 7 Professional)

\* On-screen animation

\* PCB Layout

\* Interactive PCB layout simulation

\* Automatic PCB routing

\* Gerber export

This is the software used in our Teach-In 2011 series. Standard £61.25 inc. VAT Professional £91.90 inc. VAT. See Direct Book Service – pages 75-77 in this issue

## Answers to Check questions

9.1. See page 46 and Fig.9.1

9.2. 8-bit

9.3. 1024

9.4. Only two values are needed in the resistor chain of an  $R-2R$  ladder (the ratio of the two resistances is more important than their absolute values). The resistance values in a binary-weighted DAC can become very large when a large number of bits are used

9.5. High speed of operation. A typical application would be for use with high-quality audio and video signals (ie, analogue signals at relatively high frequencies)

9.6. Falling ramp (the analogue value falls linearly)

More powerful 32-bit computers (such as the Apple Macintosh, Pentium-based PC and popular console systems, including the Sony PlayStation, Nintendo GameCube, Xbox, and Wii) have word lengths of 32-bits and this allows them to manipulate integer numbers that can represent 4,294,967,296 different values.

However, if that's not quite enough in terms of resolution, the most recent 64-bit systems including some games consoles, such as Nintendo 64, PlayStation 2, PlayStation 3, Xbox 360, can cope with integer numbers having a staggering 18,446,744,073,709,551,616 different values!

## Next month!

In next month's Teach-In we will look at practical aspects of test instruments, measurements and testing circuits (including an introduction to PCB layout using *Circuit Wizard*).

# EPE PIC RESOURCES CD-ROM V2

Version 2 includes the EPE PIC Tutorial V2 series of Supplements (EPE April, May, June 2003)

The CD-ROM contains the following Tutorial-related software and texts:

- EPE PIC Tutorial V2 complete series of articles plus demonstration software, John Becker, April, May, June '03
- PIC Toolkit Mk3 (TK3 hardware construction details), John Becker, Oct '01
- PIC Toolkit TK3 for Windows (software details), John Becker, Nov '01

Plus these useful texts to help you get the most out of your PIC programming:

- How to Use Intelligent LCDs, Julyan Ilett, Feb/Mar '97
- PIC16F87x Microcontrollers (Review), John Becker, April '99
- PIC16F87x Mini Tutorial, John Becker, Oct '99
- Using PICs and Keypads, John Becker, Jan '01
- How to Use Graphics LCDs with PICs, John Becker, Feb '01
- PIC16F87x Extended Memory (how to use it), John Becker, June '01
- PIC to Printer Interfacing (dot-matrix), John Becker, July '01
- PIC Magick Musick (use of 40kHz transducers), John Becker, Jan '02
- Programming PIC Interrupts, Malcolm Wiles, Mar/Apr '02
- Using the PIC's PCLATH Command, John Waller, July '02
- EPE StyloPIC (precision tuning musical notes), John Becker, July '02
- Using Square Roots with PICs, Peter Hemsley, Aug '02
- Using TK3 with Windows XP and 2000, Mark Jones, Oct '02
- PIC Macros and Computed GOTOs, Malcolm Wiles, Jan '03
- Asynchronous Serial Communications (RS-232), John Waller, unpublished
- Using I2C Facilities in the PIC16F877, John Waller, unpublished
- Using Serial EEPROMs, Gary Moulton, unpublished
- Additional text for EPE PIC Tutorial V2, John Becker, unpublished

NOTE: The PDF files on this CD-ROM are suitable to use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader – included on the CD-ROM



**ONLY  
£14.75**

INCLUDING  
VAT and P&P

## EPE PIC RESOURCES V2 CD-ROM ORDER FORM

Please send me ..... (quantity)

### EPE PIC RESOURCES V2 CD-ROM

Price £14.75 each – includes postage to anywhere in the world.

Name .....

Address .....

.....

.....

..... Post Code .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ please charge my Visa/Mastercard/Maestro £ .....

Card No. ....

Card Security Code .....

(The last 3 digits on or just under the signature strip)

Valid From ..... Expiry Date .....

Maestro Issue No. ....



SEND TO:

**Everyday Practical Electronics,  
Wimborne Publishing Ltd.,  
113 Lynwood Drive, Merley, Wimborne,  
Dorset BH21 1UU.**

Tel: 01202 880299. Fax: 01202 843233.

Email: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally posted within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

**Order on-line from  
[www.epemag.com](http://www.epemag.com)  
or by Phone, Fax, Email or Post.**

## BECOME A PIC WIZARD WITH THE HELP OF EPE!

# STORE YOUR BACK ISSUES ON CD-ROMS

**FIVE YEAR DVD/CD-ROMS NOW AVAILABLE**

**ONLY £16.45 (£29.95 FOR 5 YEAR) each including VAT and p&p**

- VOL 1: BACK ISSUES** – January 1999 to June 1999  
Plus some bonus material from Nov and Dec 1998
- VOL 2: BACK ISSUES** – July 1999 to December 1999
- VOL 3: BACK ISSUES** – January 2000 to June 2000
- VOL 4: BACK ISSUES** – July 2000 to December 2000
- VOL 5: BACK ISSUES** – January 2001 to June 2001
- VOL 6: BACK ISSUES** – July 2001 to December 2001
- VOL 7: BACK ISSUES** – January 2002 to June 2002
- VOL 8: BACK ISSUES** – July 2002 to December 2002
- VOL 9: BACK ISSUES** – January 2003 to June 2003
- VOL 10: BACK ISSUES** – July 2003 to December 2003
- VOL 11: BACK ISSUES** – January 2004 to June 2004
- VOL 12: BACK ISSUES** – July 2004 to December 2004
- VOL 13: BACK ISSUES** – January 2005 to June 2005
- VOL 14: BACK ISSUES** – July 2005 to December 2005
- VOL 15: BACK ISSUES** – January 2006 to June 2006
- VOL 16: BACK ISSUES** – July 2006 to December 2006
- VOL 17: BACK ISSUES** – January 2007 to June 2007
- VOL 18: BACK ISSUES** – July 2007 to December 2007
- VOL 19: BACK ISSUES** – January 2008 to June 2008
- VOL 20: BACK ISSUES** – July 2008 to December 2008
- VOL 21: BACK ISSUES** – January 2009 to June 2009
- VOL 22: BACK ISSUES** – July 2009 to December 2009

**FIVE YEAR CD-ROM No.1 – Jan '03 to Dec '07**

**FIVE YEAR CD-ROM No.2 – Jan '04 to Dec '08**

**FIVE YEAR DVD-ROM No.3 – Jan '05 to Dec '09**

**NOTE:** These DVD/CD-ROMs are suitable for use on any PC with a DVD/CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat))

## WHAT IS INCLUDED

All volumes include the *EPE Online* editorial content of every listed issue, plus links to all the available **PIC Project Codes** for the PIC projects published in those issues. **Please note that we are unable to answer technical queries or provide data on articles that are more than five years old. Please also ensure that all components are still available before commencing construction of a project from a back issue.**

A great way to buy *EPE* Back Issues – our DVD/CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software links and web links. **Note: no free gifts are included.**

**Order on-line from**  
**[www.epemag.com](http://www.epemag.com)** (go to the UK store or US store)  
or by phone, fax, email or post

## BACK ISSUES DVD/CD-ROM ORDER FORM

Please send me the following Back Issue DVD/CD-ROMs.

Volume Numbers: .....

**Price £16.45 each, £29.95 for Five Year DVD/CD-ROMs** – includes postage to anywhere in the world.

Name .....

Address .....

Post Code .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ please charge my Visa/Mastercard/Maestro £ .....

Card No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

Valid From ..... Expiry Date .....

Maestro Issue No. ....



**SEND TO: Everyday Practical Electronics,  
Wimborne Publishing Ltd., 113 Lynwood Drive, Merley,  
Wimborne, Dorset BH21 1UU.**

Tel: 01202 880299. Fax: 01202 843233.

**E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)**

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally posted within seven days of receipt of order.



## UK readers you can SAVE 79p on every issue of EPE

How would you like to pay £3.46 instead of £4.25 for your copy of EPE ?



Well you can – just take out a one year subscription and save 79p an issue, or £9.50 over the year. You can even save £1 an issue if you subscribe for two years – a total saving of £24.00.

Overseas rates also represent exceptional value.

You also:

- Avoid any cover price increase for the duration of your subscription
- Get your magazine delivered to your door each month
- Ensure your copy, even if the newsagents sell out

Order by phone or fax with a credit card or by post with a cheque or postal order, or buy online from [www.epemag.com](http://www.epemag.com) (go to the 'UK Store').

## EPE EVERYDAY PRACTICAL ELECTRONICS

### SUBSCRIPTION PRICES

Subscriptions for delivery direct to any address in the UK: 6 months £21.95, 12 months £41.50, two years £78.00; Overseas: 6 months £25.00 standard air service or £35.00 express airmail, 12 months £48.00 standard air service or £68.00 express airmail, 24 months £91.00 standard air service or £131.00 express airmail.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Tel: 01202 880299. Fax: 01202 843233. Email: [subs@epemag.wimborne.co.uk](mailto:subs@epemag.wimborne.co.uk). Also via the Web at <http://www.epemag.com> (go to the 'UK Store').

Subscriptions start with the next available issue. We accept MasterCard, Maestro or Visa. (For past issues see the Back Issues page.)

### ONLINE SUBSCRIPTIONS

Online subscriptions, for downloading the magazine via the Internet, \$19.99US (approx. £13.00) for one year available from [www.epemag.com](http://www.epemag.com).

### SUBSCRIPTION ORDER FORM

- ☐ 6 Months: UK £21.95, Overseas £25.00 (standard air service), £35.00 (express airmail)
- ☐ 1 Year: UK £41.50, Overseas £48.00 (standard air service) £68.00 (express airmail)
- ☐ 2 Years: UK £78.00, Overseas £91.00 (standard air service) £131.00 (express airmail)

To: Everyday Practical Electronics,  
Wimborne Publishing Ltd., 113 Lynwood Drive, Merley,  
Wimborne, Dorset BH21 1UU  
Tel: 01202 880299 Fax: 01202 843233  
E-mail: [subs@epemag.wimborne.co.uk](mailto:subs@epemag.wimborne.co.uk)

I enclose payment of £ ..... (cheque/PO in £ sterling only), payable to *Everyday Practical Electronics*

☐ Please charge my Visa/Mastercard/Maestro

My card number is: .....  
Please print clearly, and check that you have the number correct

Signature .....

Card Security Code ..... Valid From Date.....  
(The last 3 digits on or just under the signature strip)

Card Ex. Date .....Maestro Issue No. ....

Name .....

Address .....

Post code ..... Tel. ....

Subscriptions can only start with the next available issue.



## LED current drivers

**A**S PART of a discussion on another contributor's LED drive circuit, frequent *EPE Chat Zone* contributor **echase** asked the following question about current source chips:

*Where can I get a simple linear constant current driver that operates at 20mA and is low drop? I guess standard 78xx series of linear regulators can be made into a constant current driver, but the drop will be a few volts at minimum. I have used an LM334 in a similar application which is cheap, simple and only drops 0.5V, but it only manages about 8mA, so it needs three in parallel to get 20mA.*

*I want to power a string of four or five LEDs in series off a 12V supply with minimal loss. A standard dropper resistor is dodgy, as variations in the 12V and the LED change the volts dropped across the resistor, and hence makes the current vary a lot.*

Later he answered his own question, with the following suggestions.

*In a post last month, I asked if there was a simple constant current driver for LEDs that behaved like a LM334, but at higher current. Well, it seems the ON Semiconductor NSI45020A is available for only 40p from Farnell and provides 20mA at up to 45V. There are 10mA, 15mA, 25mA and 30mA variants too. It's a 2-pin SOD123 SMD. Heat dissipation could be a problem if the  $V_{in}$  is more than 10V larger than the LED voltage. At 2V it does not manage quite as low a 'drop out' voltage as the LM334.*

*Also, RS do the 10mA and 15mA versions for less. They can be paralleled, so a mix of 10mA and 15mA devices provides a range of possible outputs.*

### Current drivers

Other chips were also suggested by Chat Zone contributors, specifically the LM317LZ and BCR402. So this month we will look at the need for constant current drive of LEDs, and the use of constant current regulator chips for this purpose. We will use the NSI45020A as an example device (where stated), although much of the discussion will apply to a range of similar chips from a variety of manufacturers, since echase mentions the NSI45020A is made by ON semiconductor ([www.onsemi.com](http://www.onsemi.com)).

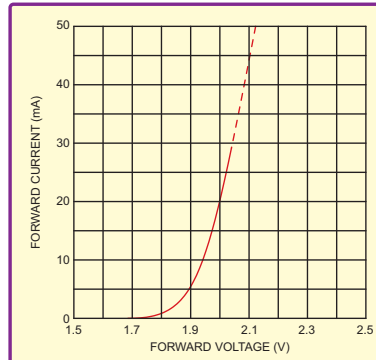


Fig.1. Relationship of forward voltage and current for an example LED (Kingbright L1334IT datasheet)

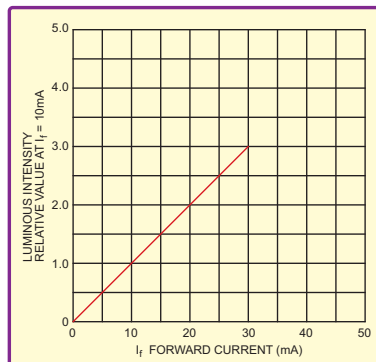


Fig.2. Relationship of forward current and luminous intensity for an example LED (Kingbright L1334IT datasheet)

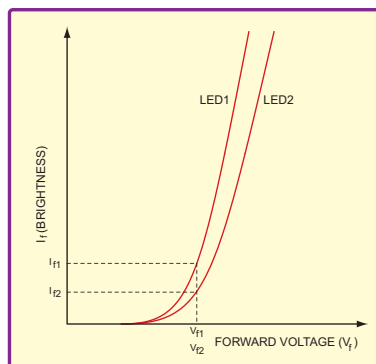


Fig.3. With the same forward voltage the LEDs may have different forward current and hence different brightness

The reason echase is asking about 'current drivers' is because LEDs are current controlled devices – in

that the light output (brightness) is just about directly proportional to the forward current (a linear relationship). So it is the current, not the voltage which sets the brightness. The characteristics of a typical high efficiency red 3mm LED (specifically the Kingbright L1334IT) are shown in Fig.1 and Fig.2.

### Relationships

The relationship between forward current and voltage for the L1334IT, which follows the typical exponential diode curve, is shown in Fig.1. Fig.2 shows the very linear relationship between forward current and luminous intensity. By implication from Fig.1, the brightness does not vary linearly with forward voltage. The LEDs characteristics shown here may be similar to those used by echase (20mA at 2V drop), although he does not give very specific details in the quoted posts.

Two individual LEDs of the same type will produce the same illumination with the same forward current ( $I_f$ ), but may have different forward voltage drops ( $V_f$ ) at this current. Possible characteristics of two individual LEDs of the same type are shown in Fig.3.

With the same forward voltage, the LEDs may have different forward current, and hence different brightness. This is a key fact that needs to be considered when designing LED drive circuits, given that it is very common when using multiple LEDs to want to have all the LEDs at the same brightness.

Two LEDs driven in parallel is shown in Fig.4. This circuit forces the LEDs to have the same forward voltage drop, which means that their forward currents and hence brightness may be different (as in Fig.3). Fig.5 shows two LEDs with separate current-limiting resistors; we can still get problems with variation between individual devices resulting in varying brightness. An example will help explain this.

Assume for the circuit in Fig.5 we have two LEDs, with LED1 having a forward voltage drop of 2V, at a forward current of 20mA. If the supply ( $V_s$ ) is 3.3V, we have  $R1 = 65\Omega$  so that  $R1$  drops 1.3V and we have 2V across LED1. If LED2 is also connected with

$R2 = 65\Omega$ , but has, say, a forward voltage drop of 2.2V, due to variations in individual device characteristics, the current in LED2 will be 16.9mA. The difference in current (15.5%) will be likely to show up as a noticeable difference in brightness.

If we use a higher supply voltage the brightness variation problem is reduced. For example, consider a 24V supply. Let's say we have  $R1 = 1.1k\Omega$  to get 20mA with a 2V drop across LED1, so the LED is driven as before. Now consider LED2 with a 2.2V drop again and  $R2 = 1.1k\Omega$ . The current in LED2 is

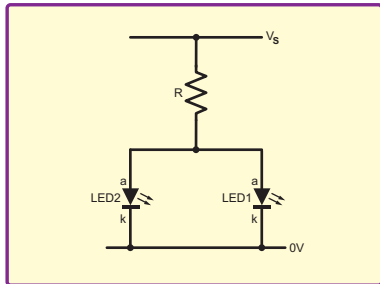


Fig. 4. Driving two LEDs in parallel

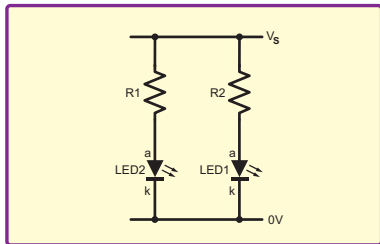


Fig. 5. Two LEDs with separate current-limiting resistors

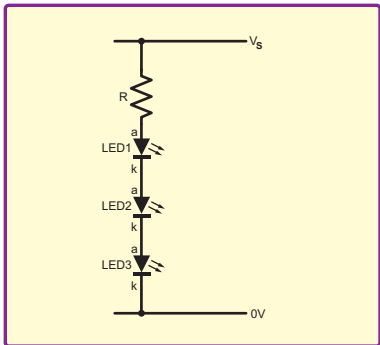


Fig. 6. Driving LEDs in series ensures the same forward current, but requires a higher drive voltage

19.8mA, almost the same as LED1, so they will be closer to being equally bright (1% difference). This comes at a price though – the total power dissipation in the two current limiting resistors is about 0.87W in the second example, which is almost twenty times higher than in the first example. The second circuit is very inefficient.

Three LEDs driven in series is shown in Fig. 6. The current through the LEDs must be equal, so their brightness will be equal. This approach requires a higher supply voltage – in this case something above 6V is needed for

three LEDs at 2V each. For a small number of LEDs (as echase requires) the supply voltage requirement may not be a serious issue.

### Potential problems

Despite the fact that the circuit in Fig. 6 guarantees equal brightness there are still a few potential problems. First, we still have individual variability of the LEDs, so if we build two copies of the circuit then the brightness might not be the same.

This may not matter too much if this is for separate projects, but if we need to drive more LEDs than we can have in series across our supply voltage (so we use several LED strings) we are back to a similar problem described in Fig. 5. As with the single LED, if the voltage across the resistor is relatively small, which it will be if we are trying to maximise the number of LEDs, then the variability will be more obvious.

Another problem with the circuit in Fig. 6 is that the LED current, and hence brightness, will depend on supply voltage. This may not be a problem if the supply is well regulated, but if the supply is taken directly from a battery, for example, this could be an issue. Furthermore, if the supply is subject to high voltage spikes, as might be the case in an automotive application, then the resistor will not protect the LEDs from excessive current.

Finally, the LEDs in the circuit in Fig. 6 may be subject to thermal runaway if conditions cause them to warm up sufficiently. LEDs have a negative temperature coefficient of forward voltage. This means that their voltage drop decreases as temperature increases.

In the circuit in Fig. 6 this would cause the voltage across the resistor to increase, increasing the LED current. The increased LED current will lead to higher power dissipation, which may further increase their temperature. This temperature increase further increases the current and so on. It is possible for this situation to result in damagingly high currents in the LEDs.

### Current driven

The problem with all the circuits described so far is that they are fundamentally *voltage* driven, but what we actually want to do is drive a specific *current* through the LEDs. Thus we need a current source, rather than the voltage source that we get with a standard power supply or battery.

An electrical source 'supplies' both current and voltage if it is doing anything useful, so when we say 'current' source we typically mean a *constant* current source. An ideal current source would power an LED – see Fig. 7.

However, practical current sources are typically circuits designed to deliver a fixed current, rather than

something like a battery or the mains, which act as actual sources of electrical energy. They obtain their power from a conventional voltage-based power supply (see Fig. 8), thus strictly speaking they are 'constant current regulators' rather than true current sources, but behave (more or less) like current sources within the circuit context for which they are designed.

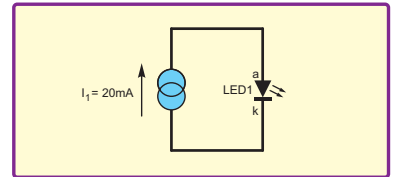


Fig. 7. An ideal current source could power an LED directly, but practical current sources are usually just current regulators

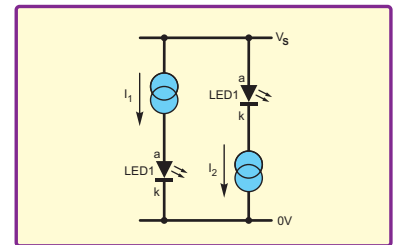


Fig. 8. Here,  $I_1$  is a current source or high side current regulator, while  $I_2$  is a current sink or low side regulator

Current sources connected to ground, through which current flows to ground, are sometimes called current sinks (see Fig. 8). The terms 'high side' and 'low side' are also used to describe current regulators which can be operated connected to the supply and ground respectively (see Fig. 8).

An ideal current source outputs a particular current irrespective of the voltage(s) required at its terminals to achieve this. This corresponds with an ideal voltage source, which can deliver any current depending on the nature of the load.

In practice, of course, voltage sources are limited in terms of current capacity – an AAA 1.5V battery will not deliver 150A into a  $0.01\Omega$  load. Similarly, a small current source chip delivering 20mA will not handle the 1000V required to push this current through a  $50k\Omega$  load!

### Operating voltage

The datasheets for current regulator chips, such as those mentioned by echase and others will specify the maximum voltage which can occur across the device. There will also be a minimum voltage which must be maintained across the chip in order for it to be able to operate, which is sometimes called 'voltage overhead' or 'dropout voltage'. This is because the internal components, such as transistors, will require this in order



to switch on and operate. Remember, for example, a bipolar transistor typically requires 0.6V to 0.7V base-emitter voltage to conduct.

To illustrate the operating voltage range for a real device, Fig.9 shows the characteristics of the NSI45020A two-terminal current regulator. The graph shows voltage across the NSI45020A against current through it. A minimum of around 2V is needed across the device for it to operate.

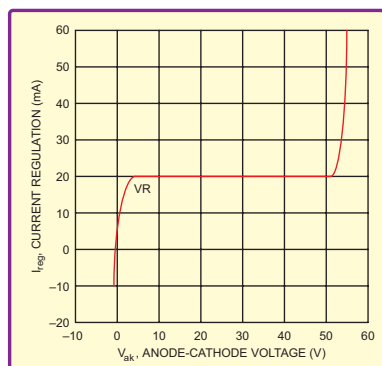


Fig.9. Graph of voltage across the NSI45020A two terminal current regulator against current through it. Current regulation occurs between 2V and 50V approximately (ON Semiconductor datasheet).

Current is constant for voltages above this, until the device breaks down at around 50V (the specified maximum voltage is 45V). This means that unlike resistor-based circuits, such as Fig.6, use of a current regulator will result in constant LED brightness for a reasonable range of supply voltage variation.

The ability of devices such as the NSI45020A to regulate up to quite high voltages (eg. 50V) can protect LEDs from supply voltage spikes. Consider the circuit in Fig.5 with a 12V supply, three 2V, 20mA LEDs and a 300Ω resistor. A 50V pulse on the supply would dramatically increase the LED current. If we assume each LED voltage drop increases to 2.4V (an arbitrary guesstimate, but the exponential diode characteristic means the LED voltage will not change much) the LED current will be around 140mA from  $(50 - (2.4 \times 3)) / 300$ .

Using the Kingbright L1334IT mentioned earlier as an example, we find the absolute maximum continuous current is 30mA, and the absolute maximum forward pulse current is 160mA for a 0.1ms pulse width. A 50V pulse causing 140mA for significantly longer than this may damage the LEDs. Using a current regulator that can regulate up to 45V would maintain the 20mA LED current during the 50V spike. The current regulator will experience increased power dissipation during the surge, but with correct thermal design (board layout/heatsinking) it should not be damaged.

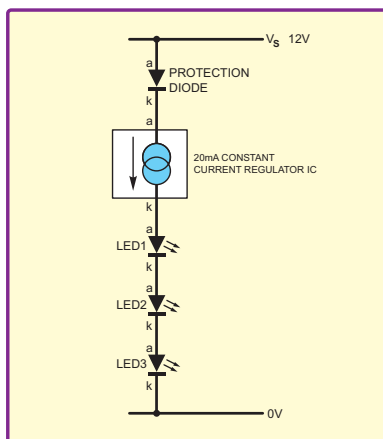


Fig.10. Example LED drive circuit using a current regulator IC

Looking at the graph in Fig.9, we see that current in the NSI45020A increases very rapidly with increasing reverse voltage across the device. It follows that the NSI45020A is likely to be damaged by reverse connections, and therefore in systems where supply reversal may occur (eg, incorrectly connected batteries) a reverse protection diode should be used.

A perfect current source would prevent LEDs from being subject to thermal runaway because the current would not vary with temperature. Real current regulators are likely to have some temperature dependency. Fortunately, it is possible to ensure a small negative coefficient, which prevents thermal runaway (the NSI45020A and similar devices provide this). The regulator temperature coefficient should not be large because this may result in brightness variation with temperature.

As mentioned above, current regulators have an overhead voltage, above which they will operate correctly. This may be specified at something below the full regulated current (say 85%). Therefore, in practice, it is best to use the device at a voltage a bit above this, so that the device is into the full regulation part of the characteristic (the flat line section on Fig.9). For the NSI45020A, about 3.5V would be reasonable.

Ideally, the voltage across the regulator will not be much larger than this minimum because power dissipation increases, and efficiency decreases, for larger voltage drops. However, voltage dropped depends on the supply voltage and number of LEDs used, so some regulator dissipation will be unavoidable. If efficiency is particularly important, then switch-mode LED driver chips can be used, but these circuits are more complex and expensive.

The number of LEDs which can be driven can be calculated by subtracting the overhead voltage and reversal protection diode forward voltage (if used) from the supply

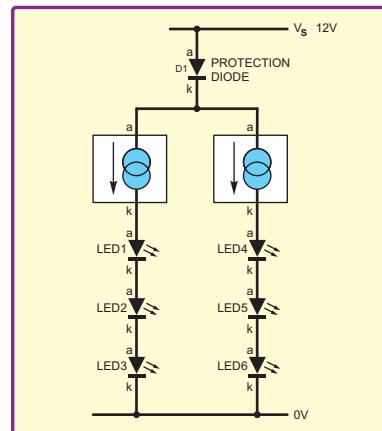


Fig.11. Driving more LEDs

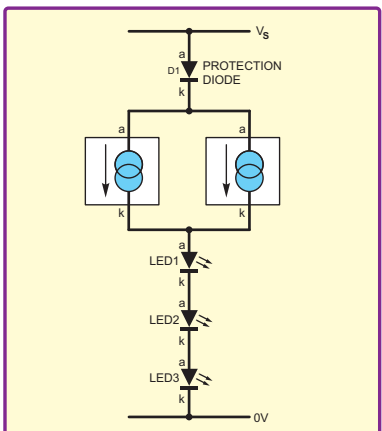


Fig.12. Driving at higher current

voltage, and then dividing this value by the expected LED voltage drop at the regulated current. For example, for a 12V supply, we assume a regulator drop of 3.5V, protection diode drop of 0.7V and an LED forward drop of 2V at 20mA; the maximum number of LEDs is  $(12 - 3.5 - 0.7) / 2$ , which gives 3.9 LEDs.

Allowing a slightly lower regulator voltage would make driving 4 LEDs possible, but some LED dimming may occur if the supply voltage dropped, due to operating close to the 'knee' in the regulator characteristic. Using three LEDs would allow more supply variation without the LEDs dimming. With three LEDs, the regulator would drop 5.3V and dissipate around 110mW. This is within the capabilities of the NSI45020A and similar devices. A suitable circuit is shown in Fig.10.

To drive more LEDs, several regulator ICs can be used to drive parallel LED strings, as shown in Fig.11 (typically only one reverse protection diode would be needed). To increase current drive, current regulator ICs can usually be operated in parallel (see Fig.12). Unlike parallel LEDs (Fig.4), which may current hog; they keep to their specified regulation current (within the operating voltage range).

# EPE PIC PROJECTS VOLUME 1 MINI CD-ROM

A plethora of 20 'hand-PICKed' PIC Projects from selected past issues of *EPE*  
Together with the PIC programming software for each project plus bonus articles

The projects are:

## **PIC-Based Ultrasonic Tape Measure**

You've got it taped if you PIC this ultrasonic distance measuring calculator

## **EPE Mind PICKler**

Want seven ways to relax? Try our PIC-controlled mind machine!

## **PIC MIDI Sustain Pedal**

Add sustain and glissando to your MIDI line-up with this inexpensive PIC-controlled effects unit

## **PIC-based MIDI Handbells**

Ring out thy bells with merry tolling – plus a MIDI PIC-up, of course!

## **EPE Mood PICKer**

Oh for a good night's sleep! Insomniacs rejoice – your wakeful nights could soon be over with this mini-micro under the pillow!

## **PIC Micro-Probe**

A hardware tool to help debug your PIC software

## **PIC Video Cleaner**

Improving video viewing on poorly maintained TVs and VCRs

## **PIC Graphics LCD Scope**

A PIC and graphics LCD signal monitor for your workshop

## **PIC to Printer Interface**

How to use dot-matrix printers as data loggers with PIC microcontrollers

## **PIC Polywhatsit**

A novel compendium of musical effects to delight the creative musician

## **PIC Magick Musick**

Conjure music from thin air at the mere untouching gesture of a fingertip

## **PIC Mini-Enigma**

Share encrypted messages with your friends — true spymaster entertainment

## **PIC Virus Zapper**

Can disease be cured electronically? Investigate this controversial subject for yourself

## **PIC Controlled Intruder Alarm**

A sophisticated multi-zone intruder detection system that offers a variety of monitoring facilities

## **PIC Big-Digit Display**

Control the giant ex-British Rail platform clock 7-segment digits that are now available on the surplus market

## **PIC Freezer Alarm**

How to prevent your food from defrosting unexpectedly

## **PIC World Clock**

Graphically displays world map, calendar, clock and global time-zone data

## **PICAXE Projects**

A 3-part series using PICAXE devices – PIC microcontrollers that do not need specialist knowledge or programming equipment

## **PIC-based Tuning Fork and Metronome**

Thrill everyone by at long last getting your instrument properly tuned!

## **Versatile PIC Flasher**

An attractive display to enhance your Christmas decorations or your child's ceiling



NOTE: The PDF files on this CD-ROM are suitable to use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader – included on the CD-ROM

**ONLY  
£14.75**

INCLUDING  
VAT and P&P

## EPE PIC PROJECTS CD-ROM ORDER FORM

Please send me ..... (quantity)

### **EPE PIC PROJECTS VOL 1 CD-ROM**

Price £14.75 each – includes postage to anywhere in the world.

Name .....

Address .....

..... Post Code .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ please charge my Visa/Mastercard/Maestro £ .....

Card No. ....

Card Security Code .....

(The last 3 digits on or just under the signature strip)

Valid From ..... Expiry Date .....

Maestro Issue No. ....



SEND TO:

**Everyday Practical Electronics,  
Wimborne Publishing Ltd.,**

**113 Lynwood Drive, Merley, Wimborne,  
Dorset BH21 1UU.**

Tel: 01202 880299. Fax: 01202 843233.

Email: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally posted within seven days of receipt of order.  
Send a copy of this form, or order by letter if you do not wish to cut your issue.

**Order on-line from  
[www.epemag.com](http://www.epemag.com)  
or by Phone, Fax, Email or Post.**

**BECOME A PIC PROJECT BUILDER WITH THE HELP OF EPE!**

# EPE PIC PROJECTS VOLUME 2 CD-ROM

A plethora of 20 'hand-PICKed' PIC projects from selected past issues of *EPE*  
Together with the PIC programming software for each project.

The projects are:

## **BioPIC Heartbeat Monitor**

Take a peek at the rhythmic waveforms that keep you ticking

## **EPE Moodloop**

Have a relaxing 'field-day' (or night) with our PIC-based brainwave generator!

## **EPE Morse Code Reader**

Multi-function Morse Code translation and learning aid; standalone plus optional PC interface!

## **Freebird Glider Control**

An automatic flight attitude control system for your free-flight model glider!

## **IC Tester**

Let a PIC and PC check the health of your digital logic chips!

## **Interior Lamp Delay**

Don't you just hate being plunged into darkness when the car door shuts? Here's a solution! Plus lights-on alarm and battery saver!

## **Multi-Channel Transmission System**

An 8 to 16-channel 2-wire PIC-based signalling link, with optional interface for private phone systems!

## **Musical Sundial**

When the sun has got his hat off (hip-hip-hip-hooray) there's no shadow of doubt you'll find fun with our PIC-based musical garden gnomon!

## **PIC-A-Colour Game**

PIC your wits against a colourful code-setting mastermind!

## **PIC-based Brainbot Buggy**

A low-cost, easy-build buggy that has a mind of its own!

## **PIC-based Fido Pedometer**

Keeping track of how far you've walked!

## **PIC-based Intelligent Garden Lights**

An easy-to-build lights controller that knows when it's time to switch off!

## **PIC-based Remote Control IR Decoder**

Allows PIC programming enthusiasts to remotely control their designs!

## **PIC-based Monitored Dual PSU**

Workshop power supply with multiple options and monitoring of voltage and current using a PIC microcontroller plus LCD readout!

## **PIC Pocket Battleships**

Become a Sea Lord with our interpretation of the age-old pen and paper game!

## **PIC Random LED Flasher**

Enjoy the fun of an interesting and attractive pattern display!

## **PICronos LED Wall Clock**

Ancient and modern techniques display timely brilliance on a grand scale!

## **PIC Virus Zapper MK.2**

An alternative method that could keep those bugs at bay!

## **Time and Date Generator**

Add time and date codes to your CCTV security monitor!

## **Water Monitor**

How costly is it to keep your garden watered? Find out and control it!



NOTE: The PDF files on this CD-ROM are suitable to use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader

**ONLY  
£14.75**

INCLUDING  
VAT and P&P

## EPE PIC PROJECTS VOL. 2 CD-ROM ORDER FORM

Please send me ..... (quantity)

### **EPE PIC PROJECTS VOL 2 CD-ROM**

Price £14.75 each – includes postage to anywhere in the world.

Name .....

Address .....

.....

.....

..... Post Code .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ please charge my Visa/Mastercard/Maestro £ .....

Card No. ....

Card Security Code .....

(The last 3 digits on or just under the signature strip)

Valid From ..... Expiry Date .....

Maestro Issue No. ....



SEND TO:

**Everyday Practical Electronics,  
Wimborne Publishing Ltd.,**

**113 Lynwood Drive, Merley, Wimborne,  
Dorset BH21 1UU.**

Tel: 01202 880299. Fax: 01202 843233.

Email: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally posted within seven days of receipt of order.  
Send a copy of this form, or order by letter if you do not wish to cut your issue.

**Order on-line from  
[www.epemag.com](http://www.epemag.com)  
or by Phone, Fax, Email or Post.**

**BECOME A PIC PROJECT BUILDER WITH THE HELP OF EPE!**





# Practically Speaking

Robert Penfold looks at the Techniques of Actually Doing it!

A multi-range test meter, or 'multimeter' as these devices are generally called, used to be a major investment. A professional grade instrument cost a sum that was equivalent to several weeks' wages for 'mister average'. The better low-cost types were less rugged and probably a little less accurate as well, but were good enough for amateur and even some professional use.

However, by the standards of the day they still represented a significant outlay. A multimeter was something that you bought after gaining some experience at electronics construction, if you could afford one.

Some types of test equipment are still relatively expensive today, but non-professional multimeters have gone the way of many electronic gadgets, and can now be obtained at quite low prices. On a certain well-known auction site it is possible to buy them direct from the Far East for around three pounds including postage.

If you are not prepared to wait a few weeks for delivery, they can be obtained in the UK for not a great deal more. At these prices, it is probably better to invest in a multimeter sooner rather than later.

## Speed reading

There are two main types of multimeter; the analogue and digital varieties (Fig.1). The analogue type has the readout provided by a conventional moving meter that has a fine pointer 'needle' and a scale. The digital type has a digital readout that on the lower cost units is typically a three or three and a half digit type.

While it might seem surprising that analogue multimeters are still available in this day and age, they do have a few advantages. Where a high degree of accuracy is not needed it is possible to read an analogue multimeter at a glance. You can see immediately whether the reading is 'in the right ballpark', and that is often all you need to know.

An analogue instrument is also easier to use when adjusting a preset resistor to obtain a certain voltage at a test point, or something of this general nature. As you adjust the control, the

meter's pointer responds immediately and smoothly to the changes.

Using a digital multimeter for this type of thing you tend to get a confusing set of readings. It then becomes a matter of adjusting the control, waiting for the reading to settle, adjusting the control again, waiting again, and so on until eventually the required reading is obtained.

In a similar vein, if a voltage is fluctuating slowly, an analogue instrument will follow and show the changes. In the same situation, a digital type tends to become a random number generator!

Another advantage of analogue multimeters is that they can still measure voltage and current if the battery goes flat. The battery is only needed for resistance (ohms) measurement, and probably for additional features such as a continuity buzzer and semiconductor testing.

A disadvantage of analogue multimeters is that they often require two batteries. Typically, there will be one or two 1.5V batteries plus a higher voltage type, such as a PP3 9V battery. In most cases, the higher voltage battery is only required for the highest resistance ranges.

## On reflection

Although the analogue type has its advantages and is still preferred by some, a digital instrument is generally the better choice. Even a three-digit type is likely to offer better accuracy than that provided by the pointer and scale of an analogue multimeter. Small analogue types are handy devices, but the longer scale of a larger type can be read more accurately.

Most analogue multimeters have an arc with a mirror finish mixed in with the various scales. This aids reading accuracy by combating parallax problems due to the pointer being slightly raised from the scale plate. Accurate readings are obtained when the pointer covers its reflection in the mirrored part of the scale, but for highly accurate readings a digital type is still likely to be quicker, easier, and more precise.

Many multimeters have a three and a half digit display, which is a type where the maximum reading is 1999. The extra 'half' digit gives better results on awkward readings such as 1.295V. This is no problem with a three and a half digit display, where it fits in nicely on the 1.999V range.



Fig.1. The analogue meter on the left cost about the same as the digital type on the right, and they offer similar facilities. The digital type is smaller, more rugged, and probably offers slightly better accuracy

With a three-digit type, it would have to be read on the 10V range, and would be displayed as 1.29V. The loss of a digit from the reading is unlikely to be of major importance, but most multimeters, whether digital or analogue, provide significantly reduced accuracy at low readings. I would always opt for a three and a half digit type, but in practice it is likely that both types will do a perfectly good job.

### Input resistance

Digital multimeters tend to have the advantage of being more rugged. The moving coil meter movement of an analogue multimeter is very delicate, and dropping any instrument that contains a moving coil meter is definitely not a good idea!

The meter movements in analogue multimeters are relatively large, but have been designed to respond to minute amounts of current. This makes them especially vulnerable. A severe jolt can impair the accuracy of the meter, and in a severe case the pointer can be dislodged from its bearings.

The vast majority of analogue multimeters are passive devices when measuring voltage. In other words, there is no amplifier between the test point and the meter movement. There is just a resistor in series with the meter, and the value of this resistor determines the full-scale voltage. The power needed to drive the meter movement is obtained from the test point.

This is a far from ideal approach, since the power tapped off by the meter can significantly load the voltage at the test point, giving a misleadingly low reading. The meter needs to be as sensitive as possible in order to minimise loading effects, but there is a limit to the sensitivity that can be obtained while maintaining a reasonable level of ruggedness.

The sensitivity of analogue meters is expressed in terms of so many kilohms-per-volt (k/V), and the cheaper types usually have a rating of one or two kilohms per volt. If (say) a 1k/V meter is set to the 10V range, it will have a resistance of 10k $\Omega$ , and it will draw one milliamp from the test circuit with a full-scale reading. This is of no consequence for something like checking the output voltage of a battery or a battery eliminator, but with modern low-current circuits it is likely to give frequent misleading readings when making voltage checks at various parts of a circuit.

The more expensive analogue multimeters usually have a sensitivity of 20k/V, which gives a resistance of 200k $\Omega$  on the 10V range, and requires just 50 $\mu$ A for a full scale reading. This is good enough to ensure that loading effects will only occasionally have to be taken into account when testing circuits.

Small analogue units that have low sensitivities are fine for things like checking batteries, and testing switches using a resistance range, but a larger and more expensive type is better suited to making voltage checks on circuits. In terms of input resistance, digital multimeters are even better though. Most have a constant input resistance of about 10 or 20M $\Omega$ , which is high enough to ensure that it will hardly ever be necessary to take loading effects into account.

### Resistance ranges

In general, the cheaper multimeters have fewer measuring ranges than the more upmarket types, and this tends to be especially noticeable with the resistance ranges. Most multimeters can measure quite low resistances without any problems, and it is the higher ranges above a megohm that tend to be absent on the budget models. High value resistors are not used a great deal in modern electronics, but they are used to a significant extent in multimeters, and it is probably worth paying a bit extra for a meter that covers resistances up to at least 10 or 20M $\Omega$ .

Resistance measurement using a digital multimeter is very straightforward, but there are a few complications with the resistance range of analogue types. With a suitable range selected, the two test prods are connected together and a control on the multimeter is adjusted to zero the reading.

However, zero for resistance measurements is at what is normally the full scale reading, and the resistance scales read in reverse. Furthermore, they are non-linear, with the scales getting increasingly cramped towards the high end of each range. This is not to say that an analogue multimeter cannot provide accurate resistance readings, but you do need to keep your wits about you in order to avoid reading errors, and it is all a bit primitive in comparison to a resistance measurement using a digital type.

It is not just extra resistance ranges that are provided by the more upmarket meters, and there will usually be extra ranges for some other types of measurement, and extra facilities. Even the cheaper multimeters often sport facilities such as diode and transistor testing, and possibly a continuity tester feature.

It is possible to test for continuity using a low resistance range, but a facility specifically for that task will normally indicate continuity by sounding a buzzer. This is more convenient in use as it avoids the need to look away from the test prods.

The more expensive multimeters (Fig.2) will usually have the ability to measure things that are not available at all with the cheaper types. Ranges for



*Fig.2. This mid-price digital meter has more ranges and facilities than a budget unit, including six capacitance ranges. It also has a large and easily read display*

measuring AC current are often absent from budget multimeters, but should be included with the more expensive meters. Measuring AC current is something you might never need to do, so the absence of this facility is probably not of great importance.

The capacitance ranges provided by the more expensive digital multimeters are a different matter, and the ability to check capacitors with values from a few picofarads to several hundred microfarads is a huge bonus.

### Fluke-alikes

Moving still further up the price range, there are units that look similar to the Fluke range of professional meters, and in most cases they offer a similar range of facilities. The additional features on offer usually include frequency and temperature measurement. Temperature measurement is accomplished using a separate probe, and it is used to check that power devices are not in danger of overheating. Additional features such as these are potentially useful, but the laws of diminishing returns tend to apply here. It can cost quite a lot extra for features that you might never use in earnest.

The more upmarket meters usually have auto-ranging. In other words, you just select the desired function such as DC voltage, connect the meter to the test points, and the meter does the rest. It will select the best range, put the decimal point in the right place, and indicate the units in use.

Apart from convenience, this has the advantage of avoiding the risk of overloads. There is no danger of (say) selecting a low voltage range and connecting the meter to a hundred volts or so, because the user does not select the range.

However, it is still essential to select the right function. Selecting the resistance function and connecting the meter to a few hundred volts might not have a happy outcome! All multimeters have some built-in protection against overloads and misuse, but as always with this type of thing, it is best if it is never given the 'acid test'.

### Pen name

I am not entirely sure that the 'pen' name is entirely appropriate for this type of multimeter (Fig.3), which is indeed held like a pen, but in terms of weight and bulk tends to be very much bigger than any normal pen. More out of curiosity, than because I thought it would be a valuable piece of test gear; I bought one of these many years ago when they first came out. I actually used it more than my normal analogue and digital units, and eventually wore it out.

Pen style multimeters are very convenient for many types of testing because the display is very close to the test point, and the meter itself is effectively one of the test prods. This largely avoids the tendency for the test prod to slip from the test point while your attention is required to read the display.

They are probably not a good choice for a first multimeter though, as they are relatively expensive and have some drawbacks. Auto-ranging is a standard feature of these units, but the specification can be relatively modest in other respects. There will usually be AC and DC voltage ranges, resistance measurement, and perhaps a facility for testing diodes, but there will probably be little or nothing else.

### In use

In order to get the most from a multimeter it is necessary to have a fair amount of technical knowledge. Even if a circuit diagram includes test voltages, without a reasonable understanding of electronics theory it is unlikely that any readings that are wide of the mark will enable the fault to be pinpointed.

On the other hand, it is possible to make some general tests that might help to locate the problem. A low resistance range or a continuity tester function can be used to check switches, test for broken tracks on a circuit board, and test for bad soldered connections. Using a DC voltage range it is possible to check that the battery is providing an adequate voltage, and that the voltage is getting through to the circuit board.



Fig.3. A pen style multimeter such as this offers a convenient way of making voltage checks. However, prices are relatively high and the range of features provided tends to be quite limited

It is also possible to check some components. Obviously, resistors can be checked using the resistance ranges, but bear in mind that components cannot be checked while they are fitted on the circuit board. When checking any component, at most, there must be no more than one lead connected to the board.

When testing high value resistors, it is important not to touch both of the metal prods or component leads. Doing so results in the resistance through your body being connected in parallel with the test component, which could significantly reduce readings.

Most multimeters can be used to check transistors and diodes, and it is probably worth paying a little extra to get one that can check capacitors as well.

One final point is that the test leads/prods supplied with low cost multimeters are usually of the 'cheap and cheerful' variety. This is not really surprising, since a pair of high quality prods costs more than most budget multimeters! Even so, if you use a multimeter a great deal it is probably worth investing in a higher quality type, such as the ones that have spring-loaded claws that can grip component leads, tags and solder pins.

www.epemag.com

## SHERWOOD ELECTRONICS

Buy 10 x £1 Special Packs and choose another one FREE

SP1	15 x 5mm Red Leds	SP131	2 x TL071 Op-amps
SP2	12 x 5mm Green Leds	SP133	20 x 1N4004 diodes
SP3	12 x 5mm Yellow Leds	SP134	15 x 1N4007 diodes
SP5	20 x 5mm 1 part Led clips	SP135	5 x Miniature slide switches
SP6	15 x 3mm Red Leds	SP136	3 x BFY50 transistors
SP7	12 x 3mm Green Leds	SP137	4 x W005 1.5A bridge rectifiers
SP8	10 x 3mm Yellow Leds	SP138	20 x 2.2/63V radial elect caps
SP9	20 x 3mm 1 part Led clips	SP142	2 x Cmos 4017
SP10	100 x 1N4148 diodes	SP143	5 Pairs min. croc.clips (Red+Blk)
SP11	30 x 1N4001 diodes	SP144	5 Pairs min. croc.clips (assorted colours)
SP12	30 x 1N4002 diodes	SP146	10 x 2N3704 transistors
SP18	20 x BC182B transistors	SP151	4 x 8mm Red Leds
SP20	20 x BC184B transistors	SP152	10 x 8mm Green Leds
SP22	20 x BC549B transistors	SP153	4 x 8mm Yellow Leds
SP24	4 x Cmos 4001	SP154	15 x BC548B transistors
SP25	4 x 555 timers	SP160	10 x 2N3904 transistors
SP26	4 x 741 Op-amps	SP161	10 x 2N3906 transistors
SP28	4 x Cmos 4011	SP164	2 x C106D thyristors
SP29	3 x Cmos 4013	SP165	2 x LF351 Op-amps
SP33	4 x Cmos 4081	SP166	20 x 1N4003 diodes
SP34	20 x 1N914 diodes	SP167	5 x BC107 transistors
SP36	25 x 10/25V radial elect caps	SP168	5 x BC108 transistors
SP37	12 x 100/35V radial elect caps	SP172	3 x Standard slide switches
SP38	15 x 47/25V radial elect caps	SP173	10 x 220/25V radial elect caps
SP39	10 x 470/16V radial elect caps	SP174	20 x 22/25V radial elect caps
SP40	15 x BC237 transistors	SP177	20 x 1/63V radial elect caps
SP41	20 x Mixed 0.25W CF resistors	SP178	10 x 1A 20mm quick blow fuses
SP42	200 x Mixed 0.25W CF resistors	SP178	10 x 2A 20mm quick blow fuses
SP47	5 x Min. PB switches	SP181	5 x Phono plugs - assorted colours
SP49	4 x 4 metres stranded core wire	SP182	20 x 4.7/63V radial elect caps
SP102	20 x 8 pin DIL sockets	SP183	20 x BC547B transistors
SP103	15 x 14 pin DIL sockets	SP186	8 x 1M horizontal trim pots
SP104	15 x 16 pin DIL sockets	SP189	4 x 4 metres solid core wire
SP109	15 x BC557B transistors	SP192	3 x Cmos 4066
SP112	4 x Cmos 4093	SP195	3 x 10mm Yellow Leds
SP115	3 x 10mm Red Leds	SP197	6 x 20 pin DIL sockets
SP116	3 x 10mm Green Leds	SP198	5 x 24 pin DIL sockets
SP118	2 x Cmos 4047	SP199	4 x 2.5mm mono jack plugs
SP124	20 x Assorted ceramic disc caps	SP200	4 x 2.5mm mono jack sockets
SP130	100 x Mixed 0.5W CF resistors		

### RESISTOR PACKS - C.Film

RP3	5 each value - total 365 - 0.25W	£3.55
RP7	10 each value - total 730 - 0.25W	£4.85
RP10	1000 popular values - 0.25W	£6.90
RP4	5 each value - total 305 - 0.5W	£4.45
RP8	10 each value - total 610 - 0.5W	£7.20
RP11	1000 popular values - 0.5W	£9.75


Catalogue available £1 inc. P&P or **FREE** with first order.  
P&P £2.25 per order. NO VAT  
Cheques and Postal Orders to:  
**Sherwood Electronics,**  
**10 NEWSTEAD STREET,**  
**MANSFIELD, NOTTS.**  
**NG19 6JJ**



# ELECTRONICS MANUALS ON CD-ROM £29.95 EACH

## ELECTRONICS SERVICE MANUAL

## MODERN ELECTRONICS MANUAL

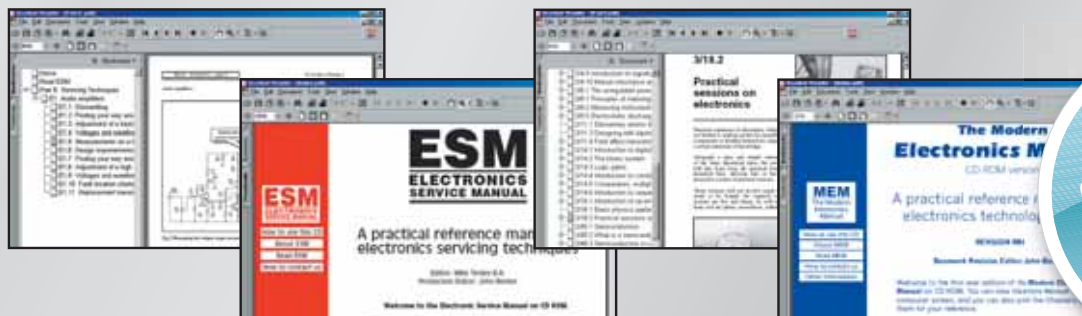

**SPECIAL OFFER**  
Order both Manuals together and  
**SAVE £10**

### Everything you need to know to get started in repairing electronic equipment

● Around 900 pages ● Fundamental principles ● Troubleshooting techniques ● Servicing techniques ● Choosing and using test equipment ● Reference data ● Manufacturers' web links ● Easy-to-use Adobe Acrobat format ● Clear and simple layout ● Vital safety precautions ● Professionally written ● Supplements

**SAFETY:** Safety Regulations, Electrical Safety and First Aid. **UNDERPINNING KNOWLEDGE:** Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and manufacturers' Data, etc. **PRACTICAL SKILLS:** Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components. **TEST EQUIPMENT:** How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc. **SERVICING TECHNIQUES:** The Manual includes vital guidelines on how to Service Audio Amplifiers. The Supplements include similar guidelines for Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc. **TECHNICAL NOTES:** Commencing with the IBM PC, this section and the Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc. **REFERENCE DATA:** Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, optoelectronic Devices, etc.

### The essential reference work for everyone studying electronics

● Over 800 pages ● In-depth theory ● Projects to build ● Detailed assembly instructions 1 Full components checklists ● Extensive data tables ● Manufacturers' web links ● Easy-to-use Adobe Acrobat format ● Clear and simple layout ● Comprehensive subject range ● Professionally written ● Supplements

**BASIC PRINCIPLES:** Electronic Components and their Characteristics; Circuits Using Passive Components; Power Supplies; The Amateur Electronics Workshop; The Uses of Semiconductors; Digital Electronics; Operational Amplifiers; Introduction to Physics, including practical experiments; Semiconductors and Digital Instruments.

**CIRCUITS TO BUILD:** The Base Manual describes 12 projects including a Theremin and a Simple TENS Unit.

**ESSENTIAL DATA:** Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

**EXTENSIVE GLOSSARY:** Should you come across a technical word, phrase or abbreviation you're not familiar with, simply look up the glossary and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety** and provides web links to component and equipment **Manufacturers and Suppliers**.

Full contents list available online at: [www.epemag.com](http://www.epemag.com)

**SUPPLEMENTS:** Additional CD-ROMs each containing approximately 500 pages of additional information on specific areas of electronics are available for £19.95 each. Information on the availability and content of each Supplement CD-ROM will be sent to you.

**PRESENTATION:** CD-ROM suitable for any modern PC. Requires Adobe Acrobat Reader which is included on the CD-ROM.

Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Tel: 01202 880299. Fax: 01202 843233.

### PLEASE send me

- ☐ THE MODERN ELECTRONICS MANUAL CD-ROM  
☐ ELECTRONICS SERVICE MANUAL CD-ROM

I enclose payment of £29.95 (for one manual) or £49.90 for both manuals (saving £10 by ordering both together).

FULL NAME .....

ADDRESS .....

POSTCODE .....

SIGNATURE .....

- ☐ I enclose cheque/PO in UK pounds payable to Wimborne Publishing Ltd.  
☐ Please charge my Visa/Mastercard/Maestro

Card No ..... Maestro Issue No .....

Valid From ..... Expiry Date ..... Card Security Code .....  
(The last 3 digits on or just under the signature strip)

### ORDER FORM

Simply complete and return the order form with your payment to the following address:

**Wimborne Publishing Ltd,  
113 Lynwood Drive, Merley, Wimborne,  
Dorset BH21 1UU**

Price includes postage to anywhere in the World

We will happily exchange any faulty CD-ROMs but since the content can be printed out we do not offer a refund on these items.



**Your CD-ROM(s) will be posted to you by first class mail or airmail, normally within four working days of receipt of your order**



# Max's Cool Beans

By Max The Magnificent

## My Boomerang won't come back

As you may recall, in my previous column I waffled on about a Geiger counter kit that I had purchased and constructed. The kit looks really cool, but sadly it doesn't count. When I turn it on, the blue LED lights up and stays on, but nothing else happens. I've since learned that the LED should only flash on to indicate a radiation event.

I've been asking around on the Internet and have been in touch with several other people who have the same kit. One person jokingly said that my remark 'my Geiger counter doesn't count' reminded him of the song 'my boomerang won't come back.' As fate would have it, this is a little ironic, because my counter is currently in Australia. Some say that their units behave just like mine – that is, they don't work at all – and these folks aren't very happy about it. Others say that their kits work just fine. One person pointed me to a video on YouTube ([www.youtube.com/watch?v=Q58-l1KYrTg](http://www.youtube.com/watch?v=Q58-l1KYrTg)) that shows an identical unit working as you would expect. Whoever took the video has the Geiger counter sitting close to an orange Fiesta Ware plate that was naturally radioactive (this variety of Fiesta Ware was discontinued because of it). The counter clicks away at a fairly high rate, which falls when the plate is moved further away toward the end of the video.

I'm not all that familiar with the way in which these things perform their magic. Fortunately, I have a friend called David Ashton who lives 'down under' in Australia. David is an electronics expert who can fix almost anything. So, at his invitation I shipped my Geiger counter to him (the post cost only \$5, which I thought was an amazingly good deal). A few days ago, David emailed me to say that the unit had arrived, so now I am all aquiver in anticipation.

One of the problems I ran into when I first constructed the Geiger counter was that I didn't know how it should behave, and how often it should trigger due to background radiation. I simply didn't have a radiation source to hand with which to test it.


I mentioned all of this in my postings on the Internet. Shortly after I'd returned from dispatching my Geiger counter to Australia, I received an email from Nick Bricteux ([www.xtor.us](http://www.xtor.us)) saying that he had just posted two uranium glass marbles to me. Nick also assured me that these are perfectly safe, being only about five to ten times more active than background radiation.

The marbles arrived a few days ago and are sitting on my desk as we speak. Life can be a funny old thing, can't it? First I had a Geiger counter, but no source of radioactivity. Now I have a pair of radioactive marbles but no Geiger counter.
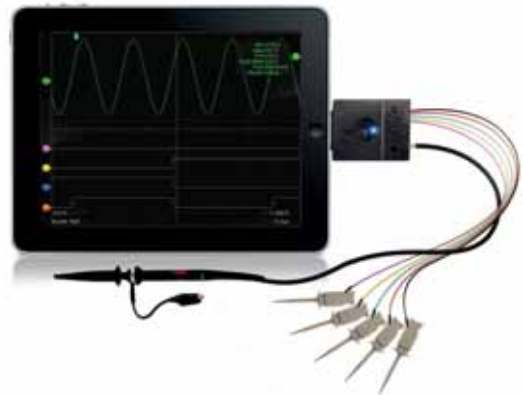
## Mega cool iPad oscilloscope

One thing that would have been very useful with regard to debugging my Geiger counter would have been an oscilloscope. Sad to relate, I don't currently own one (my old one died and I never got around to replacing it).

By another strange quirk of fate, I now have a scope sitting on my desk. This is a really clever little device called the iMSO-104 from Oscium ([www.oscium.com](http://www.oscium.com)). Now I've seen FPGA-based oscilloscopes that plug into the USB port on a PC, but I've never seen anything similar for the iPad.



In this image, the iMSO-104 is the small connector/adaptor plugged into the right-hand side of a standard iPad. The software is free to download from the Apple Store (it runs in demo mode without hardware attached). The really cool thing is that the iMSO-104 and its software are compatible with all hardware iterations of the iPad, iPhone, and iPod touch.

The iMSO-104 simultaneously supports four digital channels up to 5MHz and one analogue channel up to 12 mega-samples per second. On the one hand these aren't tremendously high performance values – on the other hand they would work well for many of my projects.

I really like the fact that it works with an iPhone and an iPod Touch (I'd like it even better if I had an iPod Touch myself). The thing is that a lot of folks already have one of these products, so the ability to turn it into an oscilloscope is rather cool.

One of the nice things about this is the intuitive usage model, which takes full advantage of the iPad-iPod-iPhone touch screens. Setting the analogue trigger level, for example, is as easy as touching the right side of the screen and swiping either up or down. Changing the vertical and horizontal scales can be achieved by moving two fingers away from each other. And you can rearrange things by touching and swiping the desired channel to any position on the screen to customise your display.

Of course, cost is also a factor. At \$297.99 (£200 approx), the iMSO-104 isn't particularly cheap. On the other hand, it's in line with FPGA/USB equivalents for PCs. Of course, it's true that FPGA/USB equivalents for PCs can typically handle higher bandwidths and trigger rates; but then you also have to lug around a PC with you.



# EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS




Flowcode 4 is one of the World's most advanced graphical programming languages for microcontrollers. The great advantage of Flowcode is that it allows those with little experience to create complex electronic systems in minutes.

Flowcode's graphical development interface allows engineers to construct a complete electronic system on-screen, develop a program based on standard flow charts, simulate the system and then produce hex code for PICmicro® microcontrollers, AVR microcontrollers, ARM microcontrollers, dsPIC and PIC24 microcontrollers.


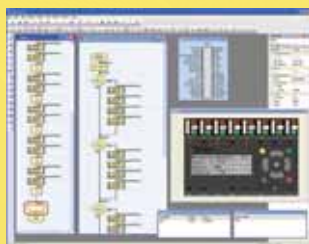
## Design

Flowcode contains standard flow chart icons and electronic components that allow you to create a virtual electronic system on screen. Drag icons and components onto the screen to create a program, then click on them to set properties and actions.



## Simulate

Once your system is designed you can use Flowcode to simulate it in action. Design your system on screen, test the system's functionality by clicking on switches or altering sensor or input values, and see how your program reacts to the changes in the electronic system.



## Download

When you are happy with your design click one button to send the program directly to your microcontroller based target. Targets include a wide range of microcontroller programmers, upstream E-blocks boards, the Formula Flowcode robot, the MIAC industrial controller, or your own system based on ECIO technology.



## FlowKit

The FlowKit can be connected to hardware systems to provide a real time debug facility where it is possible to step through the Flowcode program on the PC and step through the program in the hardware at the same time. The FlowKit can be connected to your own hardware to provide In-Circuit Debug to your finished designs.

## PRICES

Prices for each of the CD-ROMs above are: (Order form on third page)

(UK and EU customers  
add VAT to 'plus VAT'  
prices)

Hobbyist/Student .....	£45.95	inc VAT
Professional (Schools/HE/FE/Industry) .....	£149	plus VAT
Professional and Flowkit bundle .....	£175	plus VAT



# PICmicro TUTORIALS AND PROGRAMMING


## HARDWARE

### VERSION 3 PICmicro MCU development board

*Suitable for use with the three software packages listed below.*

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

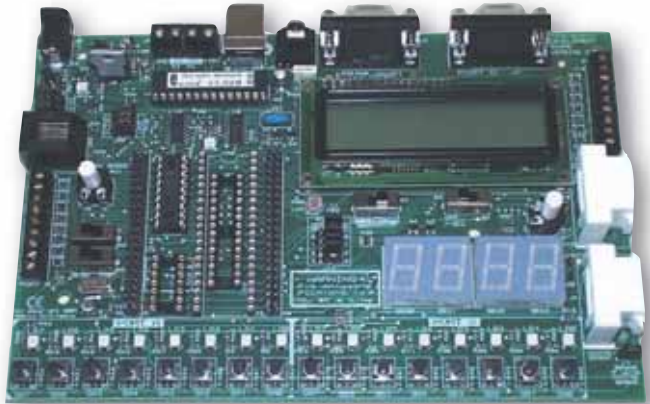- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual LEDs, quad 7-segment display and alphanumeric LCD display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



**£161 including VAT and postage, supplied with USB cable and programming software**

## SOFTWARE

### ASSEMBLY FOR PICmicro V3

**(Formerly PICtutor)**

Assembly for PICmicro microcontrollers V3.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes.

The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller, this is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed, which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.



### 'C' FOR 16 Series PICmicro Version 4

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD-ROM contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.


Flowcode will run on XP or later operating systems

### FLOWCODE FOR PICmicro V4

Flowcode is a very high level language programming system based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and LCDs. The use of macros allows you to control these devices without getting bogged down in understanding the programming. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- 16-bit arithmetic strings and string manipulation
- Pulse width modulation
- I2C.

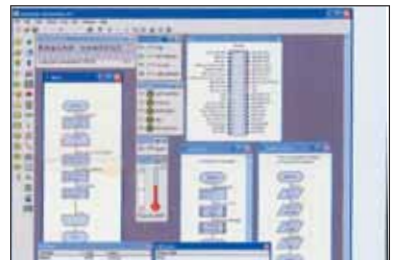New features of Version 4 include panel creator, in circuit debug, virtual networks, C code customisation, floating point and new components. The Hobbyist/Student version is limited to 4K of code (8K on 18F devices)



## PRICES

**Prices for each of the CD-ROMs above are:**  
(Order form on next page)

(UK and EU customers add VAT to 'plus VAT' prices)

Hobbyist/Student .....	£45.95	inc VAT
Professional (Schools/HE/FE/Industry) .....	£99	plus VAT
Professional 10 user (Network Licence) .....	£350	plus VAT
Site Licence .....	£699	plus VAT
Flowcode Professional (Schools/HE/FE/Industry) .....	£149	plus VAT
Flowcode 10 user (Network Licence) .....	£399	plus VAT
Flowcode Site Licence .....	£799	plus VAT


# CIRCUIT WIZARD

Circuit Wizard is a revolutionary new software system that combines circuit design, PCB design, simulation and CAD/CAM manufacture in one complete package.

Two versions are available, Standard or Professional.

By integrating the entire design process, Circuit Wizard provides you with all the tools necessary to produce an electronics project from start to finish – even including on-screen testing of the PCB prior to construction!

- \* Circuit diagram design with component library (500 components Standard, 1500 components Professional)
- \* Virtual instruments (4 Standard, 7 Professional)
- \* On-screen animation
- \* Interactive circuit diagram simulation
- \* True analogue/digital simulation
- \* Simulation of component destruction
- \* PCB Layout
- \* Interactive PCB layout simulation
- \* Automatic PCB routing
- \* Gerber export
- \* Multi-level zoom (25% to 1000%)
- \* Multiple undo and redo
- \* Copy and paste to other software
- \* Multiple document support

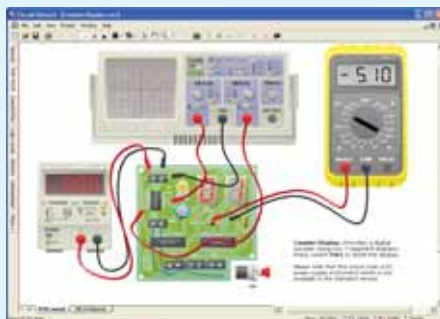


This is the software used in our *Teach-In 2011* series.  
Standard **£61.25** inc. VAT  
Professional **£91.90** inc. VAT

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 2000/ME/XP, mouse, sound card, web browser.
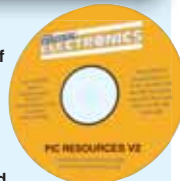
## EPE PIC RESOURCES V2

Version 2 includes the EPE PIC Tutorial V2 series of Supplements (EPE April, May, June 2003)



The CD-ROM contains the following Tutorial-related software and texts:

- EPE PIC Tutorial V2 complete series of articles plus demonstration software, John Becker, April, May, June '03
- PIC Toolkit Mk3 (TK3 hardware construction details), John Becker, Oct '01
- PIC Toolkit TK3 for Windows (software details), John Becker, Nov '01

Plus 18 useful texts to help YOU get the most out of your PIC programming.

Price **£14.75** inc. VAT

## ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 jpg images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details).



Now contains Irfan View image software for Windows, with quick-start notes included.

Price **£19.95** inc. VAT

### Please send me: CD-ROM ORDER FORM



- ☐ Assembly for PICmicro V3
- ☐ 'C' for 16 Series PICmicro V4
- ☐ Flowcode for PICmicro
- ☐ Flowcode for AVR
- ☐ Flowcode for ARM
- ☐ Flowcode for dsPIC & PIC24

#### Version required:

- ☐ Hobbyist/Student
- ☐ Professional
- ☐ Professional 10 user
- ☐ Professional + Flowkit
- ☐ Site licence

Note: The software on each version is the same, only the licence for use varies.

- ☐ PICmicro Development Board V3 (hardware)

- ☐ Circuit Wizard – Standard
- ☐ Circuit Wizard – Professional
- ☐ EPE PIC Resources V2
- ☐ Electronic Components Photos

Full name: .....  
Address: .....  
Post code: ..... Tel. No: .....  
Signature: .....

- ☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £ .....
- ☐ Please charge my Visa/Mastercard/Maestro: £ .....
- Valid From: ..... Card expiry date: .....
- Card No: ..... Maestro Issue No. ....
- Card Security Code ..... (The last 3 digits on or just under the signature strip)

## ORDERING ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard/Hobbyist Version price includes postage to most countries in the world  
EU residents outside the UK add £5 for airmail postage per order

**Professional, Multiple User and Site License Versions** – overseas readers add £5 to the basic price of each order for airmail postage (**do not add VAT** unless you live in an EU (European Union) country, then add VAT at 20% or provide your official VAT registration number).

Send your order to:  
**Direct Book Service**  
**Wimborne Publishing Ltd**  
113 Lynwood Drive, Merley, Wimborne,  
Dorset BH21 1UU  
To order by phone ring  
**01202 880299. Fax: 01202 843233**  
Goods are normally sent within seven days  
E-mail: [orders@wimborne.co.uk](mailto:orders@wimborne.co.uk)  
Online shop:  
[www.epemag.com](http://www.epemag.com)

# Net Work

Alan Winstanley



## Radio Ga-Ga

**L**AST month, I shone some light on the networking technologies that are heading our way, including mains-borne networking using Homeplug or Homegrid devices. The Homeplug Power Alliance (Sony, LG, TI, ST, Maxim, Netgear, Devolo and more) follow the IEEE 1901 standard, while the Homegrid Forum (BT, Intel, Telefonica and more) went down the road of the ITU G.hn protocol instead. A low power Green PHY sub-set has energy-saving metering and Smart Grids in mind. I learned that it's theoretically possible to mix different brands of Homeplug adaptors together, but sometimes mains-borne networking would not work at all.

Reader Terry Mowles reminded me of the decade-long debate by the amateur radio associations, Radio Society of Great Britain ([www.rsgb.org/plt/](http://www.rsgb.org/plt/)) and others to have power line technology either outlawed or forced to comply with the current EMC laws. In the UK, vociferous critics of this mains-borne technology include radio amateurs, with claims and counter-claims of interference being caused by power line technology to HF radio bands, emergency services and civil aviation communications. There's even the suggestion that street lamp-posts could become low-power radio beacons transmitting HF data.

The RSGB fears that power line adaptors could create an 'electronic smog' needing its own 'Clean Air' legislation. They published a lengthy discussion document voicing their concerns at <http://tinyurl.com/6l8kdv3>. Power line transmission clearly has its ardent critics, and it will be interesting to see how this marketplace evolves over time.

As broadband has rolled out and we gradually bury ourselves in a myriad of networked AV equipment, hooked together in a nest of HDMI (High Definition Multimedia Interface) and Ethernet cables, it's now possible to stream selected Internet-based services, such as BBC iPlayer, Facebook, Skype, Netflix and YouTube, direct to suitably equipped TV sets. This permits recent TV programmes to be replayed on a large modern TV, and video on demand or sports programmes, delivered by broadband direct to an Internet-enabled TV, is increasingly common.

However, one might need to keep an eye on monthly usage allowances in case TV or YouTube usage tips you over your allowed traffic quota. More options are being offered all the time as media barons strive to squeeze more out of our broadband connections.

## Domotically-enhanced

The area of *domotics* relates to home automation, and viewers of TV's 'Grand Designs' program will doubtless have seen fanciful interiors of ultra-modern houses, with all manner of lighting, ventilation, heating, music, TV and more controlled by a touch screen. It's now possible to control a 'domotically-enhanced' house using an iPad or iPhone app (eg, Domotica from Ingegni, see [www.ingegnitech.com/en/domotica](http://www.ingegnitech.com/en/domotica)). A number of mains, wireless and bus-based systems are already available. They offer the home automation enthusiast plenty to go at, and doubtless the price will eventually fall.

Peripherals that run on a home entertainment network have also arrived on the market. Sony's SMP-N100 network audio-video player, for example, is both Ethernet and WiFi enabled, allowing you to stream your AV content around the home, and even control it with an iPhone, iPod or some Android-based mobile phones.



*Sony SMP-N100 media player points the way towards running a domestic network to host your music, video and photos*



*Rear view of Sony SMP-N100 showing LAN, video and HDMI ports to connect to the latest multimedia equipment.*

## It's in our DLNA

Trying to plumb a complex HD system together, especially when differing brands of goods are used, could present its own problems, something which the Digital Living Network Alliance hopes to overcome. Just as computer-technology USB devices are plug-and-play interoperable, in the digital media world DLNA-certified devices strive to work together while avoiding compatibility problems. If you are contemplating updating your A/V equipment, then dipping your toes at [www.dlna.org](http://www.dlna.org) will help avoid you making costly mistakes in the future, and show you what to look for.

Some stand-alone network drives such as Western Digital's DLNA-compatible 'Live' are optimised to serve out your precious media collection over a DLNA-certified network. They use twin RAID-style drives to back up data, and you could stream video to your DLNA-compliant Xbox or large-screen TV, or play your music collection on an iPad. How about displaying your photo albums over the home network, using WiFi enabled digital photoframes? Nor are you tied to your own household: using remote access over the web, you can log into your system from anywhere and access files that way.

One consideration is the intrinsic and sentimental value of your media data. As BBC iPlayer users already know, media such as some TV shows or music, which are secured by Digital Rights Management (DRM) cannot be copied onto other drives. RAID drives themselves offer no cast-iron guarantee of total data protection either. Rather, protection is provided on the basis that if one drive fails then the other drive (hopefully) keeps running, which saves your data



from total loss. At that point, you have to drop what you're doing and back up your data and rebuild the RAID drive array promptly. (Consider whether your domestic insurance policy covers this eventuality).

Online backups make a lot of sense, and Amazon offers 5GB free on its 'Cloud Drive' network. If you purchase MP3s from Amazon then they can be backed up automatically on your Cloud Drive, and Amazon's new Cloud Player streams music direct onto your Android phone or tablet, Mac or PC.

For the PC enthusiast who has a collection of media files to manage, Windows Home Server 2011 could be the solution. This fast-maturing home platform from Microsoft lets you stream your media files over a network and also backs them up automatically. A range of PCs optimised for use as a home media server are available, including HP's MediaSmart server range.

With an endless influx of new standards and technologies, installing a new media system in the home will increasingly see us talking of network 'clients' and 'servers' and 'network attached storage', configuring Ethernet and WiFi instead of hooking coax cables or phono leads/plugs together. I sense a new job title of 'Domestic Network Administrator' coming into vogue,

with RAID rebuilding skills and lots of spare time considered desirable!

Embedded processors appear even in the most mundane of appliances, and Russian password-recovery specialist Elcomsoft explains how they could all be harnessed for the purposes of forensically breaking passwords. Elcomsoft already realised how the graphics CPUs resident in PCs can share the computational burden of the main CPU for this type of task.

They claim that home video consoles such as the Nintendo and Playstation can outgun many a PC, and as many domestic devices now have an embedded OS, it's worth pausing for thought when they mention digital photo frames, coffee makers, SLR digital cameras and more. Many such domestic devices, claims Elcomsoft, are over-engineered in terms of utilising a computing capacity that is way beyond the level required for the task in hand.

Elcomsoft's proposal is, therefore, to utilise these spare computing cycles in the almost surreal environment of a home cloud digital network. You can read more at [www.elcomsoft.com/home\\_cloud\\_computing.html](http://www.elcomsoft.com/home_cloud_computing.html).

That's all for this month's *Net Work*. You can contact me at: [alan@epemag.demon.co.uk](mailto:alan@epemag.demon.co.uk)



**Get your magazine 'instantly' anywhere in the world – buy and download from the web.**

**TAKE A LOOK, A FREE ISSUE IS AVAILABLE**

**A one year subscription (12 issues) costs just \$19.99(US)**



**MIAC<sup>TM</sup>**  
Now you are in control



The MIAC rugged PICmicro microcontroller is an industrial grade controller which can be used to control a wide range of different electronic systems: for mains switching, motor control, sensor monitoring and much more.

**Free Flowcode 3 with every MIAC**



- ▶ Rugged PIC 18F4455
- ▶ Programmable from USB - download software provided
- ▶ Compatible with third party PICmicro, BASIC and C compilers
- ▶ Includes free Flowcode 3 graphical programming software (no upgrade rights)
- ▶ 8 digital or analogue inputs
- ▶ 4 relay outputs - 8A
- ▶ 4 motor outputs with speed control - 12V, 500mA
- ▶ 4 line 16 character display
- ▶ Control keypad
- ▶ Fully networkable via built in CAN bus
- ▶ Lab View and Visual Basic compatible - DLL supplied
- ▶ In-Circuit Debug over USB with FlowKit

**MATRIX**

[www.matrixmultimedia.com](http://www.matrixmultimedia.com)

# READOUT

Email: [editorial@wimborne.co.uk](mailto:editorial@wimborne.co.uk)

Matt Pulzer addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly

**WIN AN ATLAS LCR ANALYSER WORTH £79**  
An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd, will be awarded to the author of the Letter Of The Month. The Atlas LCR automatically measures inductance from 1mH to 10H, capacitance from 1pF to 10,000µF and resistance from 1Ω to 2MΩ with a basic accuracy of 1%. [www.peakelec.co.uk](http://www.peakelec.co.uk)

## ★ LETTER OF THE MONTH ★

### Interference from mains-borne networking

Dear Editor

Your columns on home networking have been interesting, but there is one point about them you may have missed.

There is currently a large debate and push by the amateur radio associations, RSGB (Radio Society of Great Britain) and individuals either to have them made illegal or comply with the current EMC laws.

Some manufacturers are pushing for an exemption from EMC legislation. In their

current form, they do not comply with the EMC regulations, producing far in excess of the allowable interference to radio reception. This interference has been known to interfere with emergency services communications.

Living in Australia, I can't point you to any local sources of information other than the RSGB, but there is a reasonable amount posted on the Internet.

**Terry Mowles, by email**

*Alan Winstanley replies:  
I've touched upon Homeplug in the past*

*and was made aware of some of the criticism of the technology due to the possibility of interference. This is an important aspect, given that all electrical devices sold in the EU have to be CE approved – meaning that, among other things, they have to neither generate interference nor be adversely affected by any interference that they might be subjected to.*

*Possibly more extensive testing is needed, and it will be interesting to see whether the regulations are manipulated or relaxed in order to accommodate this form of mains-borne networking.*

### Current burden

Dear Editor

The design of the current adapter for multimeters by David L Jones in May's *EPE* is very good and a useful add-on to a DMM.

It brings to light the principle that no measurement can be made without affecting the quantity measured by the act of measurement. The design presented shows how that effect can be reduced for the case of current measurement by inserting a series resistor and measuring the volt drop.

This, however, set me thinking about the case where the current is measured by means of its magnetic field to minimise the effect of the measurement. My old AVO has a 50µA moving-coil meter, which drops 125mV for full-scale reading due to the resistance of the coil. If it was made from a superconductor operating with zero resistance, would it drop 0V at 50µA?

This seems to suggest that in the steady state there is no 'burden'. However, the energy required to move the coil must come from the circuit during the time when the coil is moving from rest and back-EMFs are induced.

So presumably there is a transient 'burden'. If a Hall effect device is used to detect the current via its magnetic field, what is the mechanism for the current to detect that it is being measured and hence feel the effect of the measurement?

**Ken Naylor, by email**

*Thank you for your interesting enquiry Ken. You are right, all observations will 'disturb' the observed, an effect of particular significance in quantum physics and described by the Heisenberg uncertainty*

*principle. While EPE readers may not be interested in measuring parameters on the atomic scale, it is always worth remembering that a measurement should interfere as little as possible with what is being measured.*

*A Hall effect device will interact with a magnetic field and hence it will, to a small extent, draw power from the circuit, altering the value of current slightly. However, the effect is small and can usually be discounted – a more serious question is how can you calibrate the Hall effect current-measuring device, given that its output will vary with the angle of its orientation in three dimensions.*

*I must confess that I have never fully got to grips with the strange world of superconductivity – I have always been 'scared off' by an observation from a physicist cousin of mine: 'Only three people really understand superconductivity; one of them is mad and the other two don't agree'.*

### More on PIC/Excel communication

Dear Editor

When I sent my initial email regarding the import of data to MS Excel from a PIC, I did not expect the number and quality of the responses published in *EPE*. I am therefore pleased to see these.

However, what I was looking for, and I am convinced I saw it done in *EPE* many years ago, is the 'live' import into MS Excel without going down the intermediary route of sending the data to a temporary holding file first, and then importing it into Excel as a second operation. I believe such a technique was in either an *Interface* or *PIC 'n Mix* article.

I have taught myself JAL for PICs and have been able to get a PIC 16F88 to measure and convert analogue voltages and send them as csv files to a PC via an RS232 serial connection, as was suggested by respondents to my letter.

If one of your readers can remember the article and point me to it, or give information on configuring MS Excel to receive RS232 data directly I would appreciate it.

Many thanks from a long time reader/subscriber of *EPE*.

**Bob White, Clevedon**

*Last call for those with long memories – anyone remember an article with the technique Bob describes?*

Dear Editor

Following up on the Bob White/David Hannaford letters about capturing data into Excel. I have, recently, been involved in converting data from files and inserting it into Excel workbooks using the VSTO (Visual Studio to Office) API in VB.Net 4.0. Using this interface, it is a simple matter to open a workbook, insert data and format cells and then saving the result using only a small number of VB.net commands.

Using VSTO and .Net, Bob would not need to extract the data from Hyperterm, into files, before importing it into Excel.

VSTO is a Microsoft API and is fully supported under the .Net framework.

**Regards, Liam Collins**

*Thank you Liam; another useful technique to consider.*

## Electronics Teach-In 3

FREE  
CD-ROM

The three sections of this book cover a very wide range of subjects that will interest everyone involved in electronics, from hobbyists and students to professionals. The first 80-odd pages of Teach-In 3 are dedicated to *Circuit Surgery*, the regular *EPE* clinic dealing with readers' queries on various circuit design and application problems – everything from voltage regulation to using SPICE circuit simulation software.

The second section – *Practically Speaking* – covers the practical aspects of electronics construction. Again, a whole range of subjects, from soldering to avoiding problems with static electricity and identifying components, are covered.

Finally, our collection of *Ingenuity Unlimited* circuits provides over 40 different circuit designs submitted by the readers of *EPE*.

The free cover-mounted CD-ROM is the complete *Electronics Teach-In 1* book, which provides a broad-based introduction to electronics in PDF form, plus interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial), together with simulations of the circuits in the Teach-In 1 series, plus Flowcode (a limited version) a high level programming system for PIC microcontrollers based on flowcharts.

The Teach-In 1 series covers everything from Electric Current through to Microprocessors and Microcontrollers and each part includes demonstration circuits to build on breadboards or to simulate on your PC. There is also a MW/LW Radio project in the series.

The contents of the book and Free CD-ROM have been reprinted from past issues of *EPE*.

160 pages+CD-ROM Order code ETI3 £8.50

### THE AMATEUR SCIENTIST 3-0 CD-ROM

CD-ROM

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards.

Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*.

Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather . . . and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems.

Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher.

Over 1,000 projects CD-ROM Order code ASICD-ROM £19.95

## PROJECT CONSTRUCTION

### IC 555 PROJECTS

E. A. Parr

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are over 70 circuit diagrams and descriptions covering basic and general circuits, motor car and model railway circuits, alarms and noise makers as well as a section on 556, 558 and 559 timers. (Note. No construction details are given.) A reference book of invaluable use to all those who have any interest in electronics, be they professional engineers or designers, students or hobbyists.

167 pages Order code BP44 £5.49

### HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT

R. A. Penfold

This book explains the basic function of an oscilloscope, gives a detailed explanation of all the standard controls, and provides advice on buying. A separate chapter deals with using an oscilloscope for fault finding on linear and logic circuits, plenty of example waveforms help to illustrate the control functions and the effects of various fault conditions. The function and use of various other pieces of test equipment are also covered, including signal generators, logic probes, logic pulser and crystal calibrators.

104 pages Order code BP267 £5.49

# DIRECT BOOK SERVICE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS AND CD-ROMS SEE THE UK SHOP ON OUR WEBSITE – [www.epemag.com](http://www.epemag.com)

All prices include UK postage

### ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages Order code BP392 £5.99

### TEST EQUIPMENT CONSTRUCTION

R. A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:-

AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Multivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe. The designs are suitable for both newcomers and more experienced hobbyists.

104 pages Order code BP248 £4.49

## COMPUTING

### ELECTRONICS TEACH-IN 2 CD-ROM

CD-ROM

#### USING PIC MICROCONTROLLERS A PRACTICAL INTRODUCTION

This *Teach-In* series of articles was originally published in *EPE* in 2008 and, following demand from readers, has now been collected together in the *Electronics Teach-In 2* CD-ROM.

The series is aimed at those using PIC microcontrollers for the first time. Each part of the series includes breadboard layouts to aid understanding and a simple programmer project is provided.

Also included are 29 *PIC N' Mix* articles, also republished from *EPE*. These provide a host of practical programming and interfacing information, mainly for those that have already got to grips with using PIC microcontrollers.

An extra four part beginners guide to using the C programming language for PIC microcontrollers is also included.

The CD-ROM also contains all of the software for the *Teach-In 2* series and *PIC N' Mix* articles, plus a range of items from Microchip – the manufacturers of the PIC microcontrollers. The material has been compiled by Wimborne Publishing Ltd. with the assistance of Microchip Technology Inc.

The Microchip items are: MPLAB Integrated Development Environment V8.20; Microchip Advance Parts Selector V2.32; Treelink; Motor Control Solutions; 16-bit Embedded Solutions; 16-bit Tool Solutions; Human Interface Solutions; 8-bit PIC Microcontrollers; PIC24 Microcontrollers; PIC32 Microcontroller Family with USB On-The-Go; dsPIC Digital Signal Controllers.

CD-ROM Order code ETI2 CD-ROM £9.50


### COMPUTING FOR THE OLDER GENERATION

Jim Gatenby

Among the many practical and useful ideas for using your PC that are covered in this book are: Choosing, setting up and understanding your computer and its main components. Writing letters, leaflets, invitations, etc., and other word processing jobs. Keeping track of your finances using a spreadsheet. Recording details of holidays and other ideas using a database. Using the Internet to find useful information, and email to keep in touch with family and friends. Making 'back-up' copies of your work and checking for viruses. How to use Windows XP to help people with impaired vision, hearing or mobility.

308 pages Order code BP601 £8.99

## RADIO

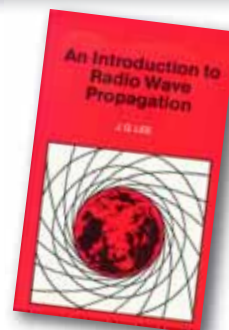

### AN INTRODUCTION TO RADIO WAVE PROPAGATION

J.G. Lee

Radio wave propagation is one of the more important discoveries made in the early 20th century. Although technology lagged behind early experimenters pursued this newly discovered phenomenon eagerly for, in understanding the physics of propagation, they were discovering more about our Universe and its workings.

Radio wave propagation has its origins in the world of solar physics. The Sun's radiation provides the mechanism for the formation of the ionosphere. How the ionosphere is formed, and how it provides long-distance communication, is carefully explained. Non-ionospheric propagation, including 'moonbounce' or satellite communications, is covered as well.

This book has been written with the average electronic hobbyist in mind. Technical language and mathematics have been kept to a minimum in order to present a broad, yet clear, picture of the subject. The radio amateur, as well as the short-wave listener, will find explanations of the propagation phenomena which both experience in their pursuit of communications enjoyment.

116 pages Order code BP293 £4.45

FOR MORE BOOKS & CD-ROMS CHECK OUT [www.epemag.com](http://www.epemag.com)



# FAULT FINDING, CIRCUITS AND DESIGN

## STARTING ELECTRONICS

Third Edition  
Keith Brindley

A punchy practical introduction to self-build electronics. The ideal starting point for home experimenters, technicians and students who want to develop the real hands-on skills of electronics construction.

A highly practical introduction for hobbyists, students, and technicians. Keith Brindley introduces readers to the functions of the main component types, their uses, and the basic principles of building and designing electronic circuits. Breadboard layouts make this very much a ready-to-run book for the experimenter, and the use of multimeter, but not oscilloscopes, and readily available, inexpensive components makes the practical work achievable in a home or school setting as well as a fully equipped lab.

288 pages

Order code NE42 £15.99

## HOW ELECTRONIC THINGS WORK – AND WHAT TO DO WHEN THEY DON'T

Robert Goodman


You never again have to be flummoxed or flustered or taken for a ride by a piece of electronics equipment. With this fully illustrated, simple-to-use guide, you will get a grasp on the workings of the electronic world that surrounds you – and even learn to make your own repairs.

You don't need any technical experience. This book gives you: Clear explanations of how things work, written in everyday language. Easy-to-follow, illustrated instructions on using test equipment to diagnose problems. Guidelines to help you decide for or against professional repair. Tips on protecting your expensive equipment from lightning and other electrical damage, lubrication and maintenance suggestions.

Covers: colour TVs, VCRs, radios, PCs, CD players, printers, telephones, monitors, camcorders, satellite dishes, and much more!

394 pages

Order code MGH3 £21.99

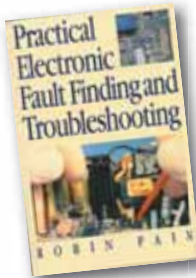


## PIC IN PRACTICE (2nd Edition)

David W. Smith

A graded course based around the practical use of the PIC microcontroller through project work. Principles are introduced gradually, through hands-on experience, enabling hobbyists and students to develop their understanding at their own pace. The book can be used at a variety of levels.

Contents: Introduction to the PIC microcontroller; Programming the 16F84 microcontroller; Introductory projects; Headers, porting code – which micro?; Using inputs; Keypad scanning; Program examples; The 16C54 microcontroller; Alphanumeric displays; Analogue to digital conversion; Radio transmitters and receivers; EEPROM data memory; Interrupts; The 12 series 8-pin microcontroller; The 16F87X microcontroller; The 16F62X microcontroller; Projects; Instruction set, files and registers; Appendices; Index.

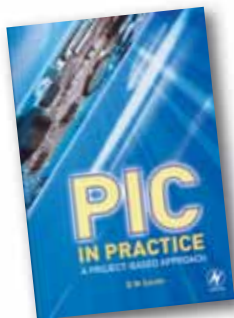

308 pages

Order code NE39 £24.99

## PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain

To be a real fault finder, you must be able to get a feel for what is going on in the circuit you are examining. In this book Robin Pain explains the basic techniques needed to be a fault finder.

Simple circuit examples are used to illustrate principles and concepts fundamental to the process of fault finding. This is not a book of theory, it is a book of practical tips, hints and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in

search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialised.

The fundamental principles of analogue and digital fault finding are described (although, of course, there is no such thing as a "digital fault" – all faults are by nature analogue). This book is written entirely for a fault finder using only the basic fault-finding equipment: a digital multimeter and an oscilloscope. The treatment is non-mathematical (apart from Ohm's law) and all jargon is strictly avoided.

274 pages

Order code NE22 £41.99

## A BEGINNERS GUIDE TO CMOS DIGITAL ICs

R. A. Penfold

Getting started with logic circuits can be difficult, since many of the fundamental concepts of digital design tend to seem rather abstract, and remote from obviously useful applications. This book covers the basic theory of digital electronics and the use of CMOS integrated circuits, but does not lose sight of the fact that digital electronics has numerous "real world" applications.

The topics covered in this book include: the basic concepts of logic circuits; the functions of gates, inverters and other logic "building blocks"; CMOS logic i.e. characteristics, and their advantages in practical circuit design; oscillators and monostables (timers); flip/flops, binary dividers and binary counters; decade counters and display drivers.

119 pages

Order code BP333 £5.45

# AUDIO AMPS

## BUILDING VALVE AMPLIFIERS

Morgan Jones

The practical guide to building, modifying, fault-finding and repairing valve amplifiers. A hands-on approach to valve electronics – classic and modern – with a minimum of theory. Planning, fault-finding, and testing are each illustrated by step-by-step examples.

A unique hands-on guide for anyone working with valve (tube in USA) audio equipment – as an electronics experimenter, audiophile or audio engineer.

Particular attention has been paid to answering questions commonly asked by newcomers to the world of the vacuum tube, whether audio enthusiasts tackling their first build, or more experienced amplifier designers seeking to learn the ropes of working with valves. The practical side of this book is reinforced by numerous clear illustrations throughout.

368 pages

Order code NE40 £29.00

## VALVE AMPLIFIERS

Second Edition. Morgan Jones

This book allows those with a limited knowledge of the field to understand both the theory and practice of valve audio amplifier design, such that they can analyse and modify circuits, and build or restore an amplifier. Design principles and construction techniques are provided so readers can devise and build from scratch, designs that actually work.

The second edition of this popular book builds on its main strength – exploring and illustrating theory with practical applications. Numerous new sections include: output transformer problems; heater regulators; phase splitter analysis; and component technology. In addition to the numerous amplifier and preamplifier circuits, three major new designs are included: a low-noise single-ended LP stage, and a pair of high voltage amplifiers for driving electrostatic transducers directly – one for headphones, one for loudspeakers.

288 pages

Order code NE33 £40.99

## BOOK ORDER FORM

Full name: .....

Address: .....

.....

.....

..... Post code: ..... Telephone No: .....

Signature: .....

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £ .....

☐ Please charge my card £ ..... Card expiry date: .....

Card Number ..... Maestro Issue No. ....

Valid From Date ..... Card Security Code ..... (the last three digits on or just below the signature strip)

Please send book order codes: .....

.....

Please continue on separate sheet of paper if necessary

## BOOK ORDERING DETAILS

**All prices include UK postage.** For postage to Europe (air) and the rest of the world (surface) please add £3 per book. For the rest of the world airmail add £4 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, or Maestro to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 113 LYNWOOD DRIVE, MERLEY, WIMBORNE, DORSET BH21 1UU.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

For a further selection of books see the next two issues of *EPE*.  
Tel 01202 880299 Fax 01202 843233. E-mail: [dbs@wimborne.co.uk](mailto:dbs@wimborne.co.uk)  
Order from our online UK shop at: [www.epemag.com](http://www.epemag.com)

# PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the *PCB Service*, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. Double-sided boards are **NOT plated through hole** and will require 'vias' and some components soldering to both sides. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Tel: 01202 880299; Fax 01202 843233; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.com.** Cheques should be crossed and made payable to *Everyday Practical Electronics (Payment in £ sterling only)*.

**NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photocopies of articles are available if required – see the Back Issues page for details. WE DO NOT SUPPLY KITS OR COMPONENTS FOR OUR PROJECTS.**

**Please check price and availability in the latest issue. A large number of older boards are listed on, and can be ordered from, our website.**

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	ORDER CODE	COST
JUNE '10		
★ PIC-Based Musical Tuning Aid	756	£9.06
★ Water Tank Level Meter – Base	757	} set £7.67
– Switch	758	
★ DSP Musicolour	759	} set £16.49
– Main	760	
– Display		
JULY '10		
★ ColdAlert Hypothermia Alarm	761	£7.68
★ Swimming Pool Alarm	762	£8.37
AUGUST '10		
★ PIC-Based Flexitimer (double-sided)	763	£12.91
DSP Musicolour – Remote Control Receiver	764	£5.93
★ UV Lightbox – Exposure Controller	765	} set £9.77
– Display/Timer	766	
Ultra LD 200W Power Amplifier (double-sided)	767	£15.52
SEPTEMBER '10		
Ultra-LD 200W Power Amplifier – Power Supply	768	£8.37
Low-Voltage Adjustable Regulator	769	£6.81
Balanced/Unbalanced Converter	770	£7.68
Planet Jupiter Receiver (double-sided)	771	£15.00
OCTOBER '10		
Bridge Adaptor For Stereo Power Amps	770	£7.68
CDI Module For Small Motors	772	£6.63
★ LED Strobe and Tachometer – 1		} pair £8.37
– Main Board	775	
– Switch Board	776	
NOVEMBER '10		
★ Railpower – Main Board	773	} pair £14.83
– Display Board	774	
★ LED Strobe and Tachometer – 2		} pair £7.15
– Photo-Interrupter	777	
– IR Reflect Amp	778	
★ USB Clock with LCD Readout – 1	779	£7.85
Balanced MIC Preamp for PCs and MP3 Players	780	£8.72
DECEMBER '10		
12V Speed Controller or 12V Lamp Dimmer	781	£6.99
★ Digital RF Level & Power Meter		} set £10.81
– Main Board	783	
– Head-end Board	784	
– RF Attenuator Board	785	
JANUARY '11		
★ Multi-Purpose Car Scrolling Display		} pair £12.21
– Main Board	786	
– Display Board	787	
USB-Sensing Mains Power Switch	788	£9.77
★ 433MHz UHF Remote Switch		} pair £10.12
– Transmitter	789	
– Receiver	790	

PROJECT TITLE	ORDER CODE	COST
<b>FEBRUARY '11</b>		
Time Delay Photoflash Trigger	791	£9.72
Tempmaster Mk.2	792	£8.59
<b>MARCH '11</b>		
★ GPS Synchronised Clock	793	£8.02
★ Digital Audio Millivoltmeter	794	£11.34
Theremin	795	£10.53
USB Printer Share Switch	796	£6.80
<b>APRIL '11</b>		
Multi-Message Voice Recorder	797	£7.53
PIR-Triggered Mains Switch	798	£8.00
★ Intelligent Remote-Controlled Dimmer	799	£6.97
<b>MAY '11</b>		
★ 6-Digit GPS Clock	800	£10.69
Simple Voltage Switch For Car Sensors	801	£6.80
The µCurrent (double-sided, surface mount)	802	£11.50
★ Digital Audio Oscillator (double-sided)	803	£11.83
<b>JUNE '11</b>		
230V AC 10A Full-Wave Motor Speed Controller	804	£8.91
Precision 10V DC Voltage Reference	805	£6.48
6-Digit GPS Clock Driver (Pt.2)	806	£6.80
Musicolour IRDA Accessory	807	£6.15
<b>JULY '11</b>		
Beam-Break Flash Trigger – IR Source	808	} pair £8.10
– Detector	809	
Metal Locator	810	£7.13
Multi-Function Active Filter	812	£8.34
Active AM Loop Antenna and Amp		} pair £8.89
– Antenna/Amp	813	
– Radio Loop (inc. Varicaps)	814	




## EPE SOFTWARE

★ All software programs for *EPE* Projects marked with a star, and others previously published can be downloaded free from the Library on our website, accessible via our home page at: [www.epemag.com](http://www.epemag.com)

## PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our website ([www.epemag.com](http://www.epemag.com)); go to the 'Library' section.

## EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
Name .....			
Address .....			
Tel. No. ....			
I enclose payment of £ ..... (cheque/PO in £ sterling only) to:			
<b>Everyday Practical Electronics</b>			
  			
Card No. ....			
Valid From .....		Expiry Date .....	
Card Security No. ....		Maestro Issue No. ....	
Signature .....			

**Note:** You can also order PCBs by phone, Fax or Email or via the Shop on our website on a secure server:

<http://www.epemag.com>

# CLASSIFIED

## ADVERTISEMENTS

If you want your advertisements to be seen by the largest readership at the most economical price our classified page offers excellent value. The rate for semi-display space is £10 (+VAT) per centimetre high, with a minimum height of 2.5cm. All semi-display adverts have a width of 5.5cm. The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Phone: 01202 880299. Fax: 01202 843233. Email: [epeads@wimborne.co.uk](mailto:epeads@wimborne.co.uk). For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

### LOOKING FOR THAT SPECIAL SWITCH OR RELAY

Visit Section 19

[www.partridgeelectronics.co.uk](http://www.partridgeelectronics.co.uk)

### BOWOOD ELECTRONICS LTD

*Suppliers of Electronic Components*

Place a secure order on our website or call our sales line

All major credit cards accepted

Web: [www.bowood-electronics.co.uk](http://www.bowood-electronics.co.uk)

Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield,  
Derbyshire S40 2QR. Sales: 01246 200222

Send 60p stamp for catalogue

### MISCELLANEOUS

**VALVES AND ALLIED COMPONENTS IN STOCK.** Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

**KITS, TOOLS, COMPONENTS. S.A.E. Catalogue.** SIR-KIT ELECTRONICS, 52 Severn Road, Clacton, CO15 3RB, <http://sir-kit.webs.com>

**DUE TO BEREAVEMENT, CLEARING OUT** over 50yrs worth of components and equipment. Please email for lists [shaunmar@sky.com](mailto:shaunmar@sky.com).

### BTEC ELECTRONICS TECHNICIAN TRAINING

**NATIONAL ELECTRONICS  
VCE ADVANCED ICT  
HNC AND HND ELECTRONICS  
FOUNDATION DEGREES  
NVQ ENGINEERING AND IT  
DESIGN AND TECHNOLOGY**

**LONDON ELECTRONICS COLLEGE  
20 PENYWERN ROAD  
EARLS COURT, LONDON SW5 9SU  
TEL: (020) 7373 8721  
[www.lec.org.uk](http://www.lec.org.uk)**

### Spinvent

Invent with the  
Propeller 8-core  
32-bit microcontroller

[www.spinvent.co.uk](http://www.spinvent.co.uk)  
01603 611 216



### CPS Solar

Solar panels, solar cells, and many more alternative energy products for battery charging etc, please visit our website for further info or call

**Tel: 0870 765 2334.**

[www.solarpanelonline.co.uk](http://www.solarpanelonline.co.uk)

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-five years.

**Robot Bits**  
Robots, Arduino & more!

[www.RobotBits.co.uk](http://www.RobotBits.co.uk)  
**0845 5 191 282**

### CANTERBURY WINDINGS

UK manufacturer of toroidal transformers  
(10VA to 3kVA)

All transformers made to order. No design fees.  
No minimum order.

[www.canterburywindings.co.uk](http://www.canterburywindings.co.uk)

**01227 450810**

Single tones to melodies.  
3bits = Enable to control.  
Compose on PC. 8 tunes,  
independent within array  
of 224 note/gap + time  
cells, 6 user-wavetables.  
Preview tune/cell/wave  
via PC. A440Hz to A880Hz  
13 note-gap. Differential  
PWM 256x128 out. Videos.

[cycling.com](http://cycling.com)

**ADVERTISE HERE FOR  
JUST £25 +VAT CALL  
STEWART KEARN  
ON 01202 880299  
[STEWART.KEARN@WIMBORNE.CO.UK](mailto:STEWART.KEARN@WIMBORNE.CO.UK)**

## ADVERTISERS INDEX

CRICKLEWOOD ELECTRONICS .....	45
DISPLAY ELECTRONICS .....	80
ESR ELECTRONIC COMPONENTS .....	6
JAYCAR ELECTRONICS .....	4/5
JPG ELECTRONICS .....	80
L-TEK POSCOPE .....	17
LABCENTER .....	Cover (iv)
LASER BUSINESS SYSTEMS .....	45
MATRIX MULTIMEDIA .....	73
MICROCHIP .....	Cover (ii)
MIKROELEKTRONIKA .....	29
PEAK ELECTRONIC DESIGN .....	Cover (iii)
PICO TECHNOLOGY .....	27

QUASAR ELECTRONICS .....	2/3
SHERWOOD ELECTRONICS .....	66
SHREYANSH ELECTRONICS .....	45
STEWART OF READING .....	Cover (iii)
TECHNOBOTS .....	45

### ADVERTISEMENT OFFICES:

113 LYNWOOD DRIVE, MERLEY, WIMBORNE,  
DORSET BH21 1UU

**PHONE:** 01202 880299 **FAX:** 01202 843233

**EMAIL:** [epeads@wimborne.co.uk](mailto:epeads@wimborne.co.uk) **WEB:** [www.epemag.com](http://www.epemag.com)

For editorial address and phone numbers see page 7



# Next Month

**AUGUST '11 ISSUE  
ON SALE 14 JULY**

## SD Card Music & Speech Recorder/Player

This is a fantastic project with a multitude of uses. It's a digital recorder that stores WAV files on low-cost MMC/SD/SDHC cards. It can be used as a jukebox, a sound effects player or an expandable 'Dictaphone'. You can use it as a freestanding recorder, or in conjunction with any Windows, Mac or Linux PC.

## Input attenuator for the Digital Audio Millivoltmeter

Remember our super Digital Audio Millivoltmeter project back in March 2011? Well, it just got even better! With this add on you can now measure AC voltages up to 140V RMS. Easy to build, it's a simple switched-input divider that lets you add 40dB, 20dB or 0dB of attenuation ahead of the meter at the touch of a knob.

## Deluxe 3-channel UHF Rolling Code Remote Control – Part 1

We've shown you how to make keyless entry systems before, but this really takes the concept to another level. It's a high-security 3-button UHF transmitter and receiver system that can be used for keyless entry into homes and commercial premises and for controlling garage doors and external lighting. Three separate outputs on the receiver can be used to activate various electrical devices, such as a door strike, a motorised garage door and 230V AC lights. Up to 16 transmitters can be used with one receiver, so it's even suitable for a small business.

## Recycle It!

More free electronics from valuable discards!

## Teach-In 2011 – Part 10

Mike and Richard Tooley discuss practical aspects of test instruments, measurements and testing circuits. Plus, you definitely do not want to miss their introduction to PCB layout using the series' excellent accompanying software package, Circuit Wizard.



Content may be subject to change

# Europe's Largest Surplus Store

**20,000,000 Items on line NOW !**  
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

**We Ship  
Worldwide**

**Surplus  
Wanted**

**www.distel.co.uk**

**Display Electronics**  
29 / 35 Osborne Road  
Thornton Heath  
Surrey UK CR7 8PD

**Telephone**  
**[44] 020 8653 3333**  
**Fax [44] 020 8653 8888**

## Rechargeable Batteries With Solder Tags

### NIMH

AA 2000mAh .....	£2.82
C 4Ah .....	£4.70
D 9Ah .....	£7.60
PP3 150mAh .....	£4.95


### NICAD

AA 650mAh .....	£1.41
C 2.5Ah .....	£3.60
D 4Ah .....	£4.95
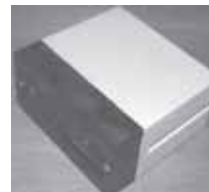
### Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = **£8.77**



Please add £1.66 + VAT = £1.95 postage & packing per order

**JPG Electronics**

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

www.JPGElectronics.com

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday



## PRE-PRODUCTION CHECK

Board Edge Defined - **CHECK**

All Components Placed - **CHECK**

All Connections Routed - **CHECK**

Power Planes Generated - **CHECK**

No Design Rule Violations - **CHECK**

# PROTEUS 7

## Design with Confidence:

The latest version of the Proteus PCB Design Software provides a multi-stage Pre-Production Check which will detect and prevent a variety of common mistakes prior to your boards being sent for manufacture.

## PROTEUS DESIGN SUITE Features:

- Hardware Accelerated Performance.
- Unique Thru-View™ Board Transparency.
- Over 35k Schematic & PCB library parts.
- Integrated Shape Based Auto-router.
- Flexible Design Rule Management.
- Polygonal and Split Power Plane Support.
- Board Autoplacement & Gateswap Optimiser.
- Direct CAD/CAM, ODB++, IDF & PDF Output.
- Integrated 3D Viewer with 3DS and DXF export.
- Mixed Mode SPICE Simulation Engine.
- Co-Simulation of PIC, AVR, 8051 and ARM7.
- Direct Technical Support at no additional cost.

All levels of the **Proteus Design Suite** include a world class, fully integrated shape-based autorouter at no additional cost - prices start from just £150 exc. VAT & delivery

**labcenter**  [www.labcenter.com](http://www.labcenter.com)  
**Electronics**

Labcenter Electronics Ltd. 53-55 Main Street, Grassington, North Yorks. BD23 5AA.  
Registered in England 4692454 Tel: +44 (0)1756 753440, Email: [info@labcenter.com](mailto:info@labcenter.com)

Visit our website or  
phone 01756 753440  
for more details





**Designed in the UK,  
Made in the UK.**

Tel. 01298 70012  
www.peakelec.co.uk  
sales@peakelec.co.uk

West Road House  
West Road  
Buxton  
Derbyshire  
SK17 6HF

**PEAK**<sup>®</sup>  
electronic design ltd

## Atlas LCR - Passive Component Analyser

The Atlas LCR (Model LCR40) is now supplied with our new premium quality 2mm plugs and sockets to allow for greater testing flexibility. Supplied with 2mm compatible hook probes as standard, others available as an option.

Test inductors (from 1uH to 10H), capacitors (1pF-10,000uF) and resistors (1Ω to 2MΩ). Auto-range and auto component selection.

Basic accuracy of 1.5%.  
Battery and user guide included.



Optional Probes

**£67.50 + VAT**

£81 inc UK VAT

Please add £3 for UK P&P

[www.stewart-of-reading.co.uk](http://www.stewart-of-reading.co.uk)

Check out our website, 1,000's of items in stock.



HP8563E SPECTRUM ANALYSER  
9KHz - 26.5GHz Synthesised..... £20A



HP33120A FUNCTION GENERATOR  
100 MicroHz - 15MHz  
Unused Boxed £595  
Used, No Moulding, No Handle £395



MARCONI 2955 RADIO  
COMMUNICATION TEST SET  
ONLY £625  
Also available Marconi 2955A & 2955B



ENI 3200L RF POWER AMPLIFIER  
250KHz-150MHz 200W 55dB

**AGILENT E4402B** Spectrum Analyser  
100Hz - 3GHz with Option 10N Tracking  
Gen; 1 DR Narrow Res; A4H GPIB,  
UKB.....£5800  
**HP 35670A** FFT Dynamic Signal Analyser  
2 Channel. Unused in original box.....£4000  
**AGILENT 83752B** Synthesised Sweeper  
0.01-20GHz.....£6000  
**HP83711B** Synthesised 1-20GHz with  
Opt IEL Attenuator.....£5000  
**AGILENT HP E4431B** Signal Generator  
250KHz-2GHz Digital Modulation.....£2750  
**MARCONI 2024** Signal Generator 9KHz-  
2.4GHz Opt 04.....£1250  
**MARCONI IFR 2030** Signal Generator  
10KHz-1.35 GHz.....£995  
**MARCONI 2022E** Synthesised AM/FM  
Signal Generator 10KHz-1.01GHz.....£500  
**HP8566A** Spectrum Analyser 100KHz-  
22GHz.....£1950  
**HP8568A** Spectrum Analyser 100KHz-  
1500MHz.....£1250  
**AVCOM PSA-37D** Spectrum Analyser  
1MHz-4.2GHz.....£-  
**IFR 1200S** Service Communication  
Monitor.....£1500  
**HP6624A** Power Supply 0-20V 0-2A  
Twice, 0-7V 0-5A; 0-50V 0.8A  
Special price.....350  
**AVO/MEGGAR FT612 AC/DC**  
breakdown tester.....£-  
**MARCONI IFR/AEROFLEX 2025** Signal  
Gen 9KHz-2.51GHz Opt 04 High Stab  
Opt 11 High Power etc As New.....£2500  
**SOLARTRON 1250** Frequency Response  
Analyser 10uHz-65KHz.....£995  
**HP3324A** Synthesised Function  
Generator 21MHz.....£500  
**HP41800A** Active Probe 5Hz-500MHz  
.....£750  
**ANRITSU MS2601A** Spectrum Analyser  
10KHz-2.2GHz 50ohm.....£750



AGILENT E4421B 250KHz-3GHz  
Signal Generator £2500

**HP53131A** Universal Counter Opt 001  
Unused Boxed 3GHz.....£850  
Unused Boxed 225MHz.....£595  
Used 225MHz.....£495  
**HP8569B** Spectrum Analyser 0.01-  
22GHz.....£1000  
**HP54616C** Oscilloscope Dual Trace  
500MHz 2GS/S Colour.....£1250  
**QUART LOCK 10A-R** Rubidium  
Frequency Standard.....£1000  
**PENDULUM CNT90** Timer/Counter  
/Analyser 20GHz.....£1950  
**ADVANTEST R3465** Spectrum  
Analyser 9KHz-8GHz.....£-  
**HP Programmable Attenuators** £300  
each  
**33320H** DC-18GHz 11db  
**33321G** DC-18GHz 70db  
Many others available  
**AGILENT E3610A** Power Supply 0-8V  
0-3A/0-15V 0-2A Unused  
**AGILENT E3611A** Power Supply 0-20V  
0-1.5A/0-35V 0-0.85V Unused  
**CIRRUS CRL254** Sound Level Meter  
with Calibrator.....£95  
**CEL328** Digital Sound Level Meter with  
CEL284/2 Acoustical Calibrator.....  
**CEL 269** Digital Sound Level Meter with  
CEL282 Acoustical Calibrator

**FLUKE SCOPEMETERS**  
99B Series II 2Ch 100MHz 5GS/G from  
£325  
97 2Ch 50MHz 25MS/S from £225

**STEWART OF READING**  
17A King Street, Mortimer,  
Near Reading RG7 3RS  
Telephone: 0118 933 1111  
Fax: 0118 933 2375  
9am - 5pm Monday - Friday

Used Equipment - **GUARANTEED**  
Prices plus Carriage and VAT

Please check availability before  
ordering or CALLING IN



**MARCONI 2945 RADIO  
COMMUNICATION TEST  
SET** with....

Opt 01 - 600 ohm Matching Unit  
Opt 03 - High Stability OCXO  
Opt 06 - Memory Card Drive with Real  
Time Clock Opt 08 - SSB Demodulator  
Opt 21 Demodulation Filters  
Opt 22 POCSAG Decode  
**Only £3,000**



HP 8569B  
Spectrum Analyser 0.01-22GHz  
£995



HP6269B Power Supply  
0-40V 0-50A £400

**AMPLIFIER RESEARCH  
POWER AMPLIFIER 1000LAM8 EPOA**